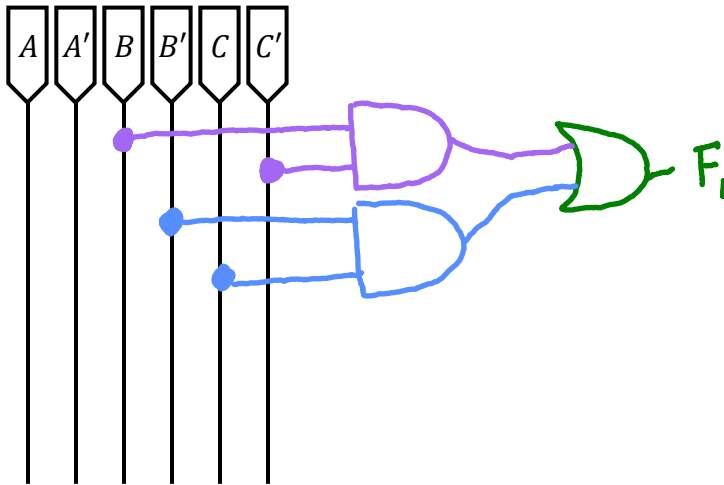


Use K-maps to reduce the expressions shown below. Your final expression should be in minimal 2-stage Sum of Products form. Draw the logic circuit to implement each function. You must use K-Maps as drawn here. Do not change the orientation or any of the labels.

For this problem the output of the previous block of the system has each of  $A, A', B, B', C, C', D$  and  $D'$  available as inputs to your circuit on the wires that are shown.


a)  $F_1(A, B, C) = \sum m(1, 2, 4, 6)$



A \ BC	BC	
	0	1
00		
01	1	1
11		
10	1	1

$$B'C + BC'$$

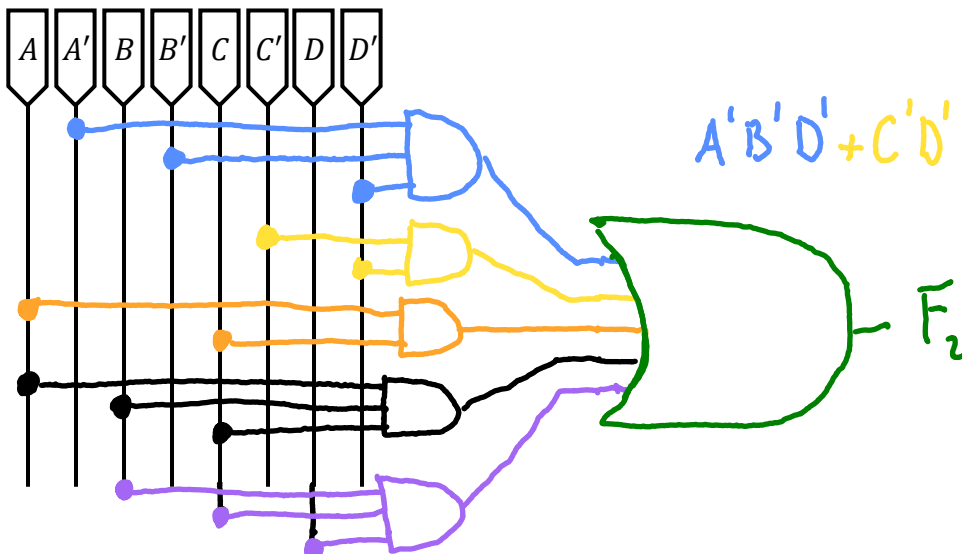b)  $F_2(A, B, C, D) = \sum m(0, 2, 4, 7, 8, 10, 11, 12, 13, 14, 15)$



AB \ CD	CD			
	00	01	11	10
00	1	1	1	1
01			1	
11		1	1	1
10	1		1	1

$$A'B'D' + C'D' + BCD + AC + ABC'$$