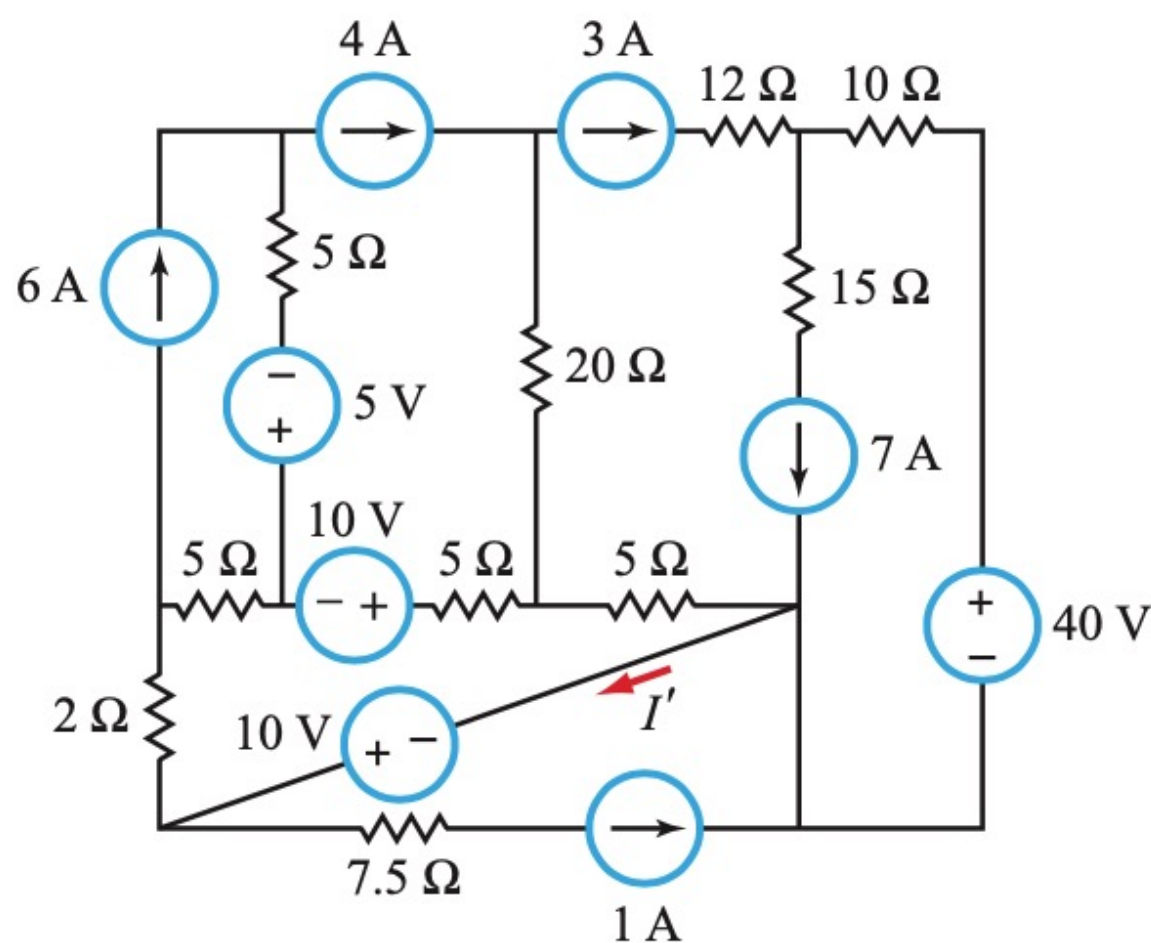




1. Identify the number of nodes and meshes in the circuit below.





**THE OHIO STATE UNIVERSITY**


---

COLLEGE OF ENGINEERING
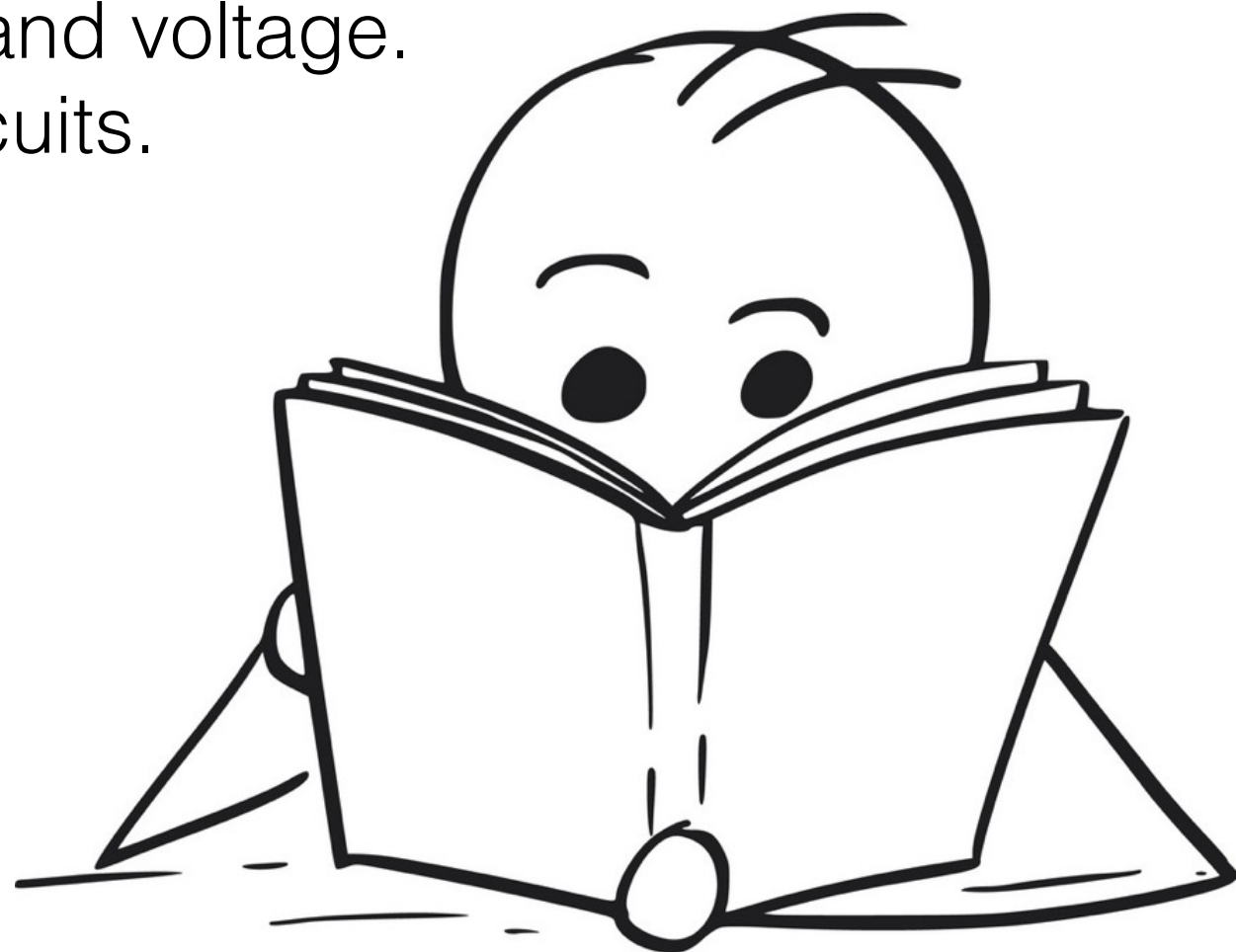
# Resistors and Kirchhoff's Laws



- Learning Objectives:
  - Understand the  $i$ - $v$  characteristic across a resistor.
  - Apply Ohm's Law.
  - Apply Kirchhoff's current and voltage laws to simple electric circuits.






- Wires are typically made of metal (silver, copper, gold).

- High conductivity ( $\sigma$ )
- Low resistivity ( $\rho$ )

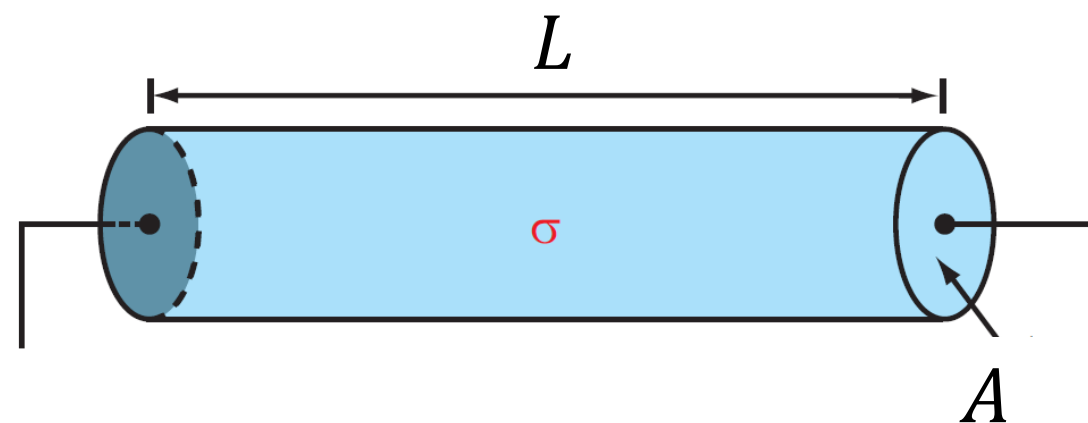electrons can move easily  
between conduction bands





wider shorter wires have  
less resistance

$$R = \rho \frac{L}{A}$$

length

cross-sectional  
area

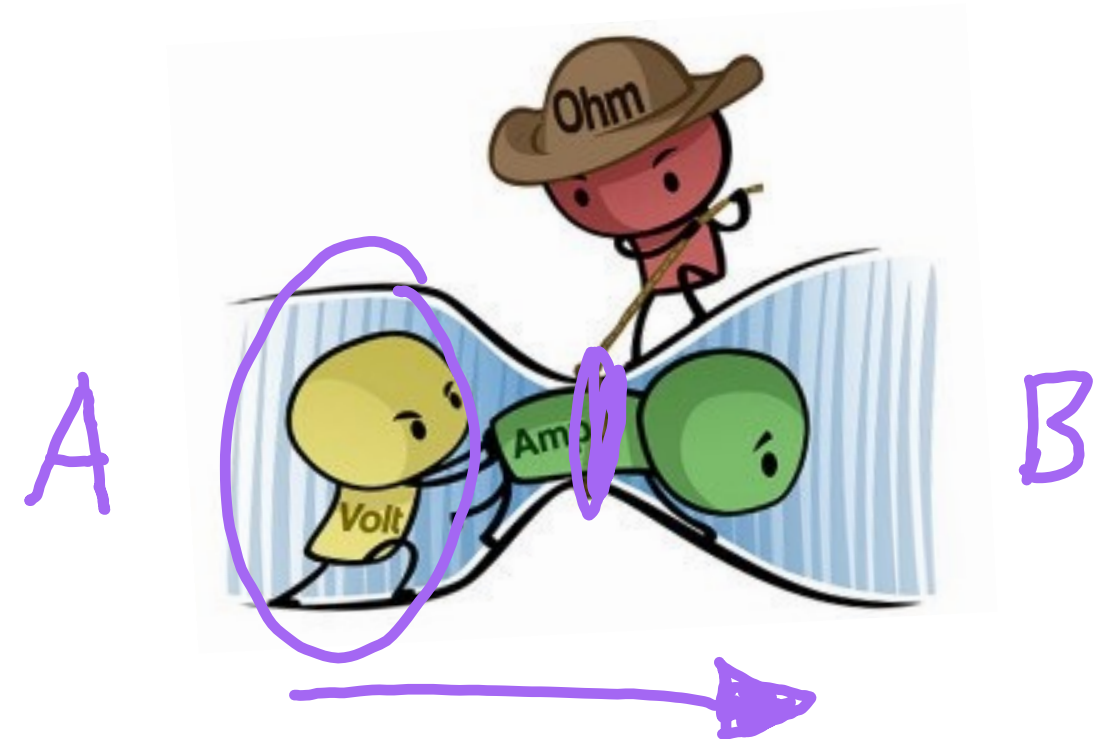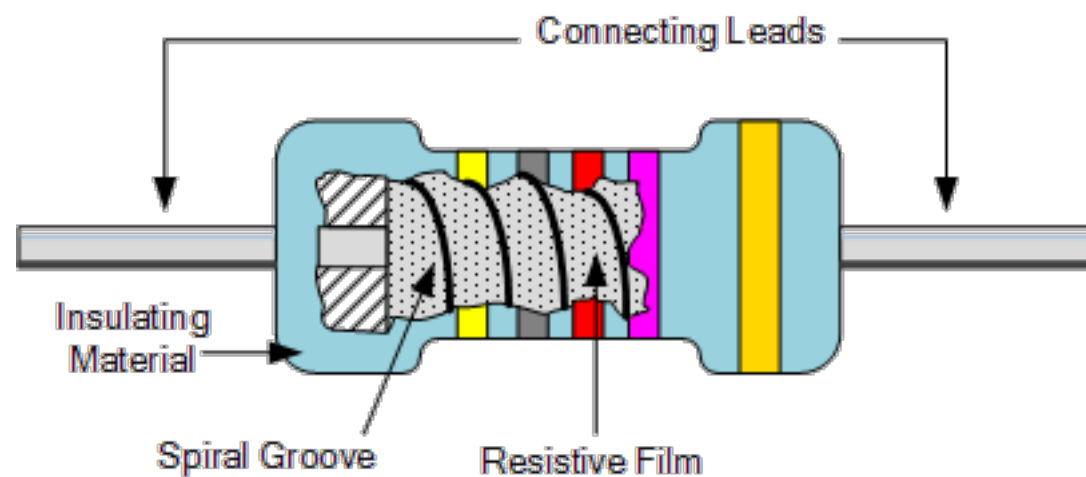- In circuits: resistance is the ability to resist flow of electric current.



circuit symbol



← complicated path for electrons flow




- Typical Resistor: “wire-wound”
  - wire wrapped around ceramic core.
  - more wraps = more length = higher resistance



- Variable Resistor: potentiometer or rheostat

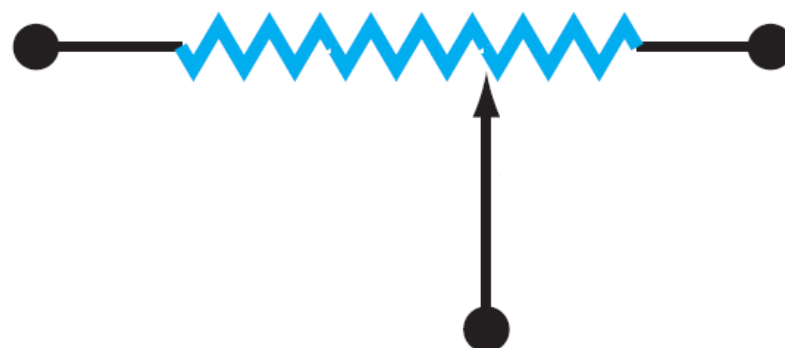- turn a knob and changes the effective length



4 bands						25 $\Omega$ , 10%
5 bands						62 M $\Omega$ , 5%
6 bands						500 k $\Omega$ , 0.25%, 15 ppm
Silver						
Gold	$b_1$	$b_2$	$b_3$	$b_4$	$b_5$	
Black	0	0	0	1		
Brown	1	1	1	10	1%	100 ppm
Red	2	2	2	100	2%	50 ppm
Orange	3	3	3	1K		15 ppm
Yellow	4	4	4	10K		25 ppm
Green	5	5	5	100K	0.5%	
Blue	6	6	6	1M	0.25%	10 ppm
Purple	7	7	7	10M	0.1%	5 ppm
Gray	8	8	8			
White	9	9	9			
	1st digit	2nd digit	3rd digit	# of zeros	Tolerance	Temperature coefficient
				$\times 10^{b_4}$		ppm/ $^{\circ}\text{C}$
4-, 5-, and 6-band color code system						




## Ohm's Law:

- Linear relationship does not apply over large ranges of voltage or current.
- Empirical relationship given by:

$$v = iR$$

- Recall that:

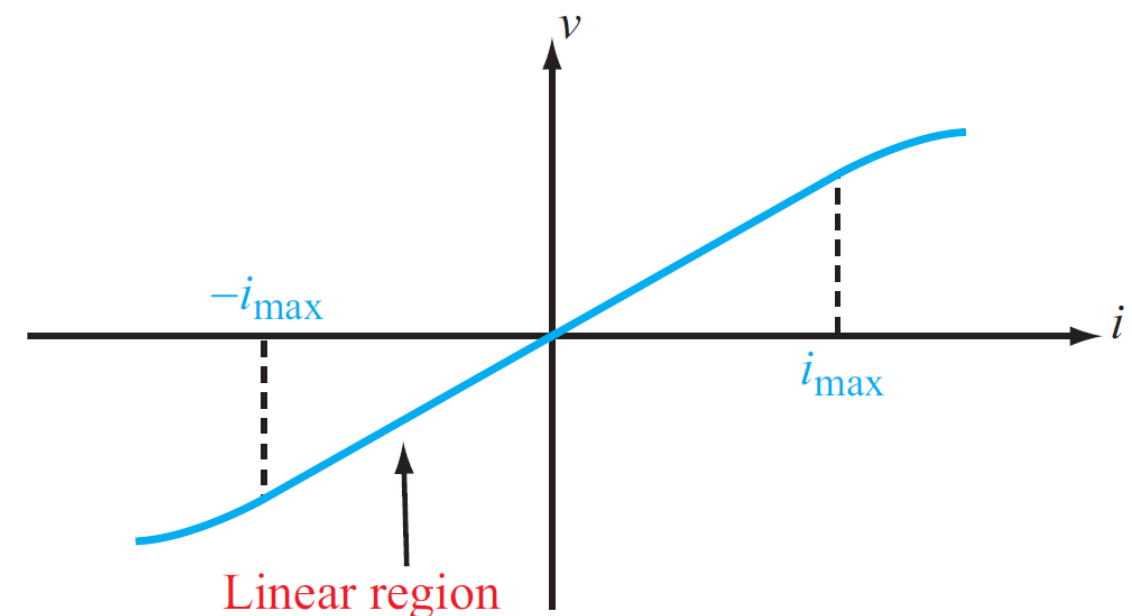

$$R = \frac{v}{i} = \left[ \frac{V}{A} \right] = [\Omega] \quad \swarrow \text{ohm's}$$



- The sum of the currents at a node must equal zero.


$$\sum_{\ell=1}^N i_{\ell} = 0$$

- Principle: charge cannot be created but must be conserved.

Pick a convention:

- $i_{in}$  = positive and  $i_{out}$  = negative.  
or
- $i_{in}$  = negative and  $i_{out}$  = positive.


$$\sum i_{in} = \sum i_{out}$$

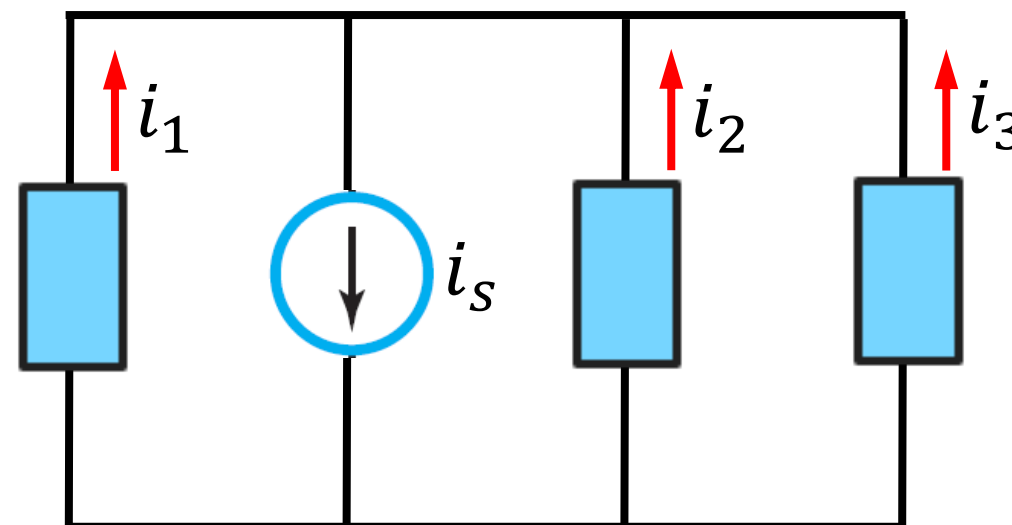





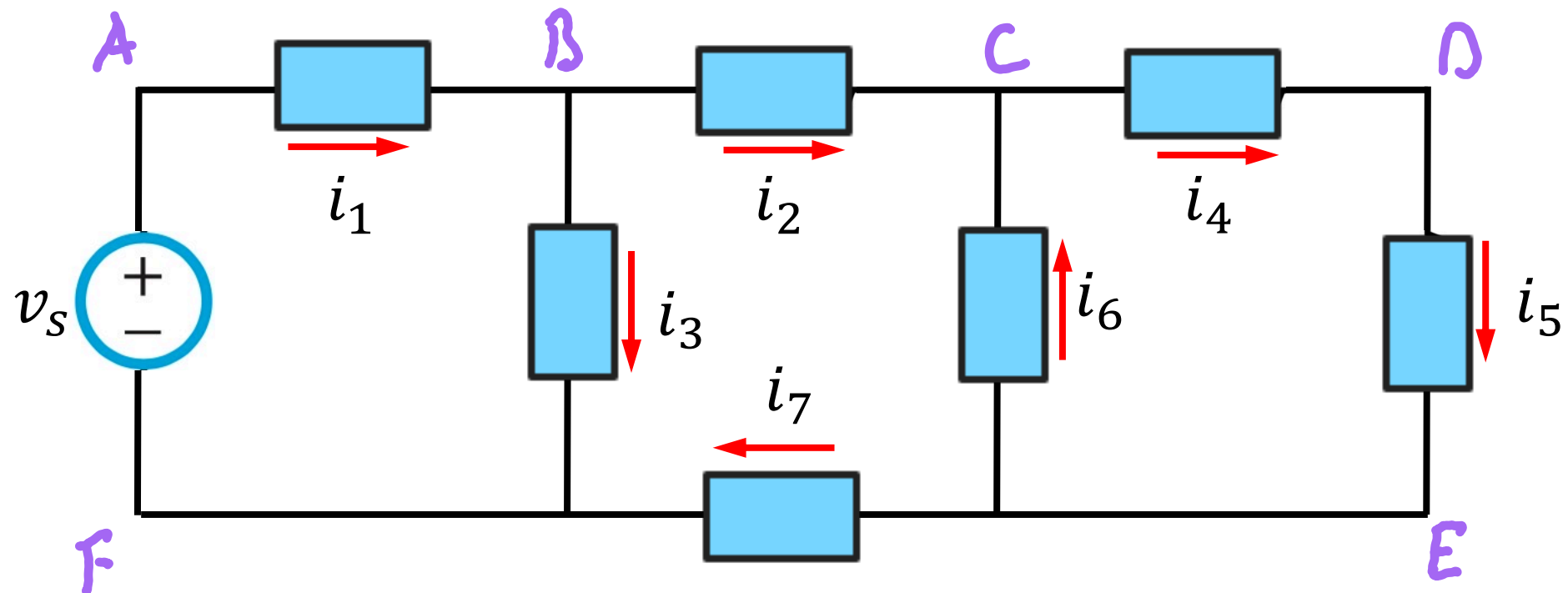How many nodes can you identify in the circuit below?  
KCL on node 3?



KCL @ C

$$i_2 + i_6 = i_4$$


KCL @ F

$$i_3 + i_7 = i_5$$





# Voltage Rise and Voltage Drop

Assume that  $v_A > v_B$

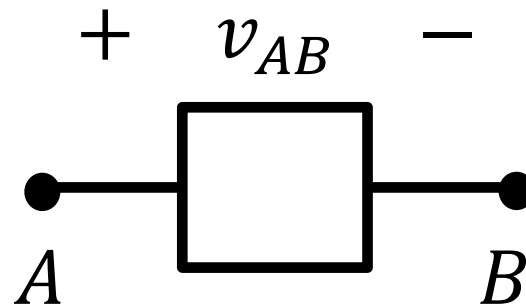

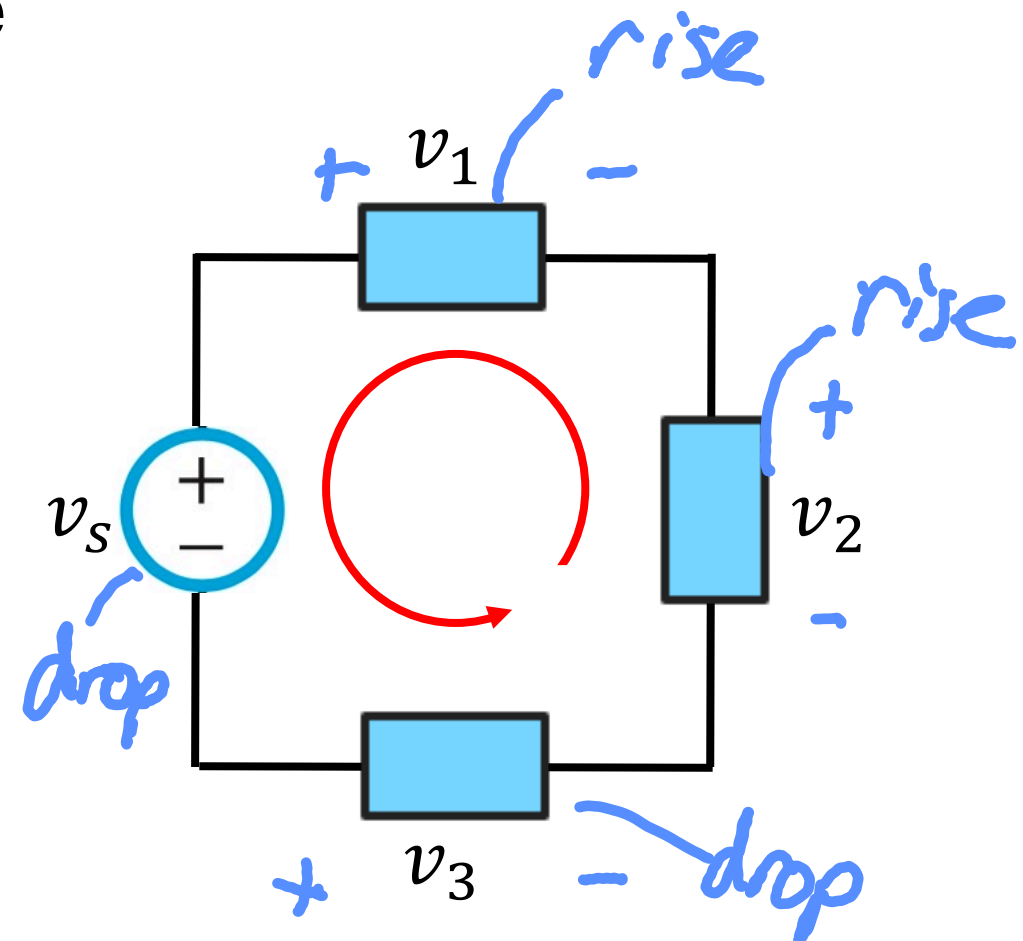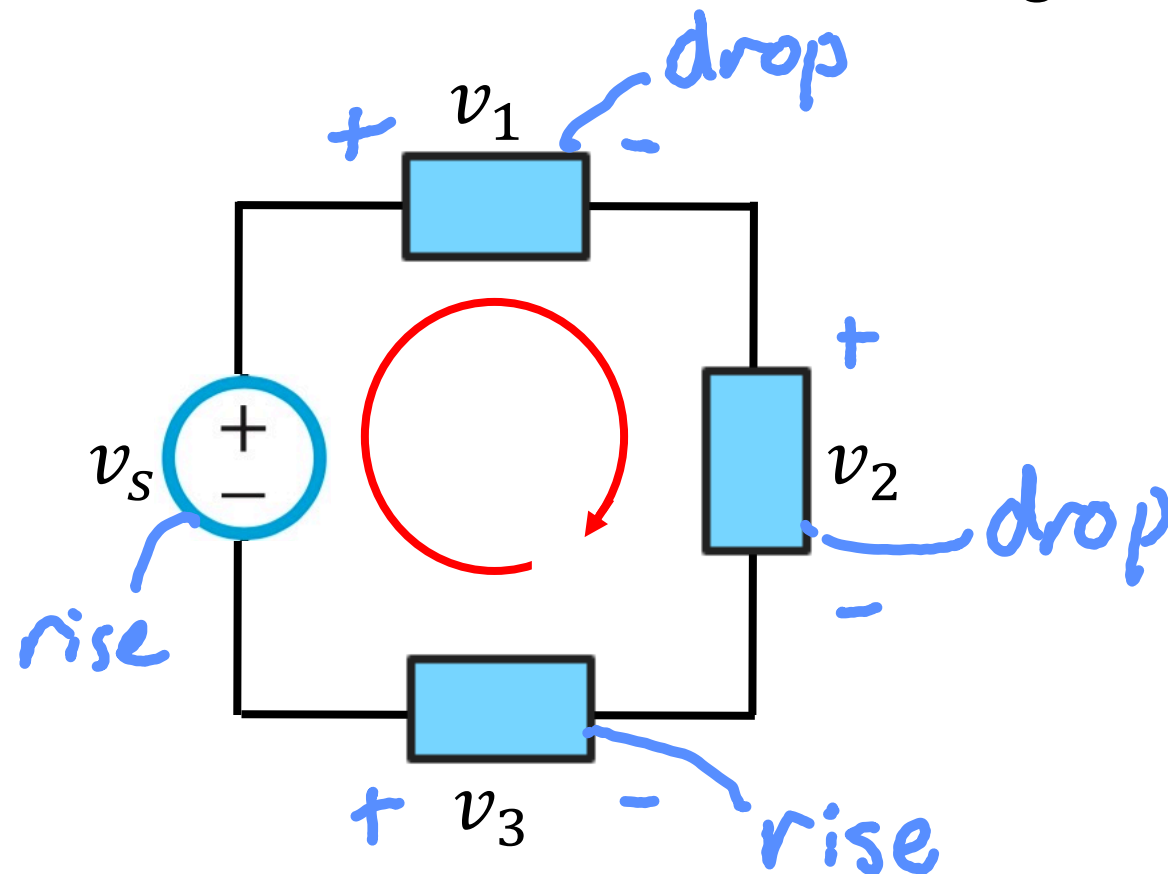- Moving:  $A \rightarrow B$  is a voltage drop  
 $B \rightarrow A$  is a voltage rise





# Kirchhoff's Voltage Law (KVL)

- The net voltage around a close loop is zero.

$$\sum_{\ell=1}^N v_{\ell} = 0$$

@ mesh  
or loop

- Principle: no energy is lost or created in an electric circuit.


Pick a convention:

- rise* = positive and *drop* = negative.  
or
- rise* = negative and *drop* = positive.

$$V_s - V_1 - V_2 - V_3 = 0$$

$$V_1 + V_2 + V_3 - V_s = 0$$


$$\sum v_{rise} = \sum v_{drop}$$

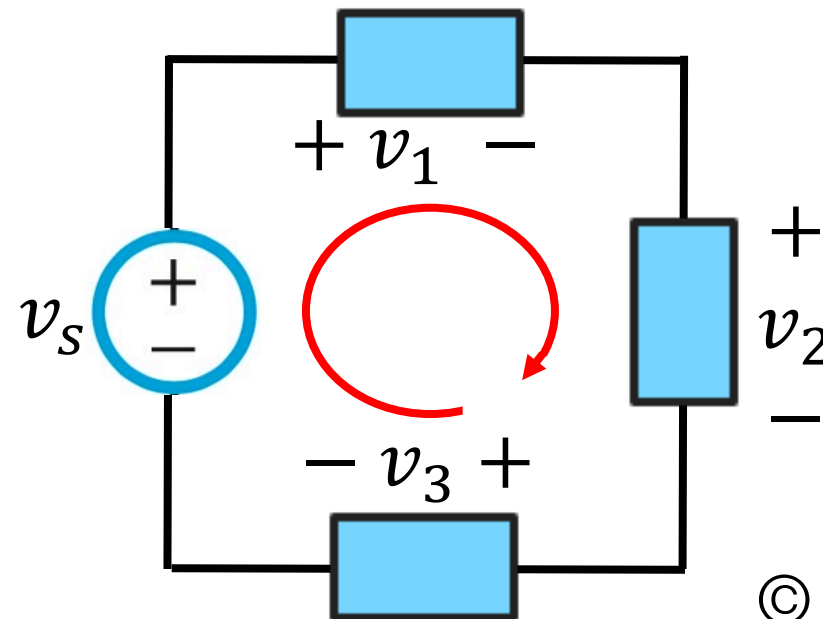



How many meshes can you identify in the circuit below?

KVL on mesh 2?

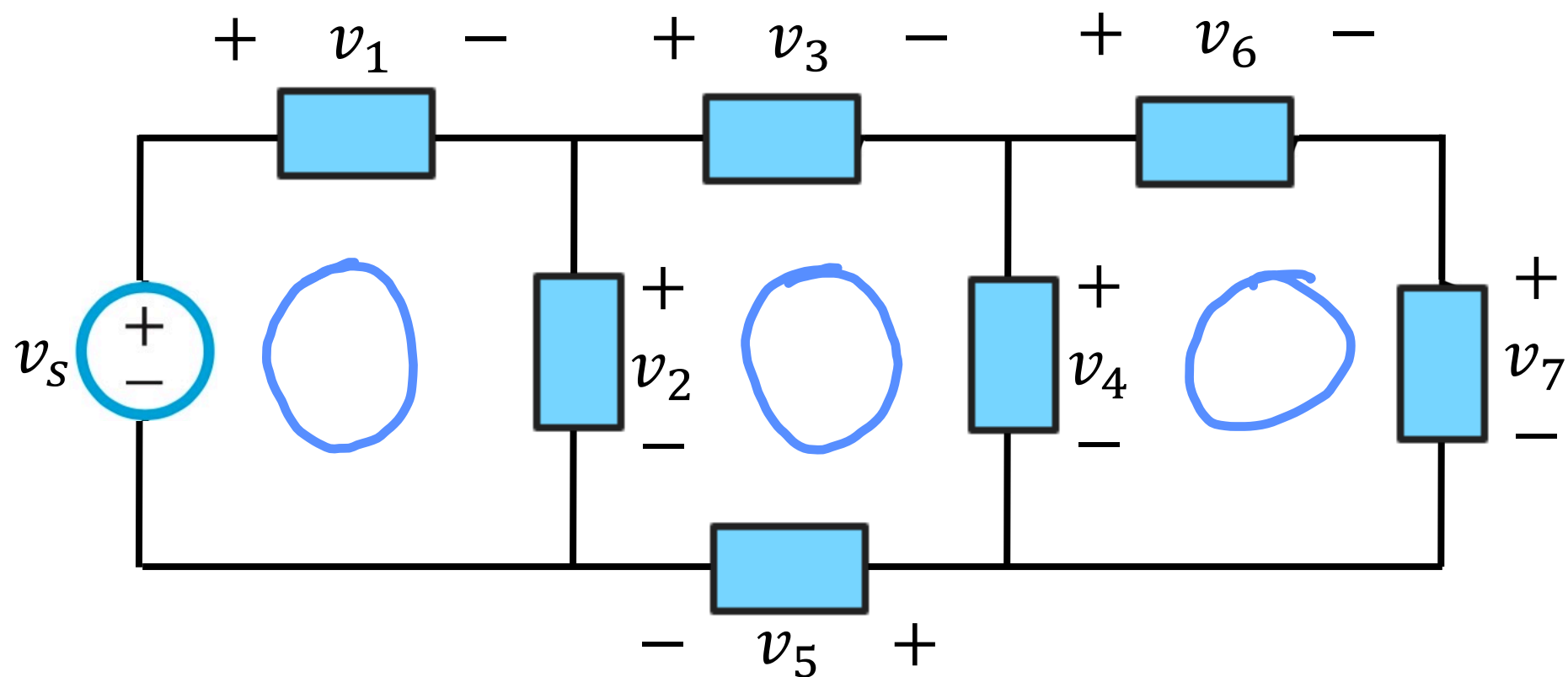


KVL 2

$$v_3 + v_4 + v_5 - v_2 = 0$$



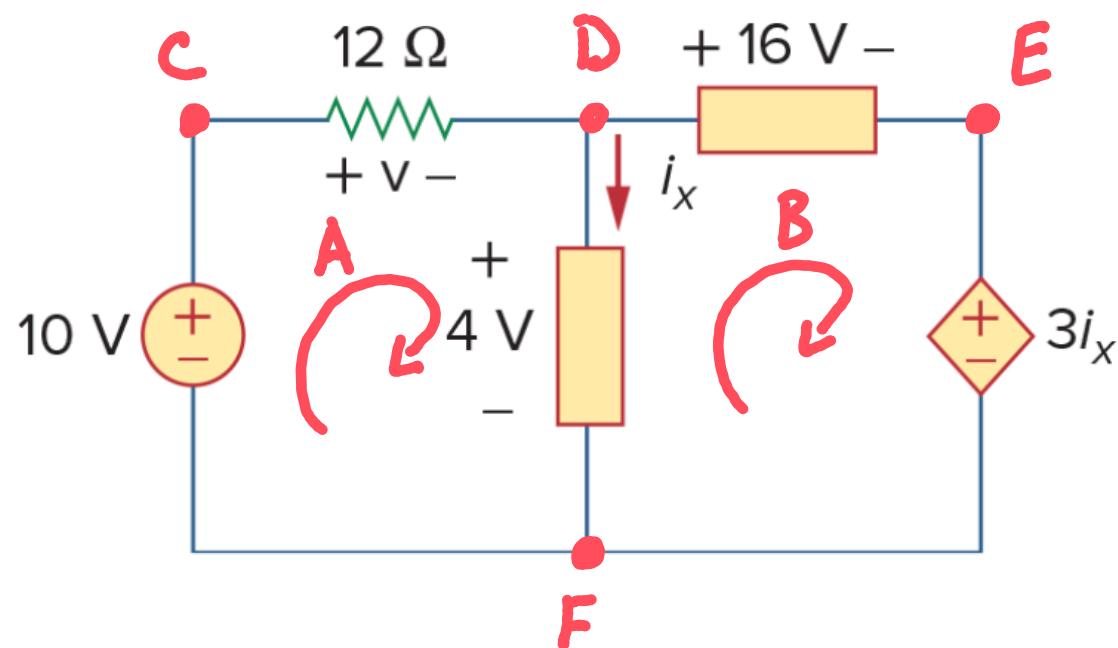Calculate  $v$  and  $i_x$  in the circuit below



KVL@A:

$$4 - 10 + v = 0$$

$$v = 6V$$

$$i_{12} = \frac{6}{12} = 0.5A$$

KVL@B:

$$16 + 3i_x - 4 = 0$$

$$i_x = -4A$$