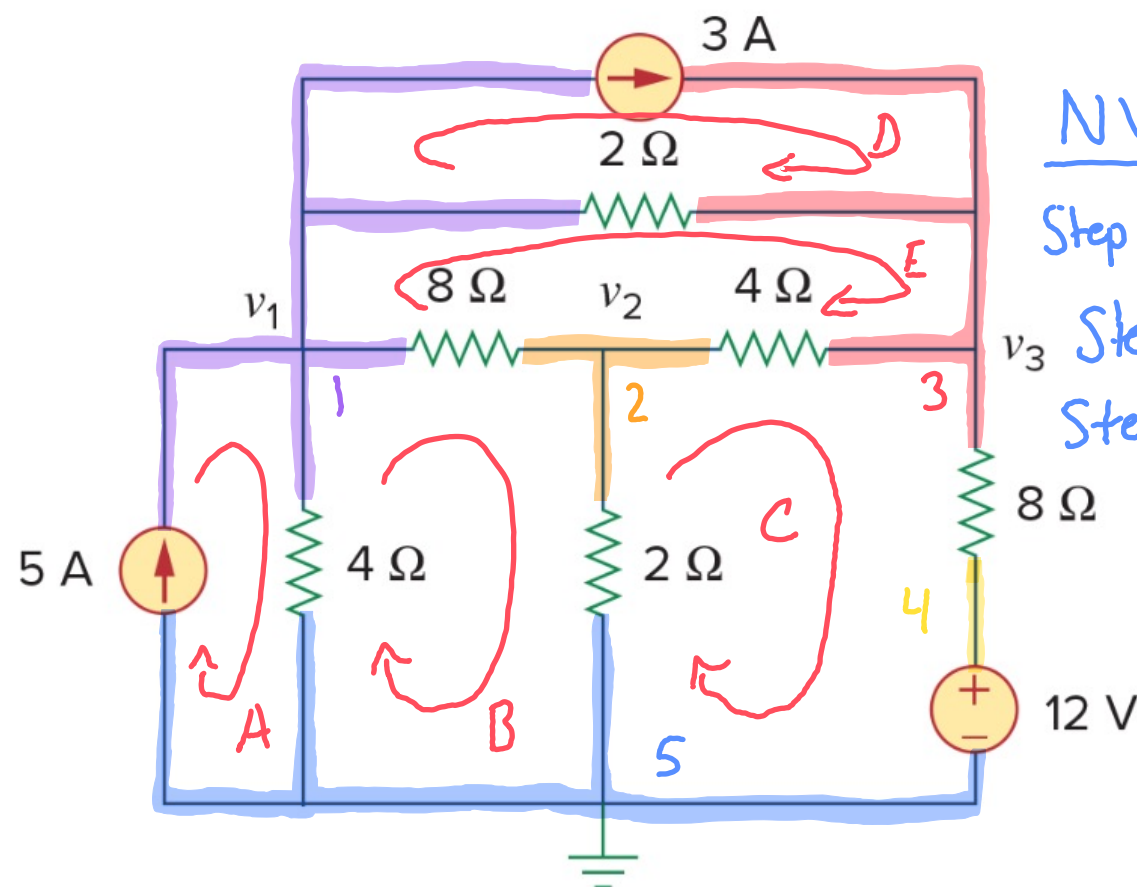




Will you use node-voltage analysis or mesh current analysis to solve this problem. Hint: Think about your system of equations.



NVA

Step 1: How many nodes 5

Step 2: Assign reference node

Step 3: known voltages 2 nodes

3 eqns

$$V_5 = 0V \quad V_4 = 12V$$

MCA

Step 1: How many meshes 5

Step 2: known currents 2 meshes

$$i_A = 5A \quad i_D = 3A \quad 3 \text{ eqns}$$

Doesn't matter,
same num of equations





THE OHIO STATE UNIVERSITY

COLLEGE OF ENGINEERING

The Principle of Superposition



- Learning Objectives:
 - Understand and apply the principle of superposition.





- Each independent source contributes independently to each voltage and current in the circuit.
- Each voltage and current in a circuit with N independent sources satisfies:



$$i = i_1 + i_2 + \dots$$

$$v = v_1 + v_2 + \dots$$


Superposition: break the circuit in two or more simpler circuits.

Turn off all independent sources except one.

Short circuit

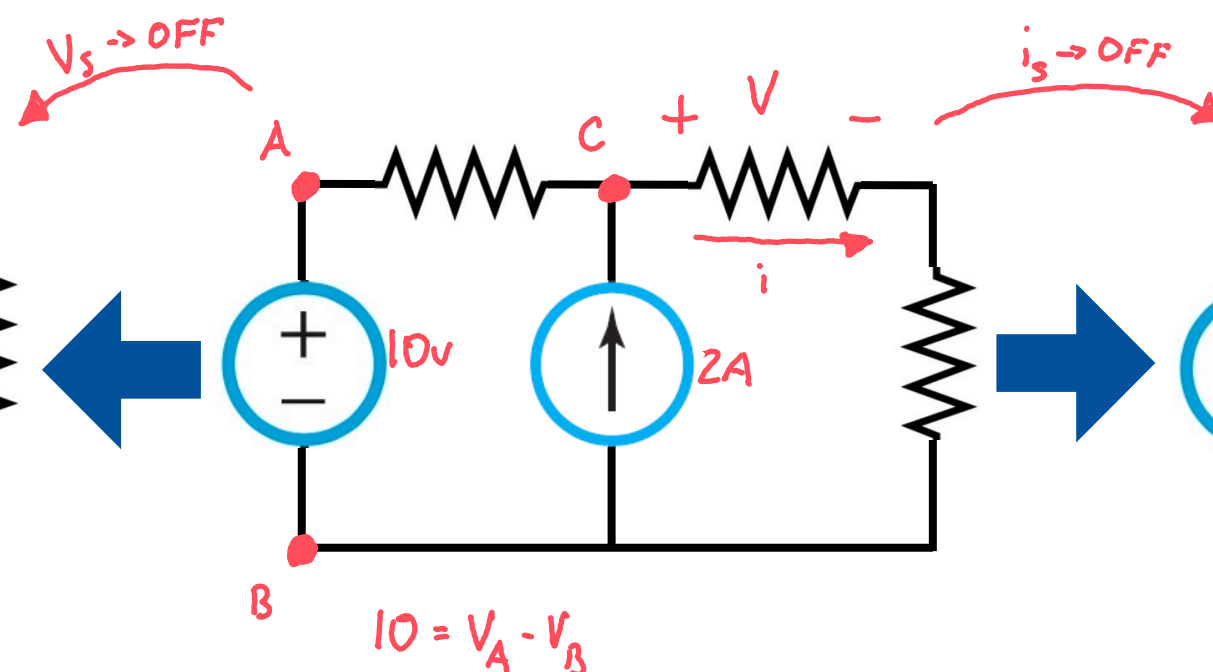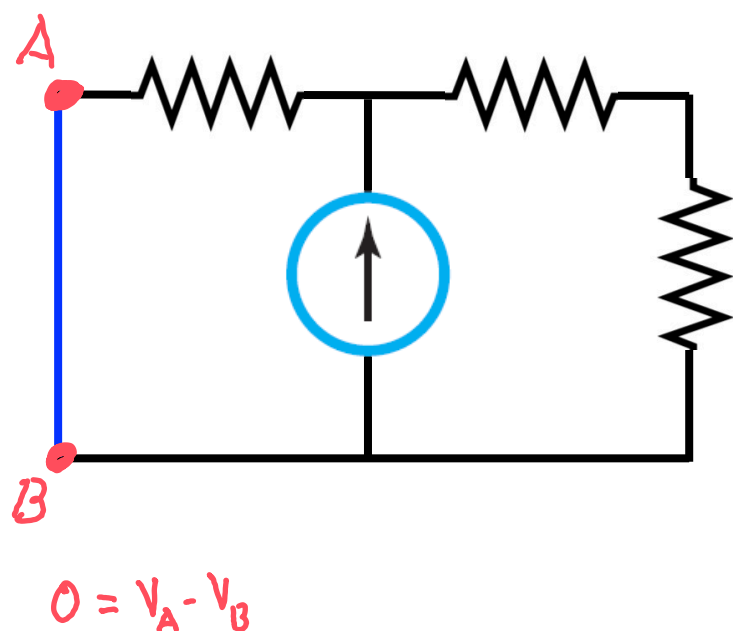


Open circuit



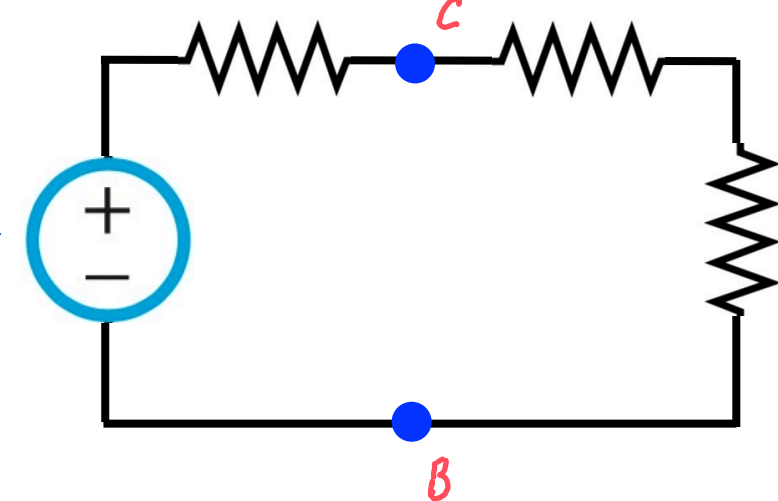




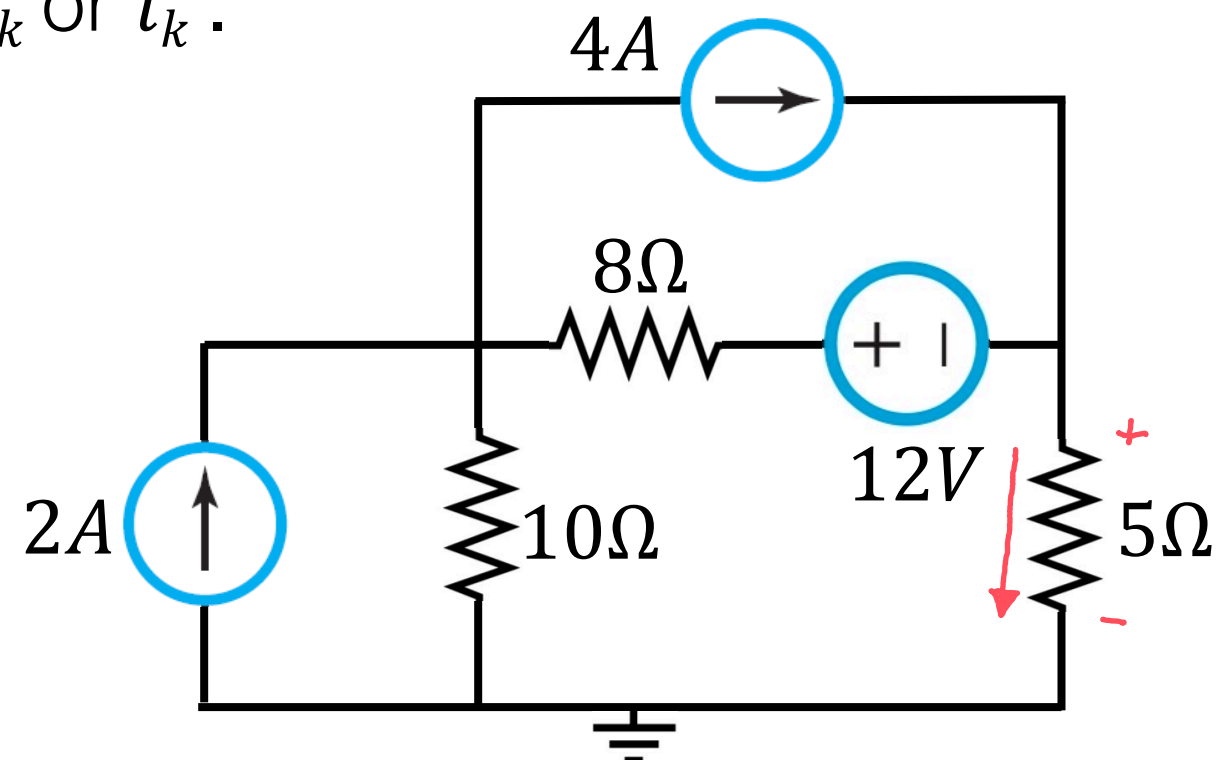1. Define voltage/current to be solved. V_5
2. For each of the N independent sources, define a component voltage v_k or current i_k .
$$V_5 = \frac{V_A}{2A} + \frac{V_B}{12V} + \frac{V_C}{4A}$$
3. Turn off all independent sources except one, source s_k .
4. Apply node voltage, mesh current, or any other circuit analysis technique to solve for v_k or i_k .
5. Repeat steps 3-4 for each independent source.



Find V_A :

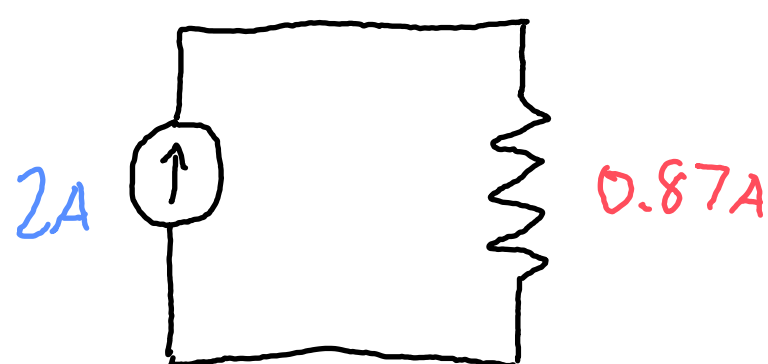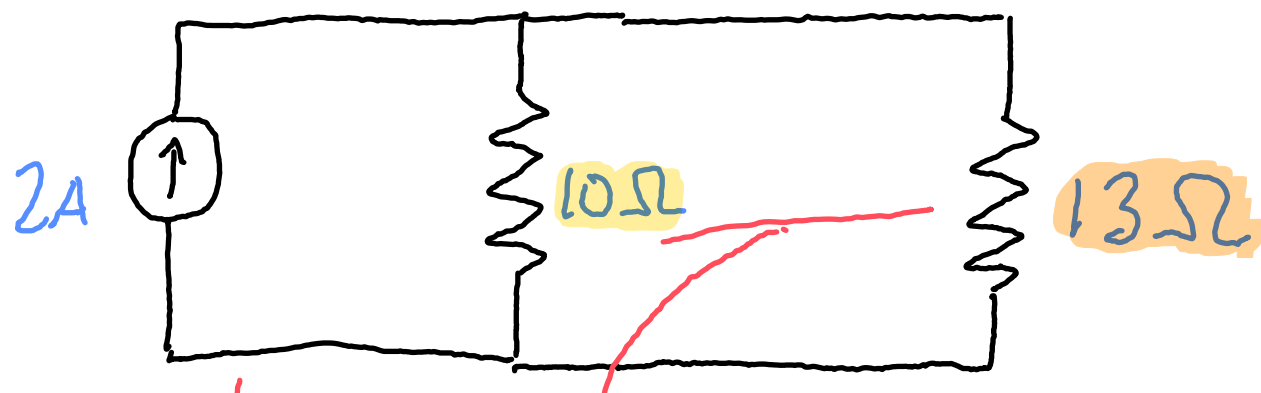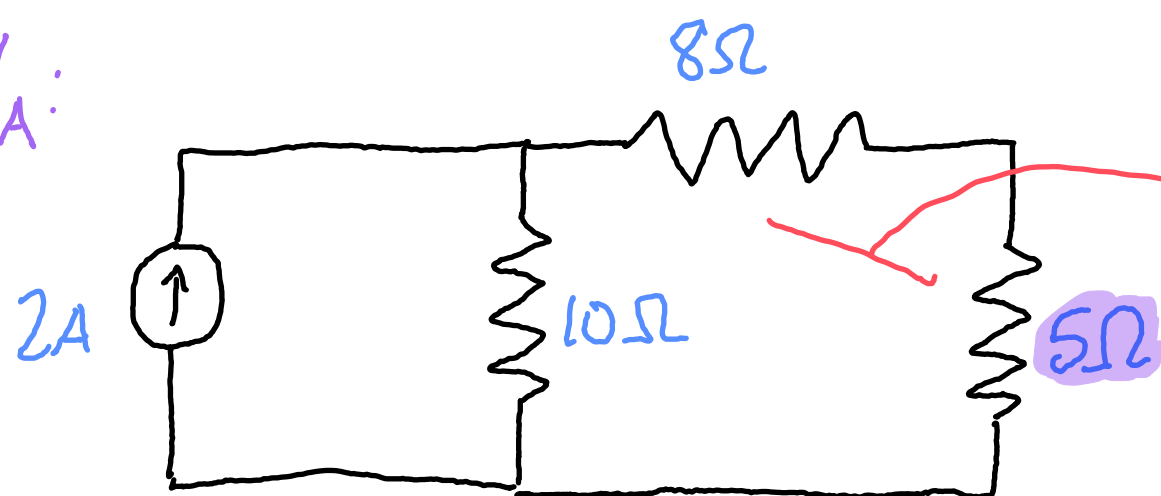



apply current division

$$\frac{10(13)}{10+13} = \frac{130}{23}$$

$$\frac{130}{23} \cdot 2 = \frac{260}{23} \text{ A}$$

$$V_A = 5i_5 = 5 \cdot \frac{20}{23} = \frac{100}{23} \text{ V}$$



Find V_B :

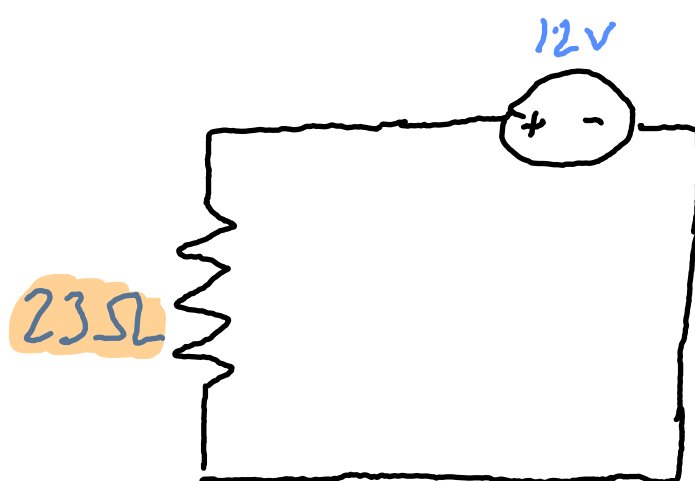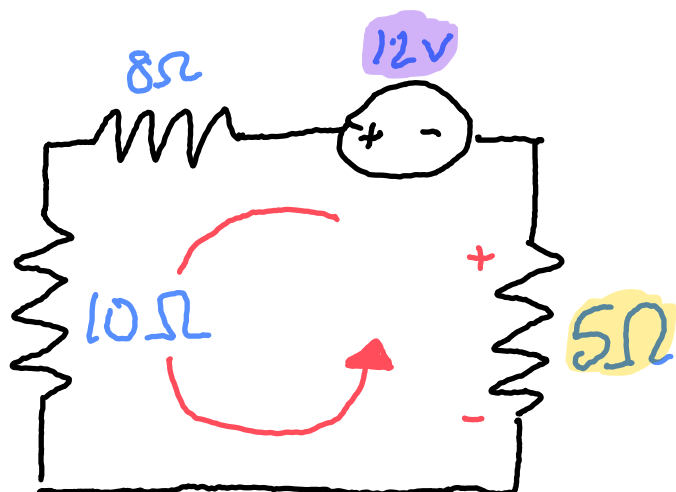

Voltage division

$$V_B = -\frac{5}{23} \cdot 12 = -\frac{60}{23} \text{ V}$$

Find V_C :

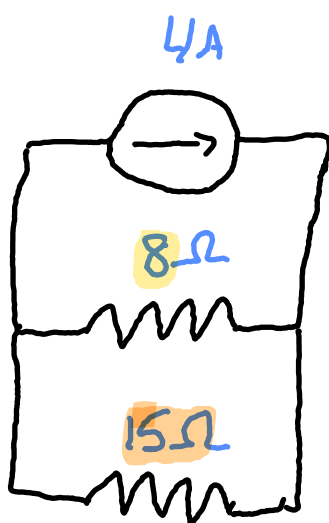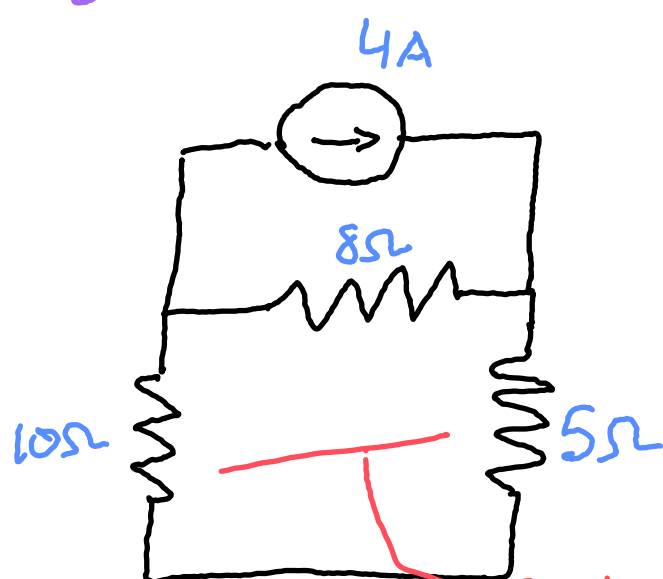

Current division

$$\frac{8(15)}{8+15} = \frac{120}{23}$$

$$\frac{120}{23} \cdot 4 = \frac{480}{23}$$

$$V_C = 5i_5$$

$$V_C = 5 \frac{32}{23} = \frac{160}{23} \text{ V}$$



In the circuit below, determine the i across the 20Ω resistor.

