

# Section 1: Basics.

Wednesday, January 10, 2024


4:06 PM

Last day to submit HWO for grade  
; 2/16/2024 @ 4:10 pm

---
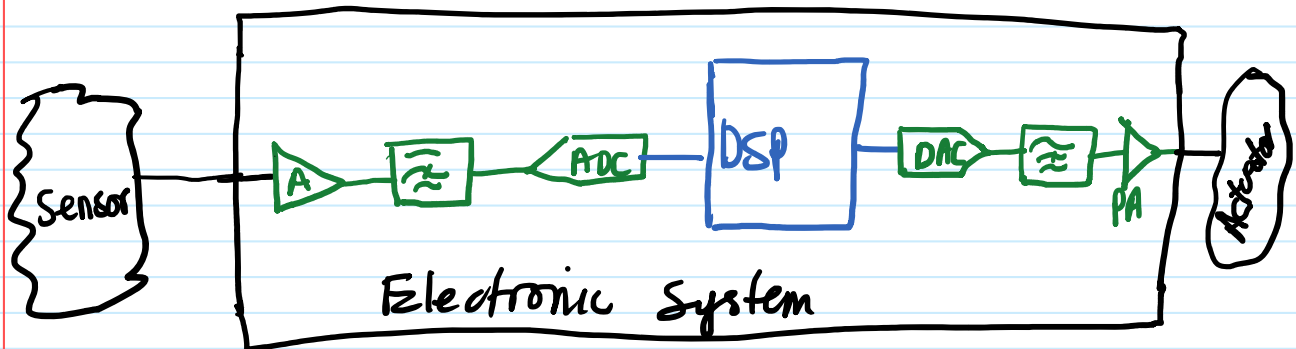
## Electronic System.

- Interface with real world (sense)
- Process sensor data to extract information
- Send information back into real world



antenna  
Microphone  
Keyboard

Camera  
Joy stick  
touch screen  
satellite  
thermometer

— . . . . . model



antenna  
Speaker  
display

sump pump  
haptics  
motor  
TNT charge

— . . . . . model

## thermometer

### Sensor Model

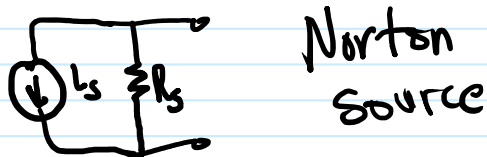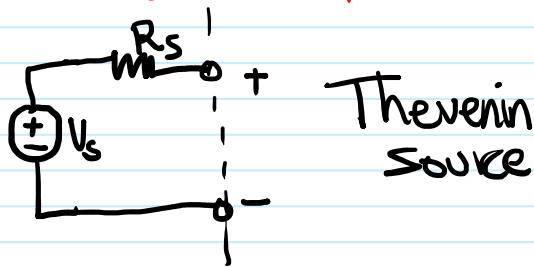


## 171 v17-7-

### Actuator Model



### Exercise #1

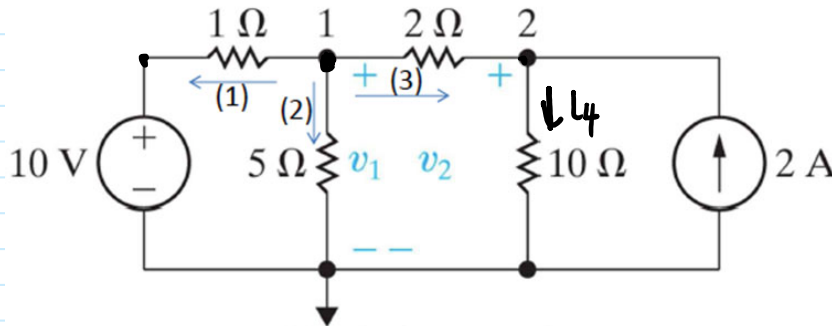

KCL @ node 1

$$\begin{aligned}
 -I_1 - I_2 - I_3 &= 0 \\
 -\frac{(V_1 - 10)}{1} - \frac{(V_1 - 0)}{5} - \frac{(V_1 - V_2)}{2} &= 0 \\
 10 - V_1 - \frac{V_1}{5} - \frac{V_1}{2} + \frac{V_2}{2} &= 0 \\
 100 - 10V_1 - 2V_1 - 5V_1 + 5V_2 &= 0 \\
 100 - 17V_1 + 5V_2 &= 0 \quad \text{--- (2)}
 \end{aligned}$$

KCL @ node 2



$$\begin{aligned}
 I_3 - I_4 + 2 &= 0 \\
 \frac{V_1 - V_2}{2} - \frac{(V_2 - 0)}{10} + 2 &= 0 \\
 5(V_1 - V_2) - V_2 + 20 &= 0 \\
 5V_1 - 6V_2 + 20 &= 0 \quad \text{--- (1)}
 \end{aligned}$$

$$V_1 = 9.09V, V_2 = 10.91V$$

### Superposition

## Superposition

Current is zero

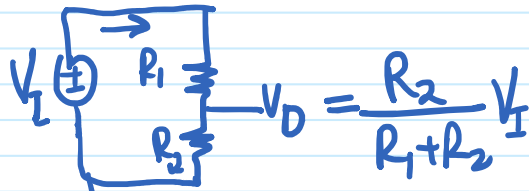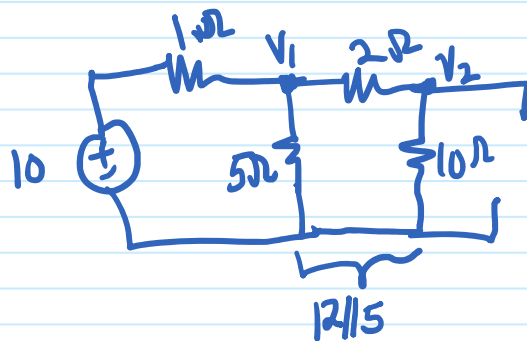

$$V_1 = \frac{12//5}{12//5 + 1} \times 10 = \frac{3.53}{4.53} = 7.77$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} \rightarrow R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

$$V_2 = \frac{10}{12} \times 7.77 = 6.49 \text{ V.}$$

