
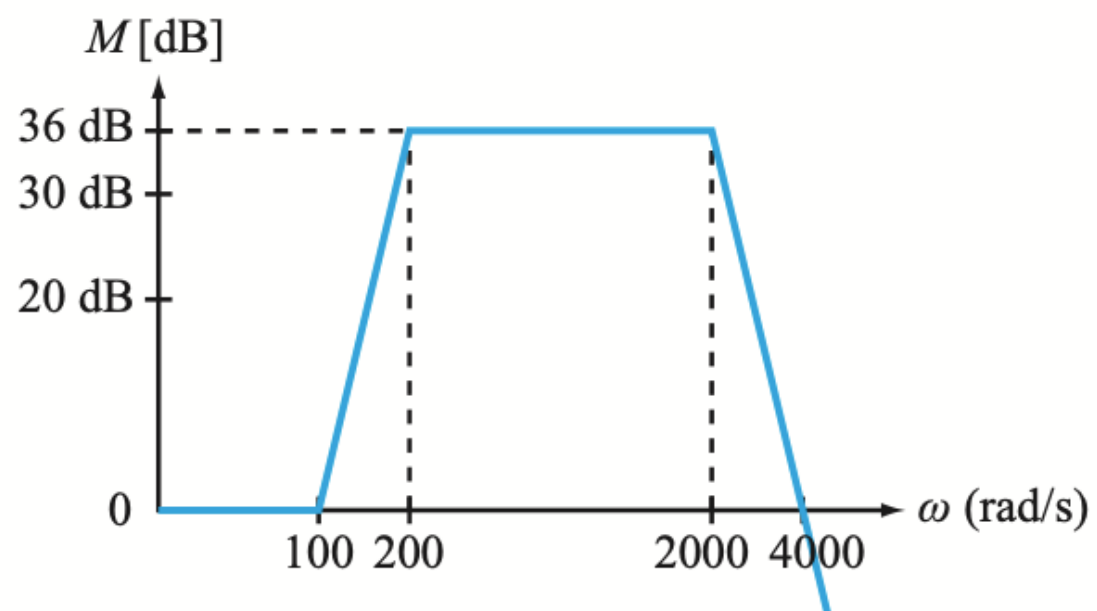


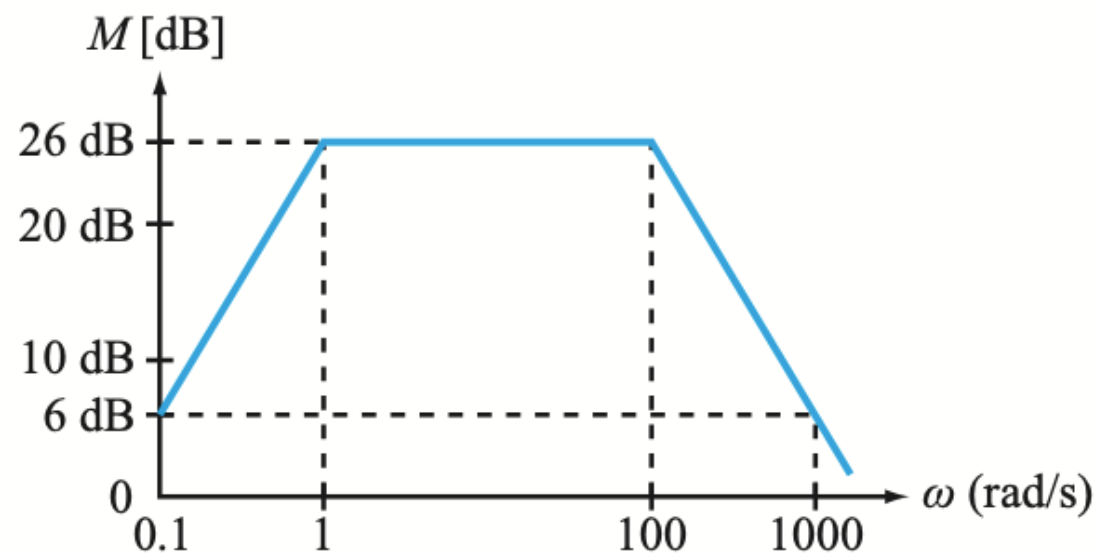

What is the gain K for the bode plots below





THE OHIO STATE UNIVERSITY

COLLEGE OF ENGINEERING

Intro to Operational Amplifiers




- Learning Objectives:
 - Describe the basic properties of an op amp and state the constraints of the ideal op-amp model.







- Amplifier:

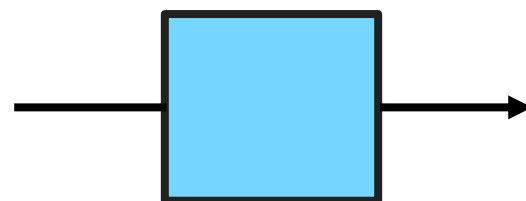

- Operational amplifier:

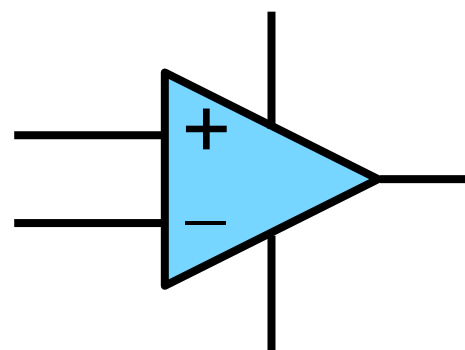


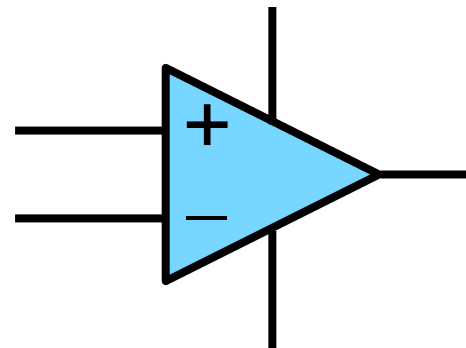- It acquired the adjective operational because it is a versatile device capable not only of amplifying a signal but also inverting it (reversing its polarity), integrating it, or differentiating it.




Properties:

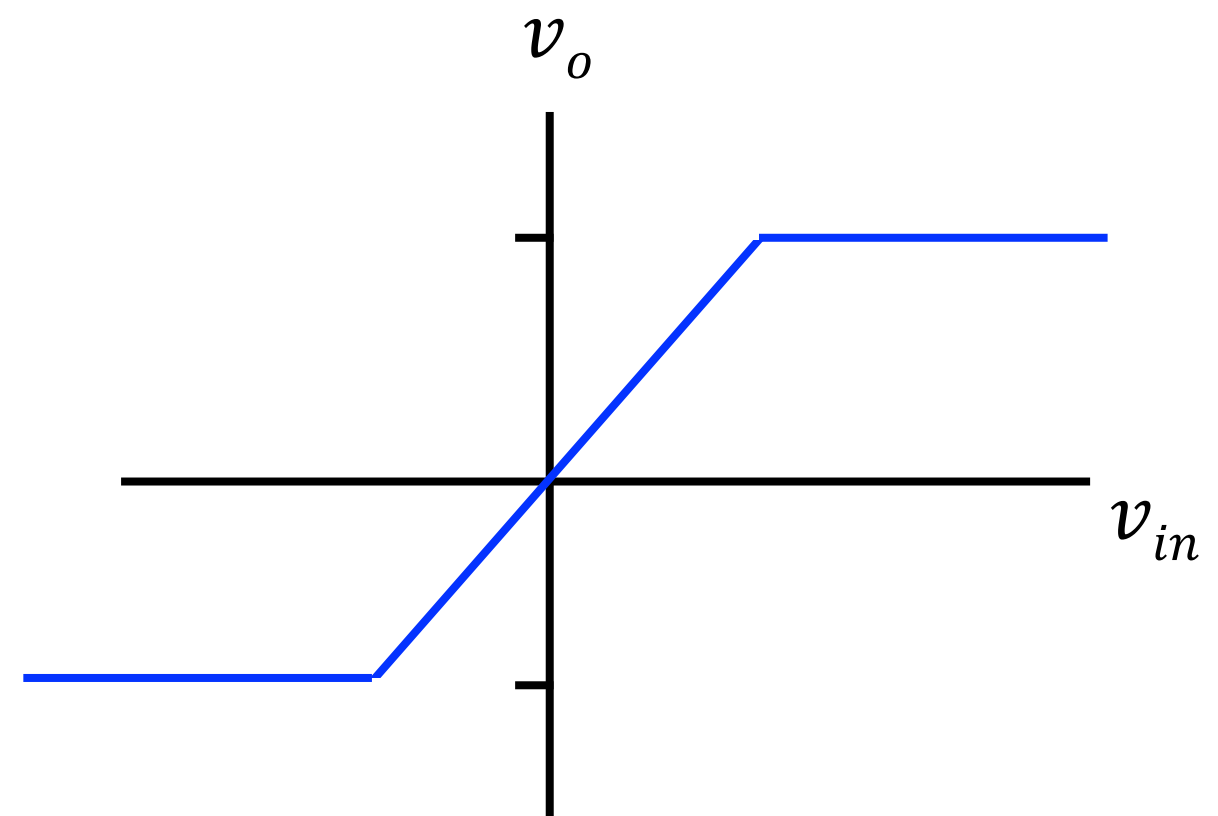- High Gain: $A = 10^5 - 10^6$
- Differential input: $v_{in} = v_p - v_n$
- Linear operating range:
- Saturated by $+v_{cc}$ and $-v_{ee}$
- Usually $v_{ee} = -v_{cc}$






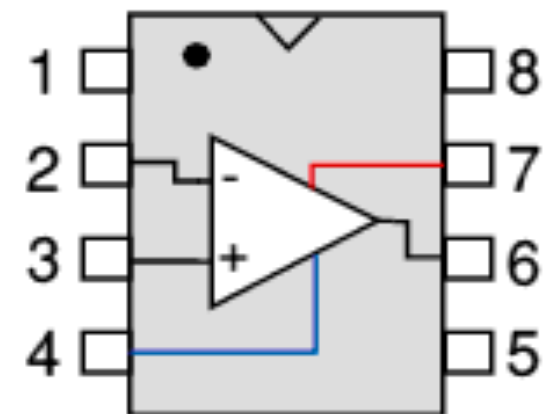
- Amplifier functions:
 - Signal Amplification.
 - Filtering.
 - Add, Subtract, Integrate, Differentiate.
- Example amplifier applications:
 - Digital audio player.
 - Measurement sensors.
 - Feedback.





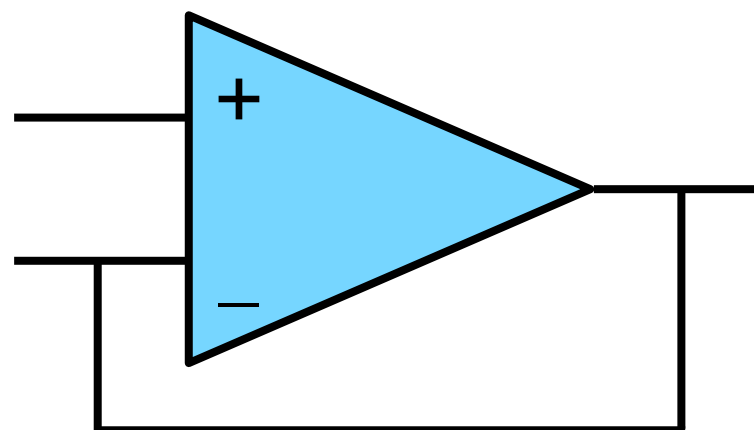- Process of using the output to reinforce (positive feedback) or inhibit (negative feedback) its input.
 - Open-loop mode if feedback is not used.
 - Closed-loop if feedback is used.
- Key benefits:
 - Decreased sensitivity to signal variations.
 - Increased bandwidth and linearity.
 - Increased signal-to-noise ratio.




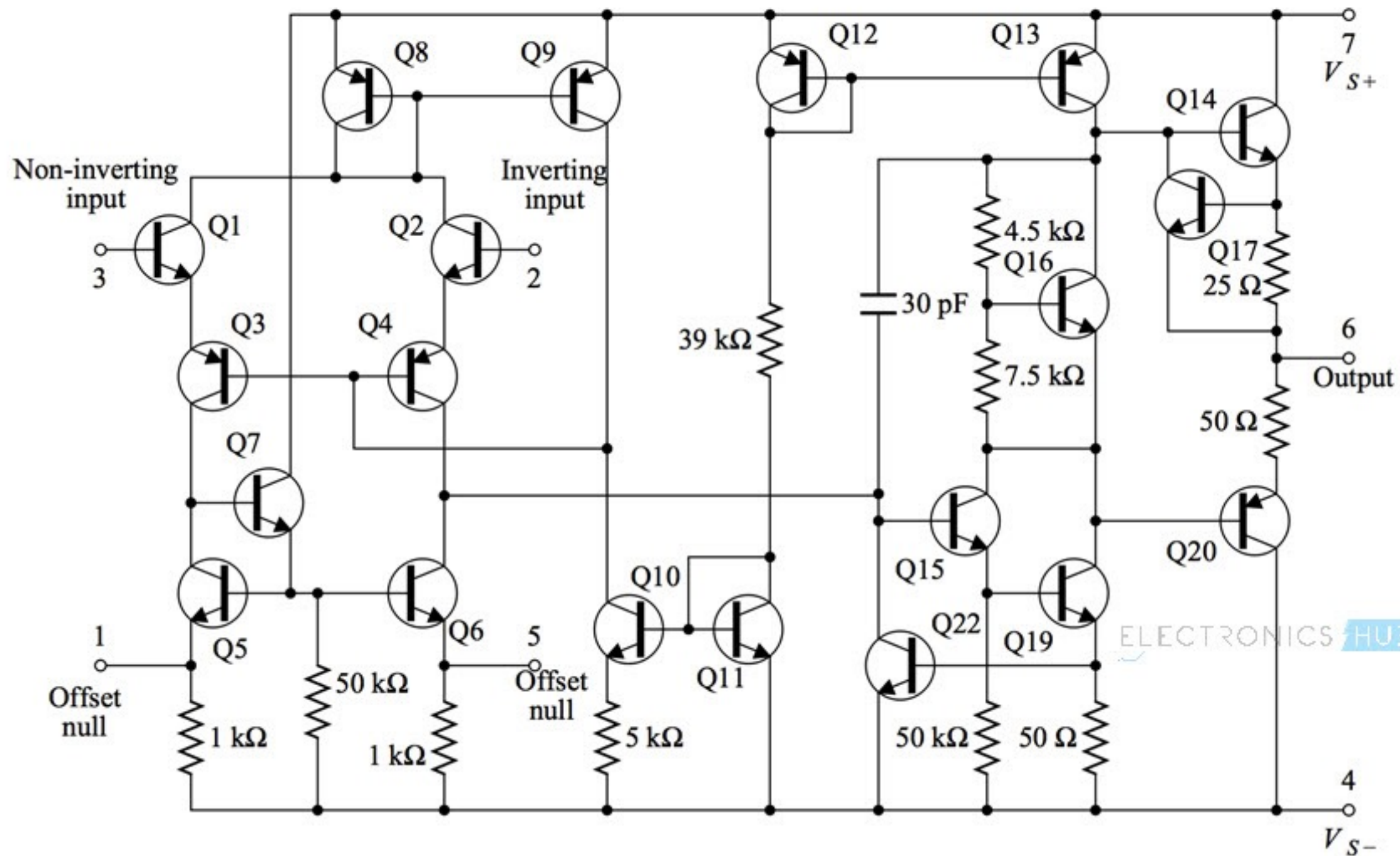



Internal Circuitry of 741 Op-Amp IC



Amplifier Behavioral Model

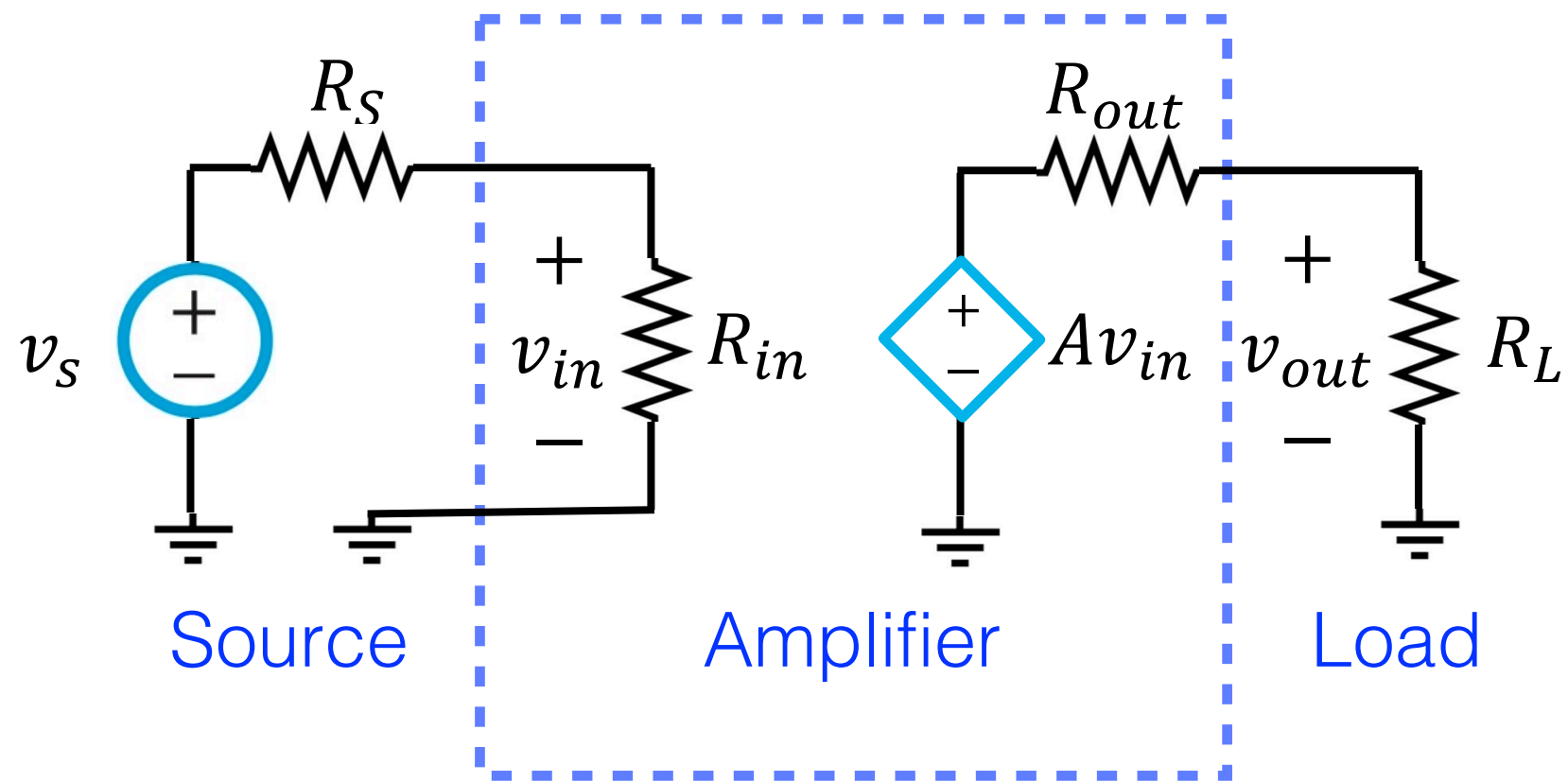

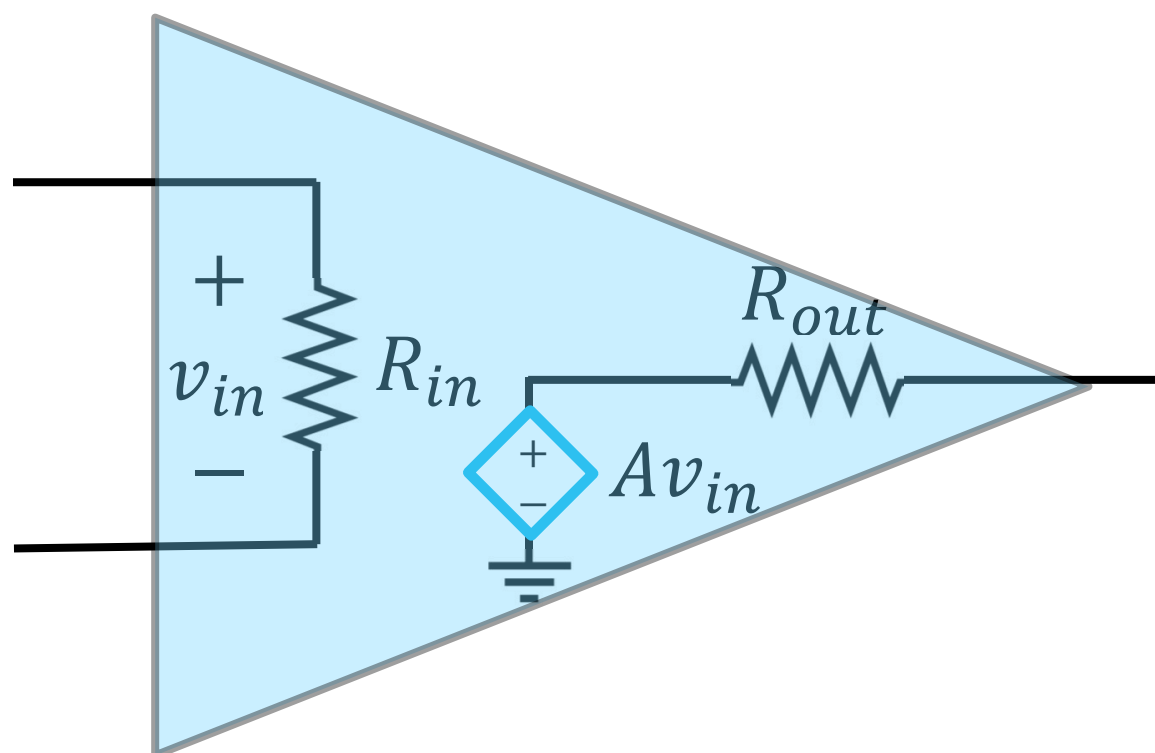

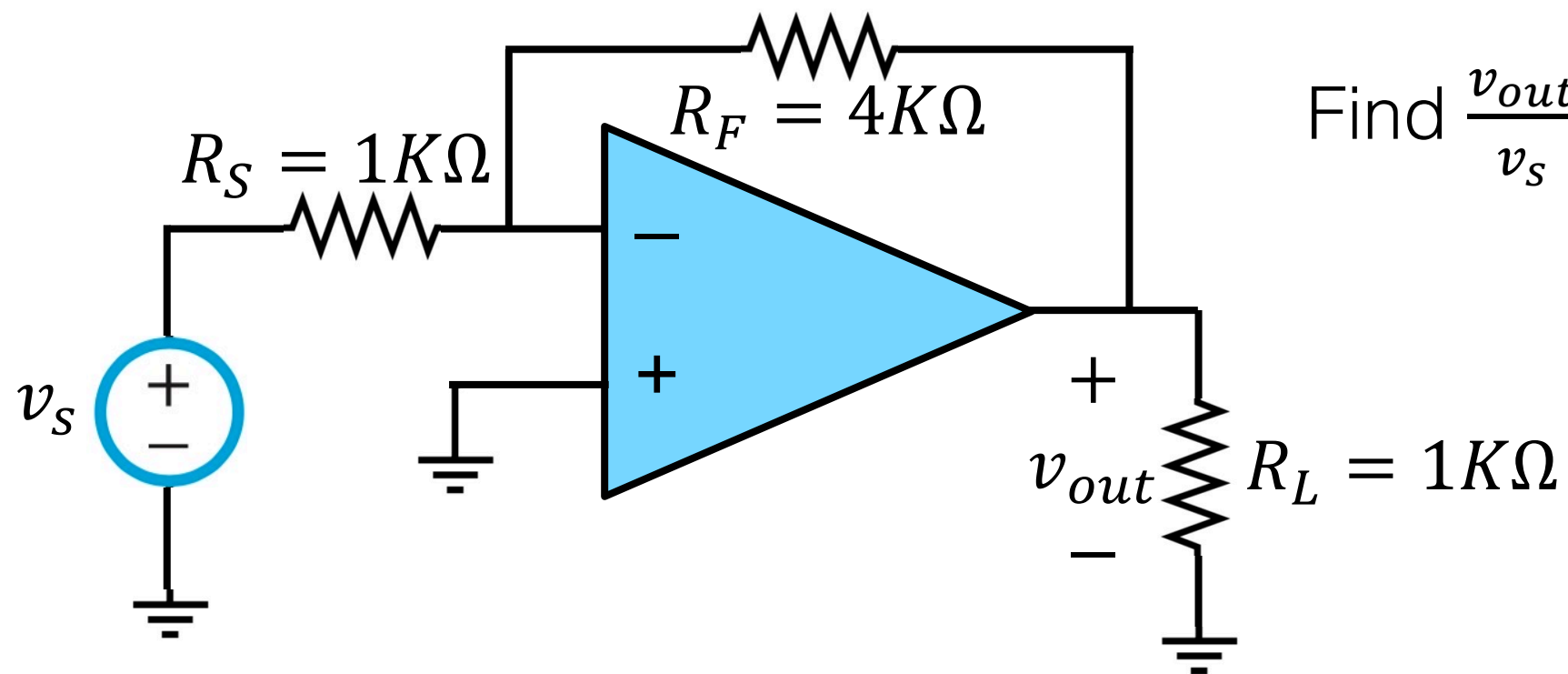

Find $\frac{v_{out}}{v_S}$ given that:

$$R_{in} = 10^6 \Omega$$

$$R_{out} = 100 \Omega$$

$$A_{vol} = 10^6$$