 


In this problem inverters have a propagation delay of 2 ns, 2-input gates have a propagation delay of 2 ns, and 3-input gates have a propagation delay of 6 ns.


The vertical lines in the timing diagrams indicate 2 ns increments in time.

- a) Determine the SOP expression for $G(A, B, C)$ in the circuit above. Complete a K-map and use it in your analysis of this circuit for potential static-1 hazards. Explain the details of your findings.
- b) Complete the following timing diagram for this circuit with $A = B = 1$. If any potential static-1 hazards found in part a) have produced any glitches in the output then circle the glitches in your timing diagram. If there were no glitches, explicitly say so here.


$$AC + BC'$$



No glitches

 

 - c) Add another NAND gate to the circuit to address the potential static-1 hazard. Draw the new circuit, and label the output of the new NAND gate "H".
- d) Complete the timing diagram for your new circuit with $A = B = 1$. Circle any glitches in the output. If there were no glitches, explicitly say so here.



No glitches

