



Finish super-mesh example.





THE OHIO STATE UNIVERSITY

COLLEGE OF ENGINEERING

Node Voltage and Mesh Current Analysis Examples



- Learning Objectives:
 - Apply the node-voltage and mesh current analysis technique to linear electric circuits.






Apply nodal analysis to find node voltages in the circuit below and then determine I_x .

Step 1 \rightarrow 5 nodes


Step 2 \rightarrow Choose ground

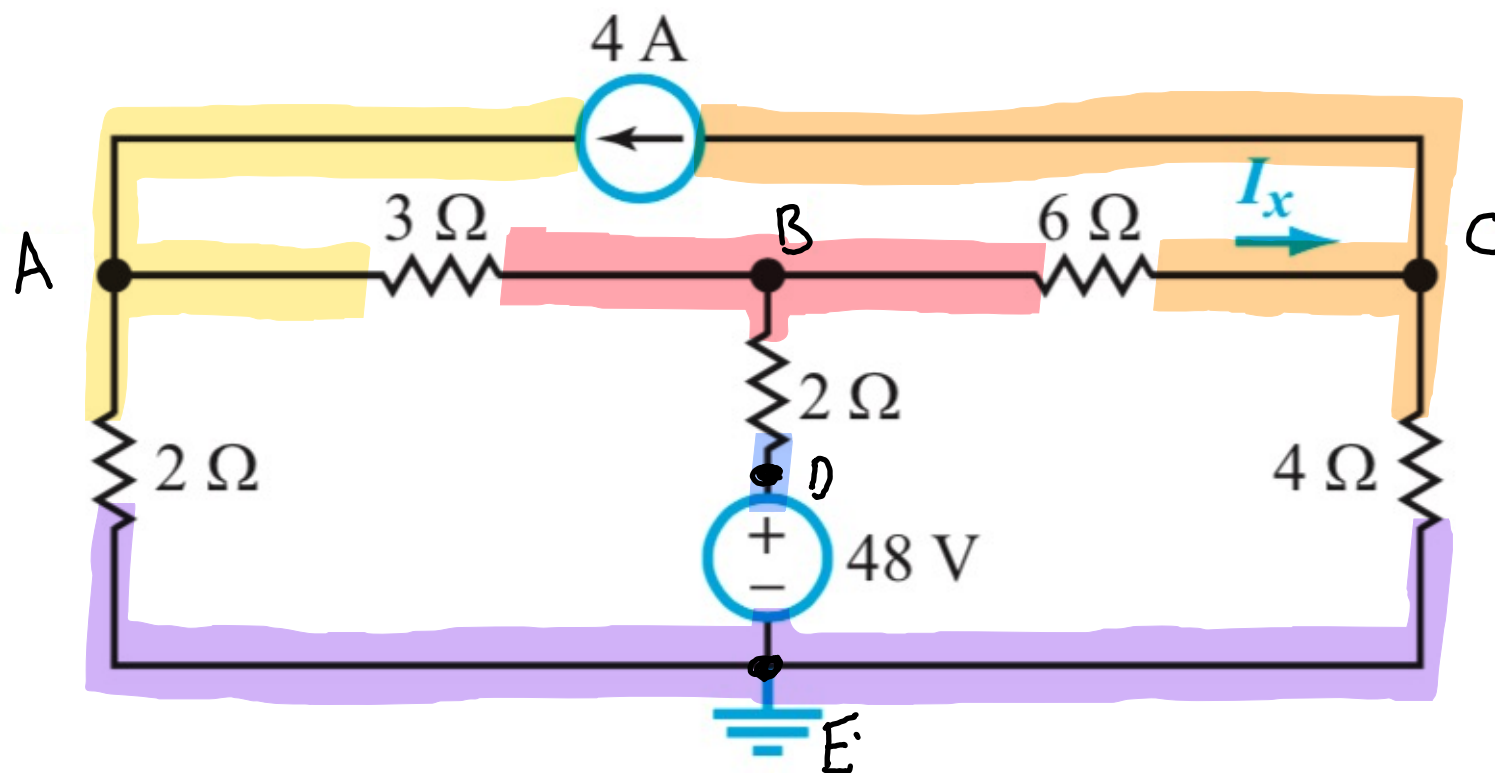






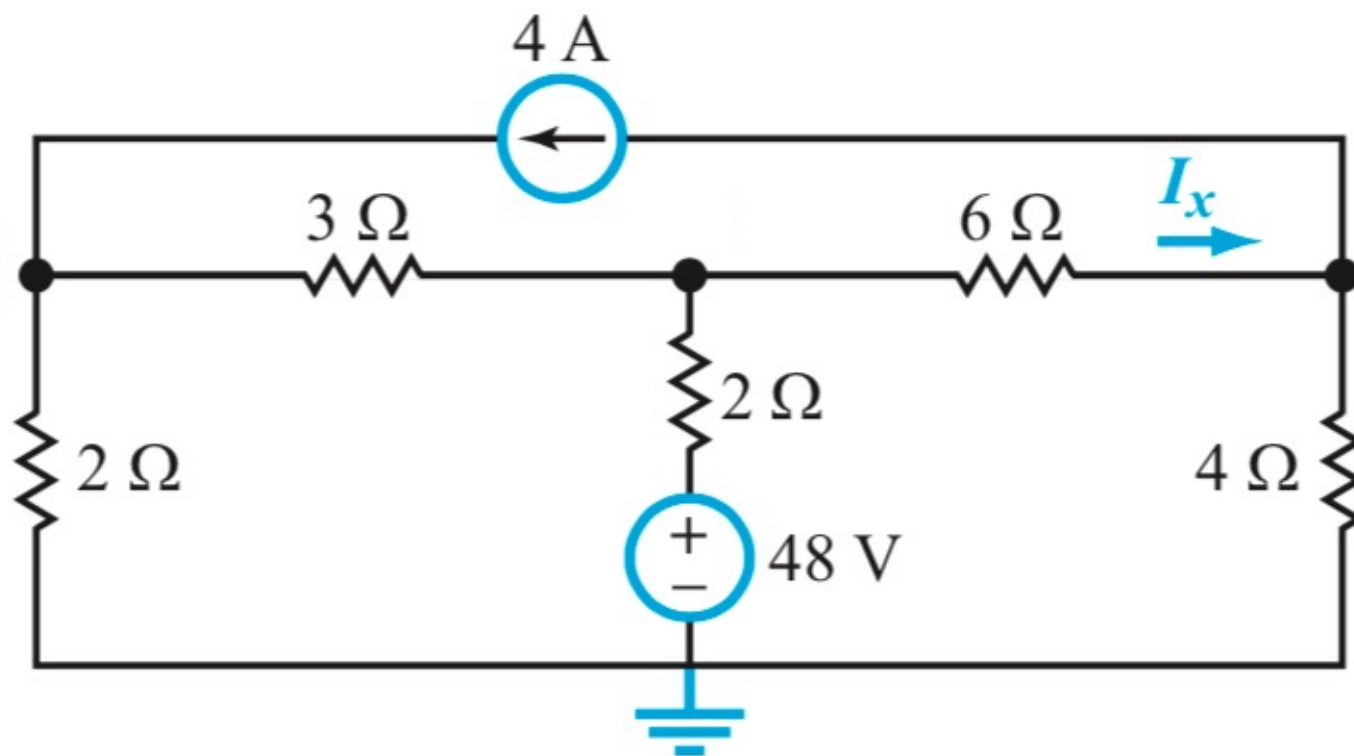Apply nodal analysis to find node voltages in the circuit below and then determine I_x .





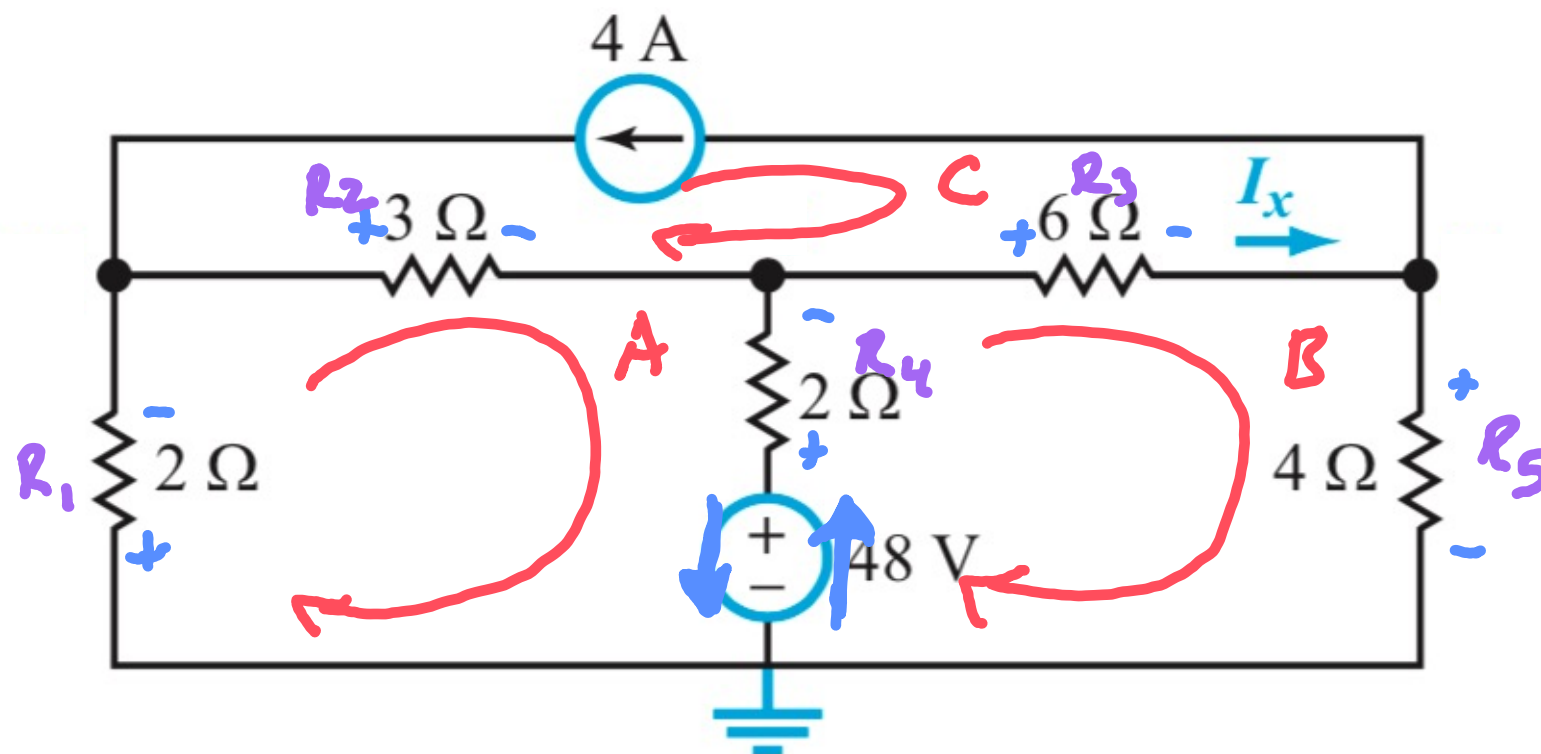Apply mesh analysis to find mesh currents in the circuit below and then determine I_x .



Step 1 → 3 meshes

Step 2 → 1 mesh

2 meshes

2 eqns

2 unknowns

KCL @ C:

$$4 = i_3 + i_2$$

Auxiliar Eqn:

$$48 = V_A - V_B$$

KCL @ Super-Mesh:

$$i_1 + i_2 + i_3 + i_5 = 0$$

Ohm's Law

$$V_1 = V_A \quad V_3 = V_B - V_C$$

$$V_2 = V_A - V_C \quad V_4 = V_A - V_B$$

$$V_5 = V_B$$

$$\frac{V_1}{2} + \frac{V_2}{3} + \frac{V_3}{6} + \frac{V_5}{4} = 0$$

KVL @ C:

$$4 = V_B - V_C + V_A - V_C$$

$$4 = V_A + V_B - 2V_C$$

$$i_x = i_3$$

??? I'm lost

KVL @ Super Mesh:

$$\frac{V_A}{2} + \frac{V_A - V_C}{3} + \frac{V_B - V_C}{6} + \frac{V_B}{4} = 0$$

$$\frac{5}{6}V_A - \frac{1}{2}V_C + \frac{5}{12}V_B = 0$$





Apply mesh analysis to find mesh currents in the circuit below and then determine I_x .

