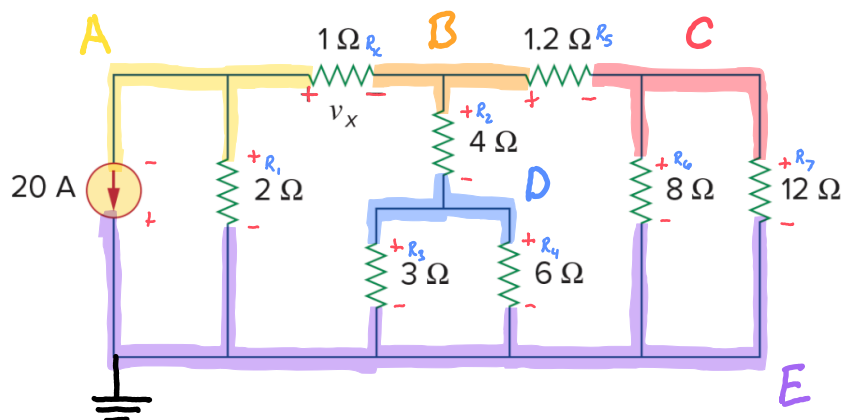


## Homework 2

Due: Friday, February 3rd, 2023 by 7PM.

**Note:** In order to receive full credit, you must show your work and carefully justify your answers. The correct answer without any work will receive little or no credit.

- Using equivalent resistance, current division, voltage division, and Ohm's Law only, find the voltage  $v_x$  in the circuit below.




$$i_A = 20A$$


$$V_E = 0V$$

$$V_B = V_A - V_C - V_D$$

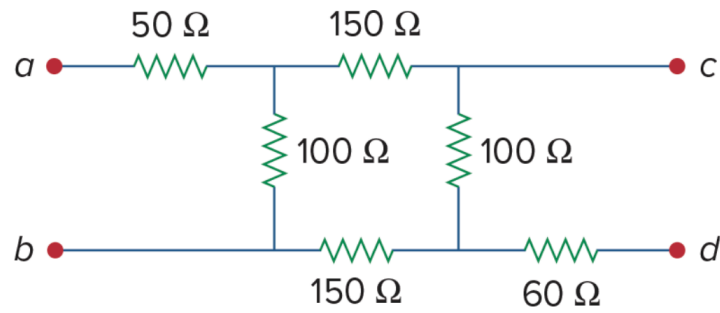2. For the circuit below:
- A. Find  $R_{eq}$  from node a and b.
  - B. Find  $R_{eq}$  from node b and c.



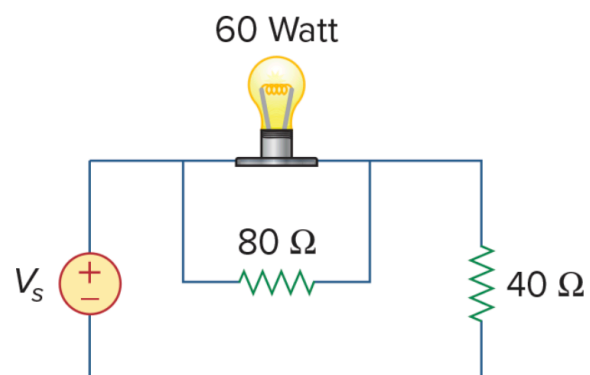3. The 60 W light bulb is rated at 120 V. Calculate the value of  $V_s$  to make the light bulb operate at its rated conditions.



4. Using node voltage analysis to find voltage  $V$  across the  $35\Omega$  resistor.

