



Lecture Outline

Reminders to self:

- ☐ Turn on lecture recording to Cloud
- ☐ Turn on Zoom microphone

- Last Lecture

- Continued Three-state buffers / Tri-state outputs
- Decoders and Encoders
- Started ROM

- Today's Lecture

- Continue ROM
- Programmable Logic Arrays
- Start Latches & Flip-Flops (primarily latches today)



Handouts and Announcements

- Announcements
 - Homework Problem 9-3
 - Posted on Carmen today
 - Due: 11:59pm Thursday 2/23
 - Homework Reminder:
 - HW 9-1 due: 11:25am Wednesday 2/22
 - HW 9-2 due: 11:59pm Thursday 2/23
 - Read for Wednesday: pages 342-352



Handouts and Announcements

- Announcements

- Mini-Exam 3 Reminder

- Available 5pm Monday 2/20 through 5:00pm Tuesday 2/21
- Due in Carmen PROMPTLY at 5:00pm on 2/21
- Designed to be completed in ~36 min, but you may use more
- When planning your schedule:
 - I recommend building in 10-15 min extra
 - To allow for downloading exam, signing and dating honor pledge, saving solution as pdf, and uploading to Carmen
- I also recommend not procrastinating

- Exam review topics available on Carmen



- Sample Mini-Exams 3 and 4 from Au20 also available



Read-Only Memory

 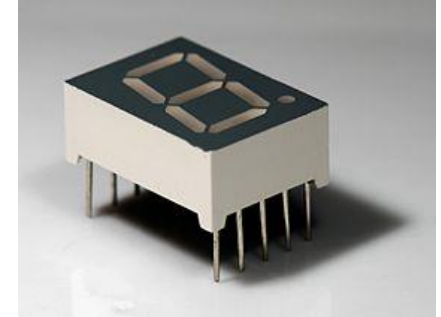Example: ROM for seven-segment display driver



- Seven-segment display: an electronic display device for displaying decimal numerals
- Alternative to the more complex dot matrix displays
- Used in things such as digital clocks, electronic meters, basic calculators, etc.
 - Light up B and C → Displays a 1
 - Light up B, C, F and G → Displays a 4
 - Etc.
- Goal: ROM LUT for BCD to seven-segment driver








Read-Only Memory

<i>W</i>	<i>X</i>	<i>Y</i>	<i>Z</i>	<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>E</i>	<i>F</i>	<i>G</i>
0	0	0	0	/	/	/	/	/	/	0
0	0	0	1	0	/	/	0	0	0	0
0	0	1	0	/	/	0	/	/	0	/
0	0	1	1	/	/	/	/	0	0	/
0	1	0	0	0	/	/	0	0	/	/
0	1	0	1	/	0	/	/	0	/	/
0	1	1	0	/	0	/	/	/	/	/
0	1	1	1	/	/	/	0	0	0	0
1	0	0	0	/	/	/	/	/	/	/
1	0	0	1	/	/	/	/	0	/	/

  



Read-Only Memory

  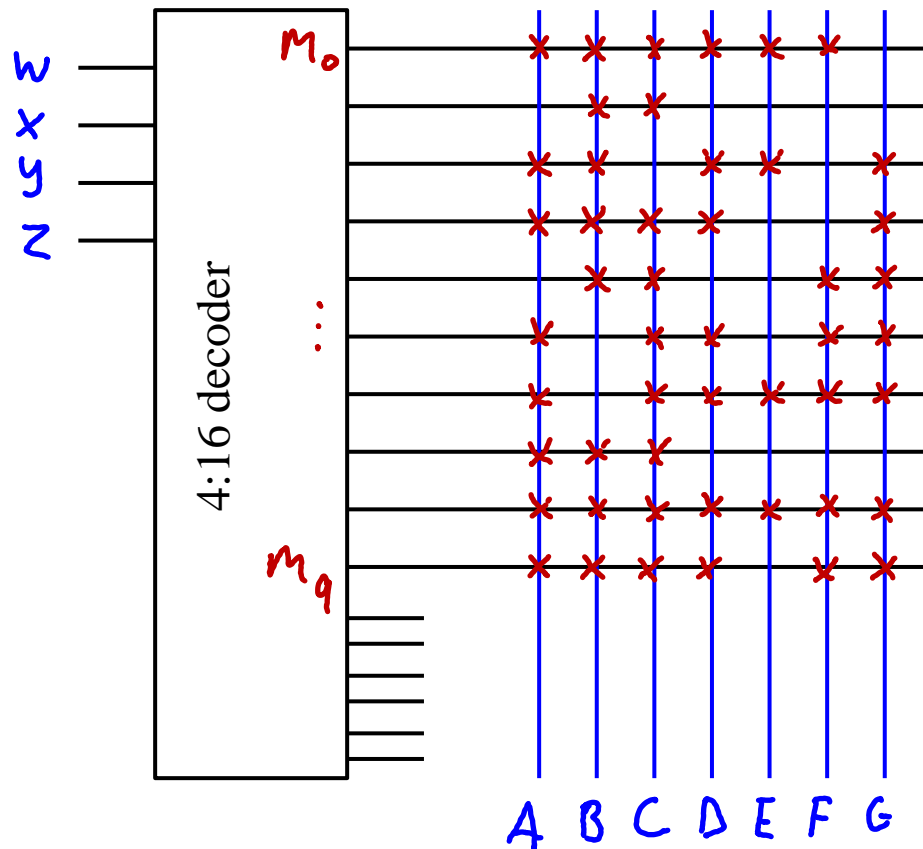



Types of ROM (Non-volatile memory)

- **Standard ROM**

- Permanent
- Switches between word and output lines hardwired in
- Either the switch is there, or it is not
- Done at “Mask-level” during fabrication of IC

- **Programmable ROM (PROM)**

- Can electronically set the locations of the “on” switches
- **Once**

- **Electronically Erasable PROM (EEPROM)**

- Can electronically reprogram
- On order of 100 to 1000 times
- Uses a special type of FET for the switches
- Takes large voltages to erase/reprogram
- Limited number of times before FET fails




Programmable Logic Arrays

- A Programmable Logic Array (PLA) performs the same basic function as a ROM.
- A PLA with n inputs and m outputs can realize m functions of n variables
- But internal organization of PLA is different than that of ROM
 - ROM directly implements a truth table
 - PLA uses arrays of ANDs and ORs to implement an SOP expression
- # Input lines: n
- # Output lines: m
- Between AND array and OR array: k Word Lines

FIGURE 9-28
Programmable
Logic Array
Structure

© Cengage Learning 2014

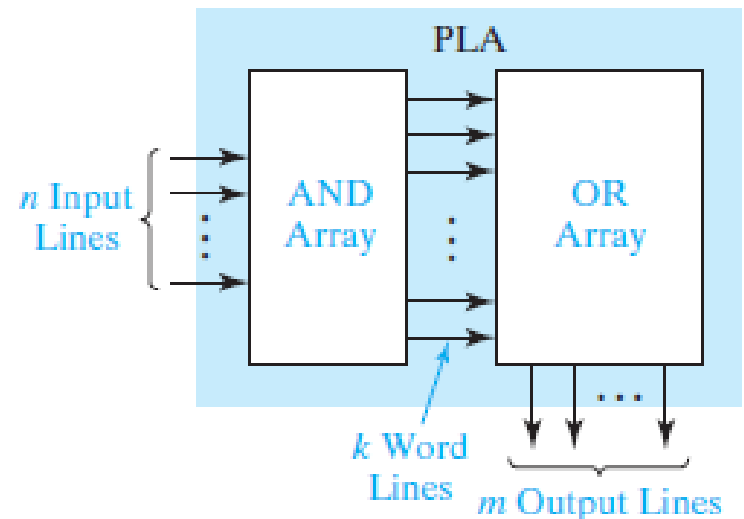



Programmable Logic Arrays

• PLA with AND and OR arrays programmed


- Switch connections in AND array on left
- OR array on right

Inputs and complements both available

Pull down resistors for OR array. Any 1 output from AND array can pull connected line to 1.

FIGURE 9-29

 PLA with Three Inputs, Five Product Terms, and Four Outputs





Programmable Logic Arrays

PLA Tables

- Symbols 0, 1, and – indicate whether a variable is
 - Complemented,
 - Not complemented, or
 - Not present in the corresponding product term
- Output side of table specifies which product terms appear in each output function
- A 1 or 0 indicates whether a given product term is present or not present in the corresponding output function

*AND array**OR array*

PLA table
for entire
example
array on
previous
slide

Product Term	Inputs A B C	Outputs F ₀ F ₁ F ₂ F ₃	
A'B'	0 0 –	1 0 1 0	F ₀ = A'B' + AC'
AC'	1 – 0	1 1 0 0	F ₁ = AC' + B
B	– 1 –	0 1 0 1	F ₂ = A'B' + BC'
BC'	– 1 0	0 0 1 0	F ₃ = B + AC
AC	1 – 1	0 0 0 1	




Programmable Logic Arrays

FIGURE 9-30
AND-OR Array
Equivalent to
Figure 9-29

© Cengage Learning 2014

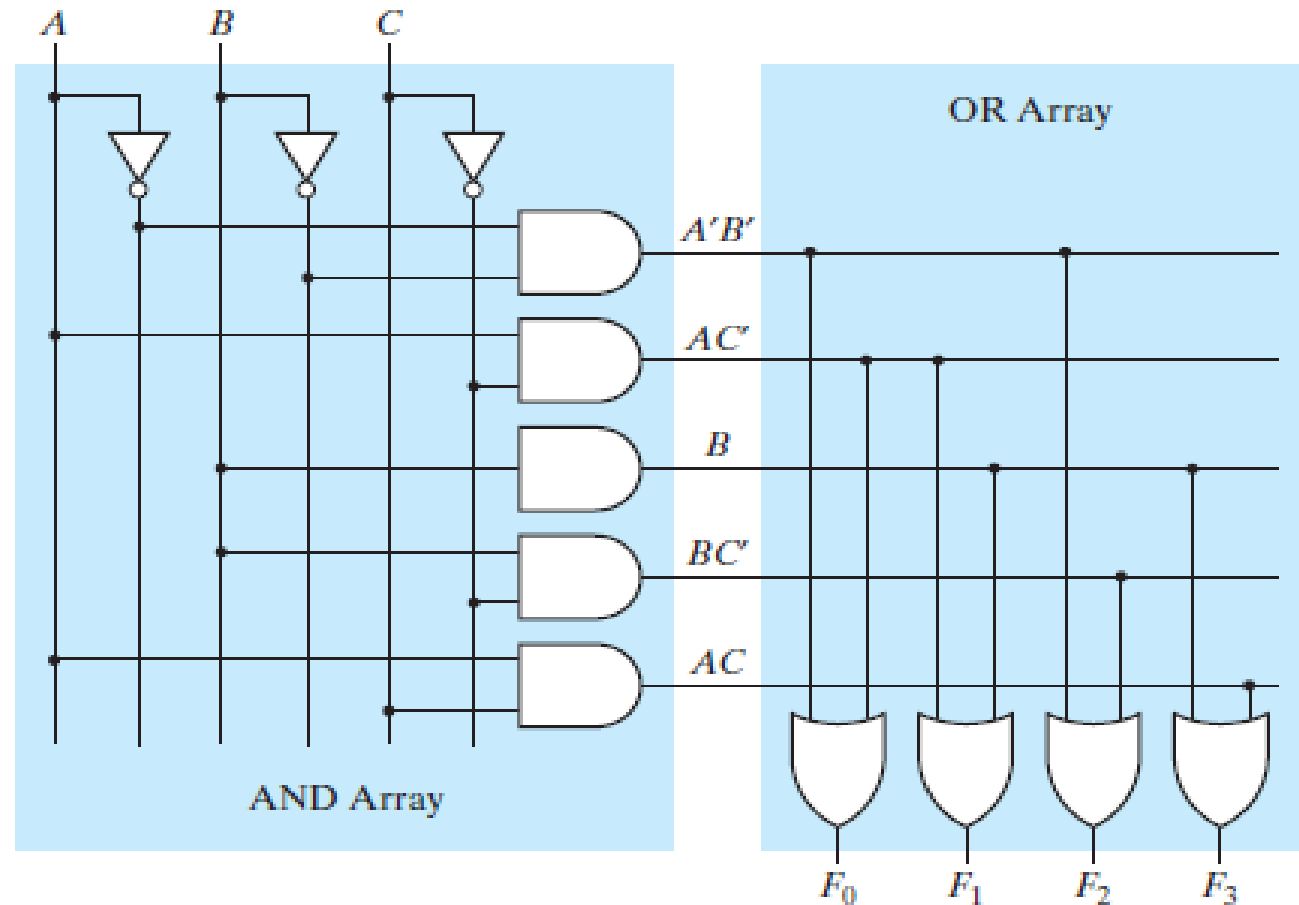AND-OR gate
array for entire
example array on
previous slides





Programmable Logic Arrays

- ROM


- Decoder iterate all minterms
- 24 inputs $\rightarrow 2^{24}$ word lines !!!

- PLA

- Reduce expression first
- Implement only those word lines that are needed



PLA Example

 

When homework or exam problem asks for “PLA Table” this is expected type of table

Product Terms	A	B	C	f_1	f_2
AB'	1	0	-	1	1
$A'C$	0	-	1	1	
$A'BC'$	0	1	0		1



Programmable Array Logic

- Programmable Array Logic (PAL) is a special case of PLAs
- Same AND-array and OR-array structure, but
 - Only the AND array is programmable
 - The OR array is fixed
- Less expensive than the more general PLA
- Easier to program
- Input buffers with both inverting and non-inverting outputs used
 - Need both inverting and non-inverting
 - And each typically must drive many AND gates
- Limited Fan-in
- Different types available, with different Fan-in limits





Programmable Array Logic

- Segment of an unprogrammed PAL
- This type has 2-input ORs

FIGURE 9-32
PAL Segment

© Cengage Learning 2014

 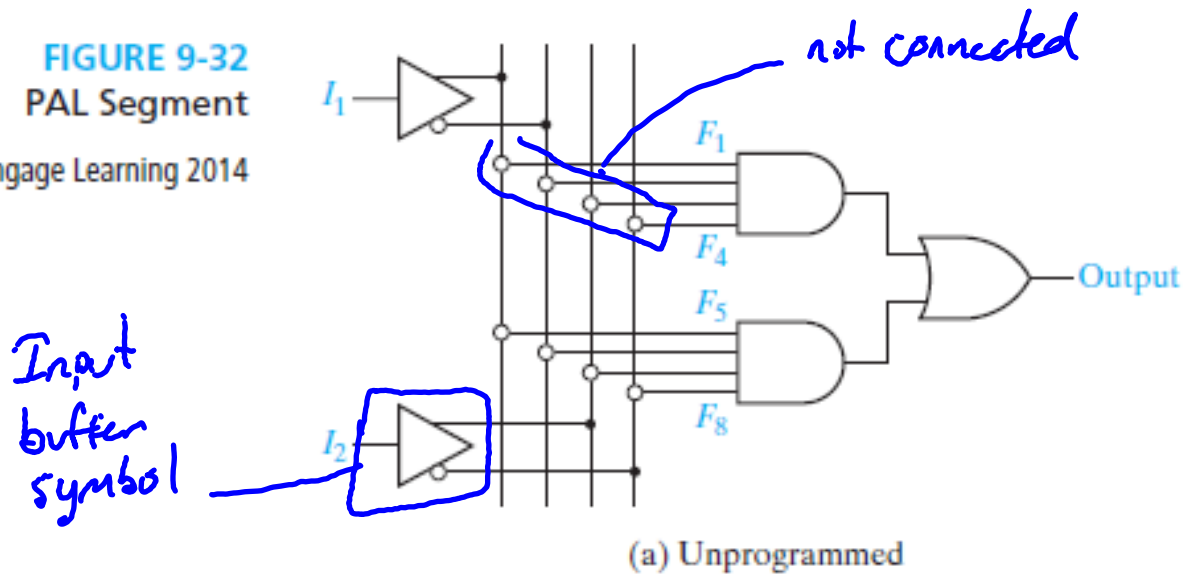



Latches & Flip-Flops

- Property of sequential switching circuits that output depends
 - Not only on present input, but
 - Also on past sequence of inputs.
- Circuits must be able to “remember” something about past history of the inputs in order to produce present output
- Latches and flip-flops are commonly used in sequential circuits
- Latches and flip-flops are memory devices that
 - Can assume one of two stable states, and
 - Have one or more inputs that can cause the output state to change



Basic difference between latches and flip-flops


- For *synchronous* digital systems: common practice is to *synchronize* operation of all flip-flops by a common *pulse signal*
- Each flip-flop has a clock input
- Flip-flops are memory devices that can only change output in response to a clock input, not data inputs
 - Data inputs determine *what* the output state will be
 - Clock triggers *when* the change to that output state happens
- A memory element that has no clock input is typically called a latch




Latches & Flip-Flops

Feedback

 - Logic circuits we have studied so far have not had feedback
- By feedback we mean that output of one of the gates is connected back into the input of another gate so as to form a *closed loop*




Inverter with feedback

 

- Known as a ring-oscillator
- Any odd number n of inverters with output of last fed back to input of first
- Oscillation period $\sim n \times$ (average propagation time)



Latches

 


Two stable conditions

- $X = 1$ or $X = 0$
- Also known as stable *states*
- But need a way to change the state

Write-Enable Latch


$$WRITE = 1 \begin{cases} \bar{D} \rightarrow A \\ D \rightarrow B \end{cases}$$
 
$$WRITE = 0 \begin{cases} \bar{A} \rightarrow B \\ \bar{B} \rightarrow A \end{cases}$$






Latches

 


Two stable conditions

- $X = 1$ or $X = 0$
- Also known as stable states
- But need a way to change the state

Replace Inverters with NOR gates

 

 - NOR operates as inverter when one input wired to 0
- Flip orientation of top NOR
- And what happens if we change the values at extra inputs?






Set-Reset Latch

Set-Reset Latch (SR Latch)

- Can be made from two NOR gates with feedback in *Cross-coupled* form
- Term $[Q(t)]$ used to denote state of Q output of the latch or flip-flop at time any input signal changes
- Term $[Q(t + \varepsilon)]$ denotes state of Q output after latch or flip-flop has reacted to input change and stabilized
- Normally we will write next state with + superscript, without explicitly showing $t + \varepsilon$

 

Present State				Next State	
S	R	Q	P	Q^+	P^+
0	0	0	1		
0	0	1	0		
0	1	0	1		
0	1	1	0		
1	0	0	1		
1	0	1	0		




Set-Reset Latch

Set-Reset Latch (**SR Latch**)

$$\left. \begin{array}{l} S = \\ R = 1 \end{array} \right\} \text{BAD!}$$

- Makes both $P = Q = 0$, but then $P \neq \bar{Q}$
- If S and R are simultaneously changed to 0, both P and Q may both change to 1
- The 1s propagate through the NOR gates changing P and Q to 0
- Latch may continue to oscillate if the gate delays are equal
- : **$S = R = 1$ must be avoided**

 The designer of the circuit using the SR Latch is responsible for avoiding it!







Set-Reset Latch

Set-Reset Latch (SR Latch)

SR Latch Component

 

 - $S = 0, R = 0$
- $S = 0, R = 1$
- $S = 1, R = 0$
- $S = 1, R = 1$ **Do Not Allow**



- Note: No clock input in component figure
- We will later use SR flip-flops, which will have a clock input
- That is how you can tell them apart





Set-Reset Latch

Set-Reset Latch (SR Latch)

- A useful application of the SR Latch is switch debouncing
- Switch contacts tend to vibrate open and closed several times before settling to their final position
- Produces an electronically noisy transition
- This noise can interfere with proper operation of a logic circuit

FIGURE 11-9
Switch Debouncing
with an S-R Latch


© Cengage Learning 2014

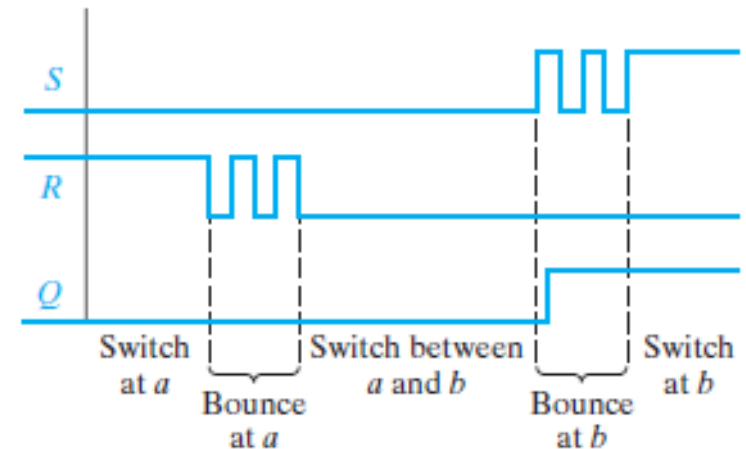 

- This debouncing circuit works for double-throw switches (position *a* or position *b*)
- Debouncing a single-throw switch requires a different circuit


 \bar{S} - \bar{R} Latch

A NAND version is also possible

  \bar{S} - \bar{R} Latch Circuit

(a)

SR Latch Component

 

(b)

Note swapped outputs and complemented inputs

- $\bar{S} = 1, \bar{R} = 1$
- $\bar{S} = 0, \bar{R} = 1$
- $\bar{S} = 1, \bar{R} = 0$
- $\bar{S} = 0, \bar{R} = 0$ Unstable: Do Not Allow

Present State Next State

\bar{S}	\bar{R}	Q	Q^+
1	1	0	0
1	1	1	1
1	0	0	0
1	0	1	0
0	1	0	1
0	1	1	1
0	0	0	-
0	0	1	-

Inputs not allowed