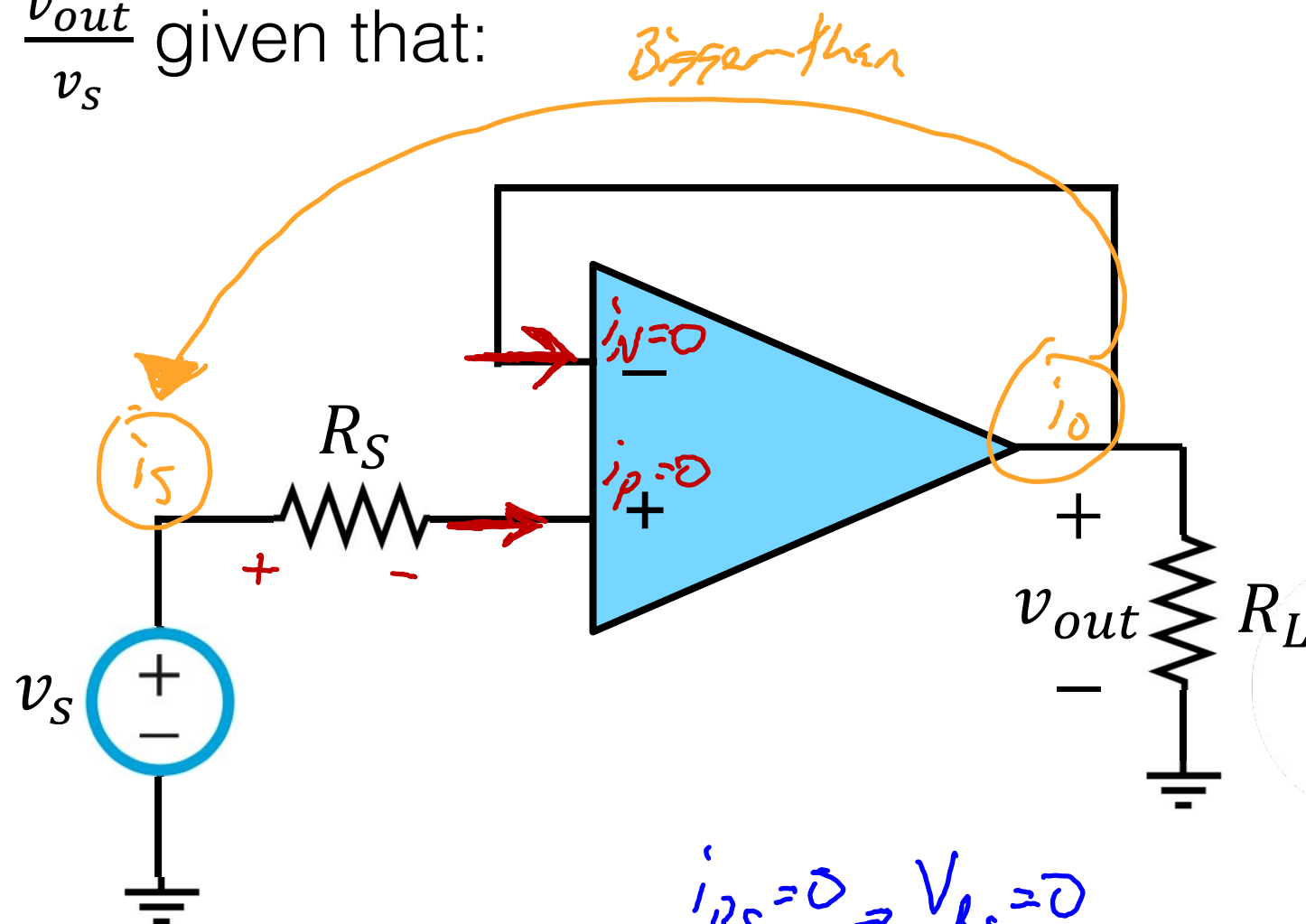




Find  $\frac{v_{out}}{v_s}$  given that:




Volt Follower

$$i_{R_S} = 0 \Rightarrow V_{R_S} = 0$$

$$V_S = V_P$$

ideal model  $V_N = V_P$
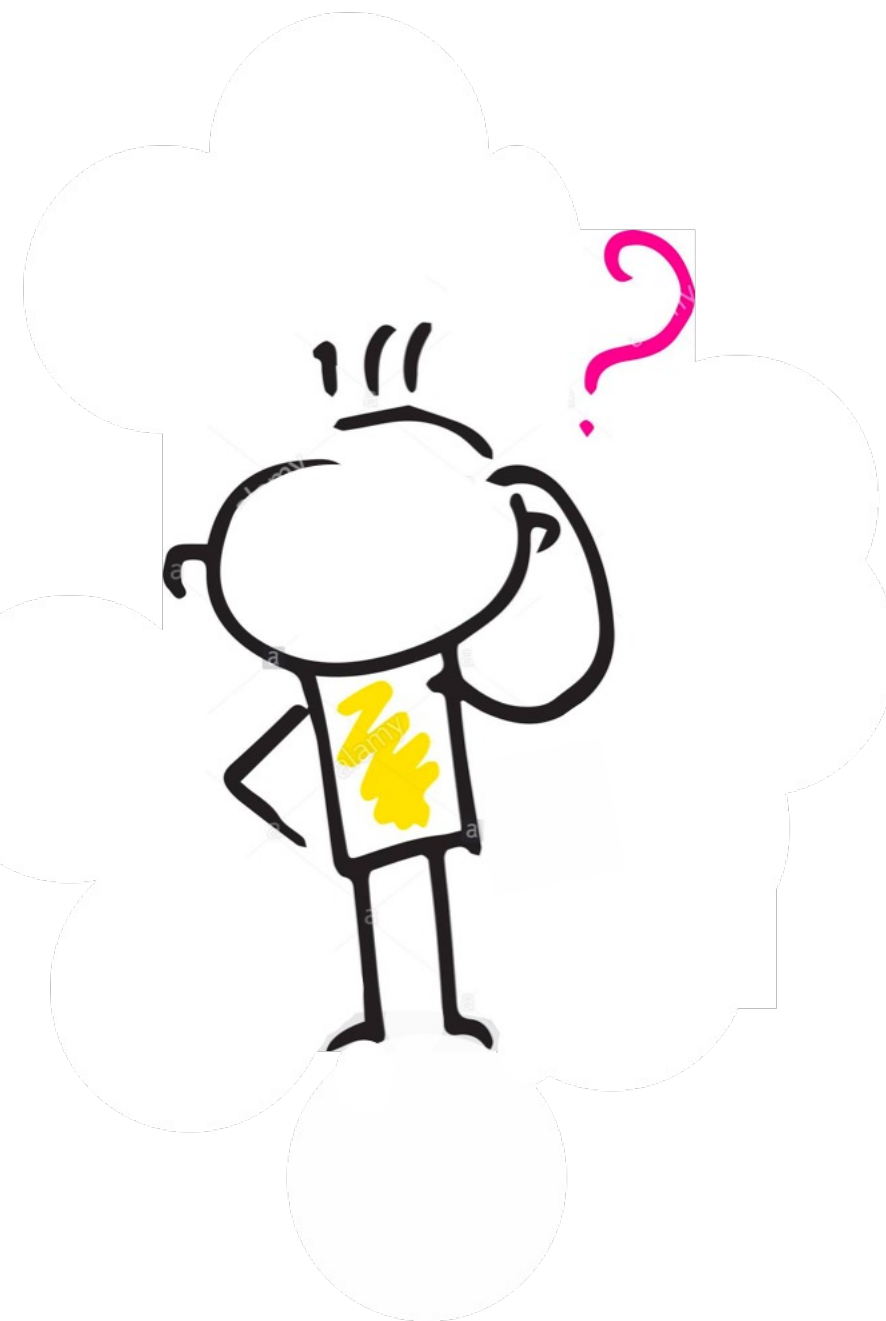
$$V_{out} = V_S = \frac{V_{out}}{V_S} = 1$$





**THE OHIO STATE UNIVERSITY**

---


COLLEGE OF ENGINEERING
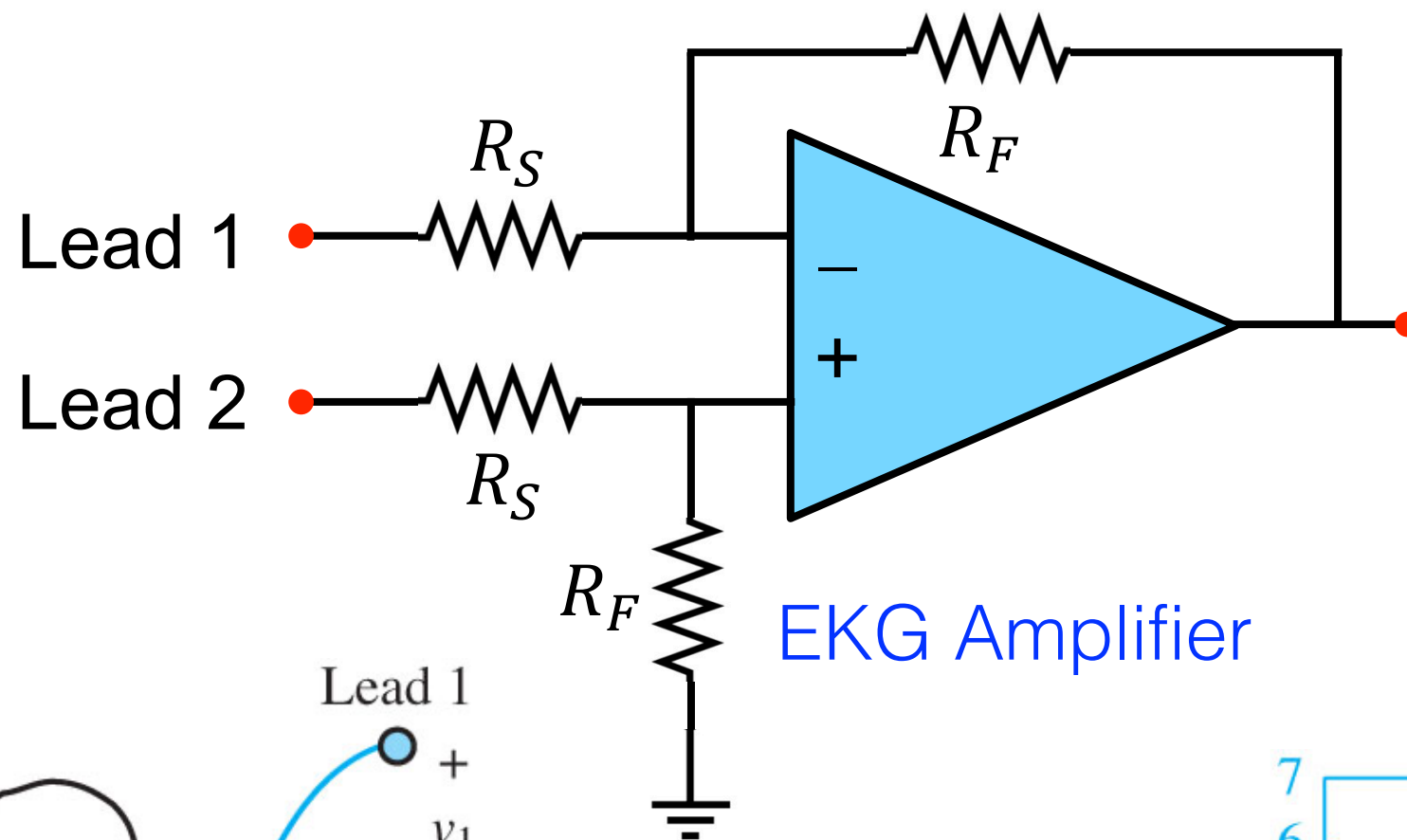
# Op-amp models (Part 2)




- Learning Objectives:
  - Analyze a circuit using the behavioral and ideal model of the op-amp.
  - Identify the voltage gain of a non-inverting and an inverting amplifier.








EKG Amplifier

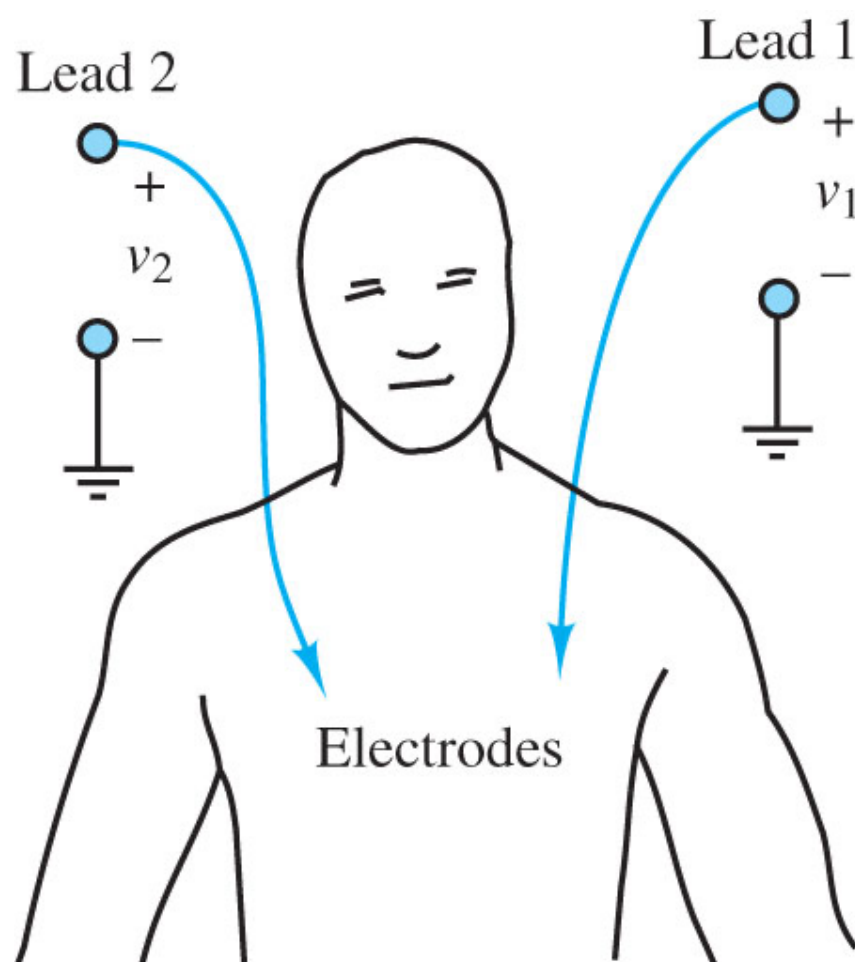

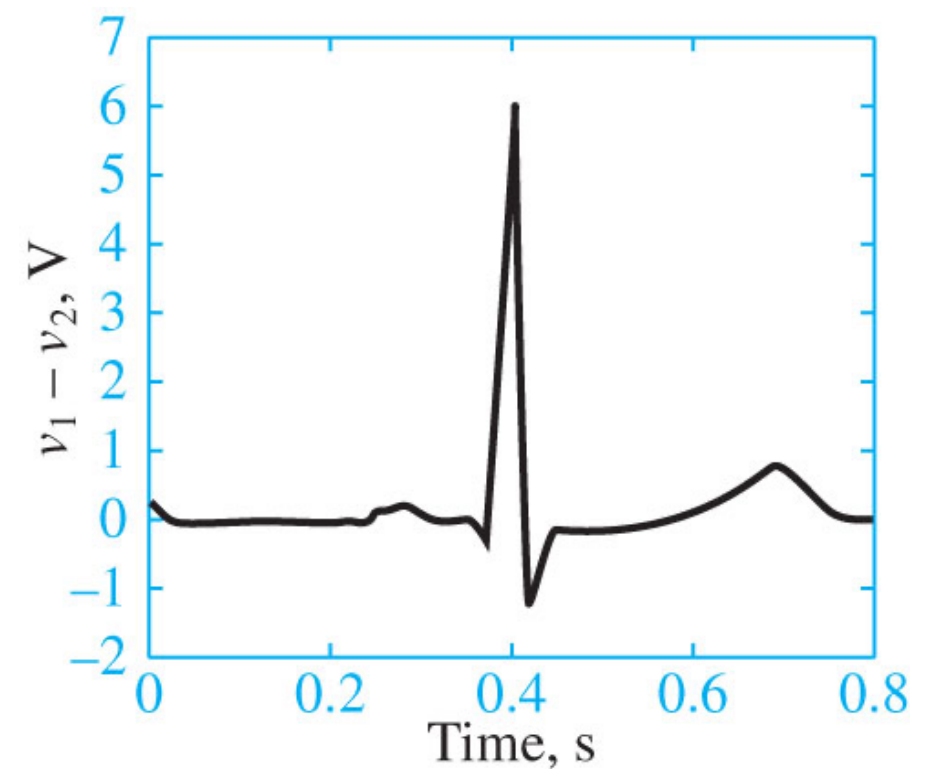Better version:  
Instrumentation  
Amplifier



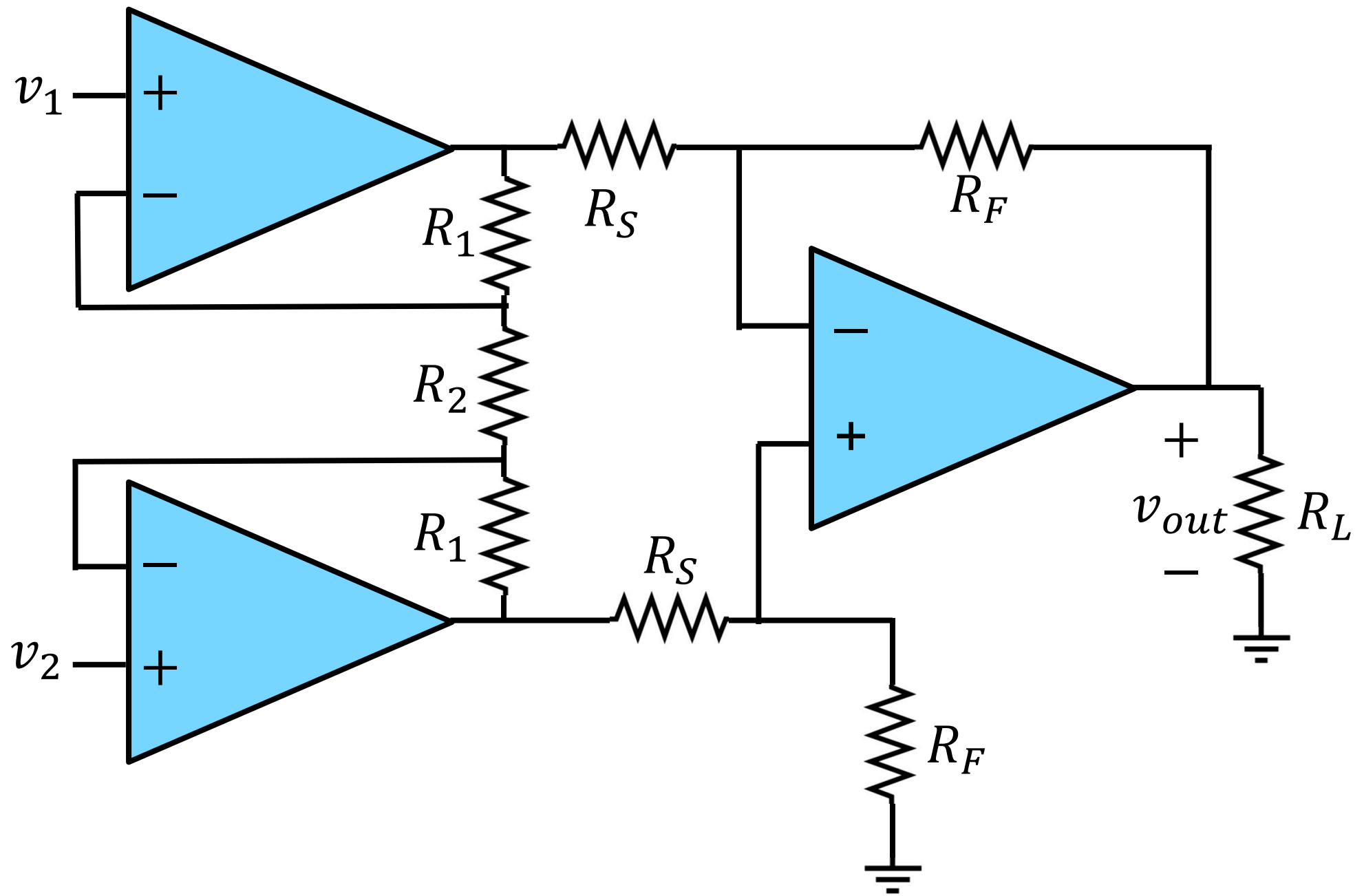

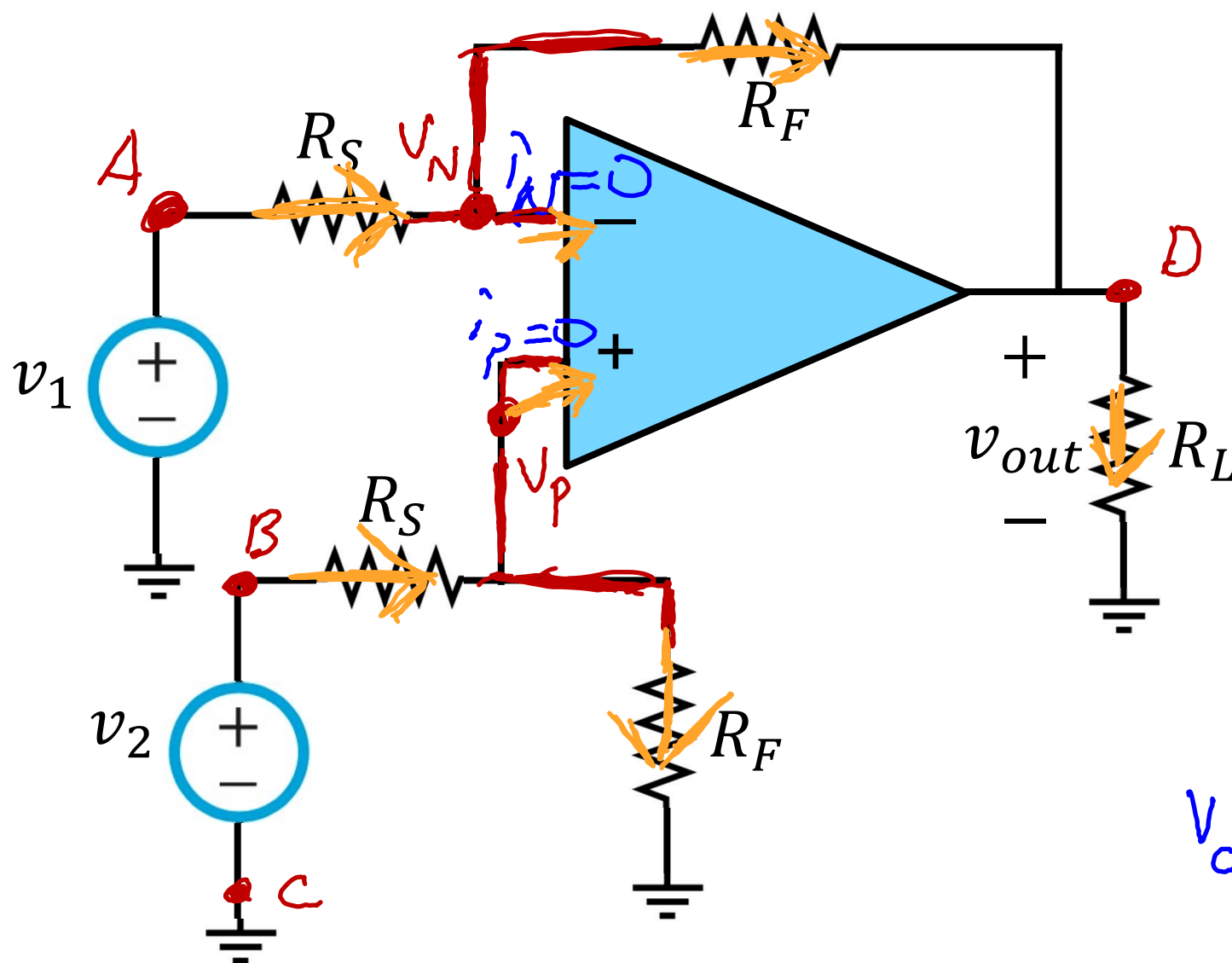

ideal model

$$i_p = i_n = 0$$

$$V_p = V_n$$

Do not do KCL @ output (D)

Node Voltage Analysis

$$V_C = 0V \quad V_A = V_1 \quad V_B = V_2$$

KCL @ N

$$i_{R_S} = i_{R_F} + 0$$

$$\frac{V_1 - V_N}{R_S} = \frac{V_N - V_D}{R_F}$$

KCL @ P

$$i_{R_S} = i_{R_F} + 0$$

$$\frac{V_B - V_P}{R_S} = \frac{V_P}{R_F}$$

$$R_F V_i - R_F V_N = R_S V_N - R_S V_D$$

$$R_F V_i - (R_F + R_S) V_N = -R_S V_D \quad \textcircled{1}$$

$$V_p = V_N \quad \textcircled{2} \text{ in } \textcircled{1}$$

$$R_F V_i - \cancel{(R_F + R_S)} \left( \frac{R_F V_D}{\cancel{R_S + R_F}} \right) = -R_S V_D$$

$$R_F (V_i - V_2) = -R_S V_D$$

$$\frac{R_F}{R_S} (V_2 - V_i) = V_D$$


$$R_F V_B - R_F V_p = R_S V_p$$

$$R_F V_B = (R_S + R_F) V_p$$


$$\textcircled{2} V_p = \frac{R_F V_B}{(R_S + R_F)}$$




# Cascading Amplifiers

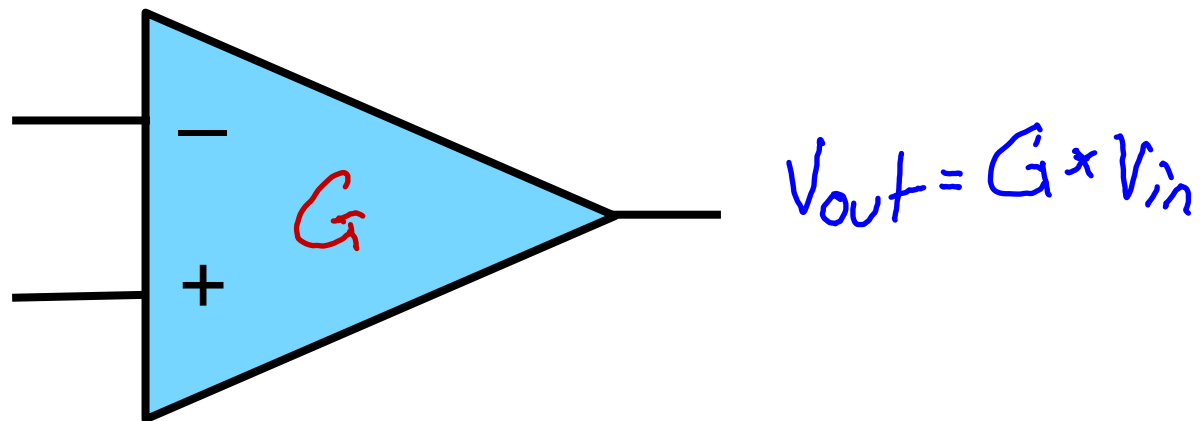


$$V_{out_1} = G_1 V_{in}$$

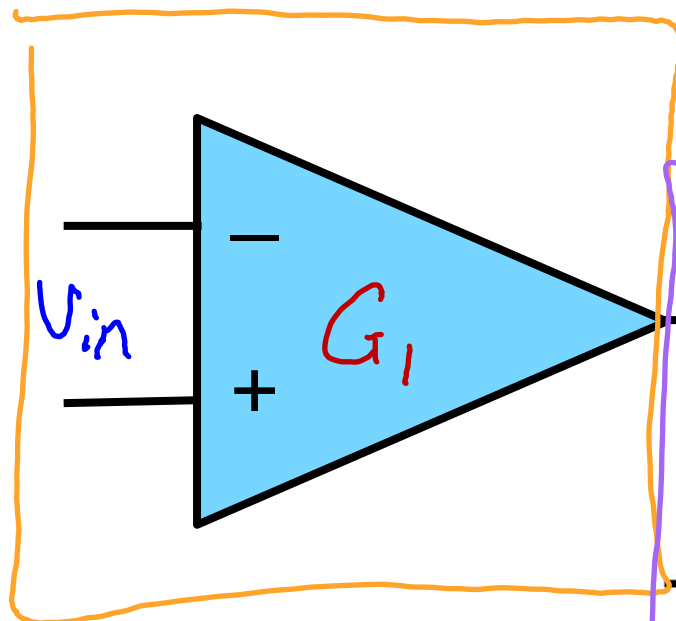
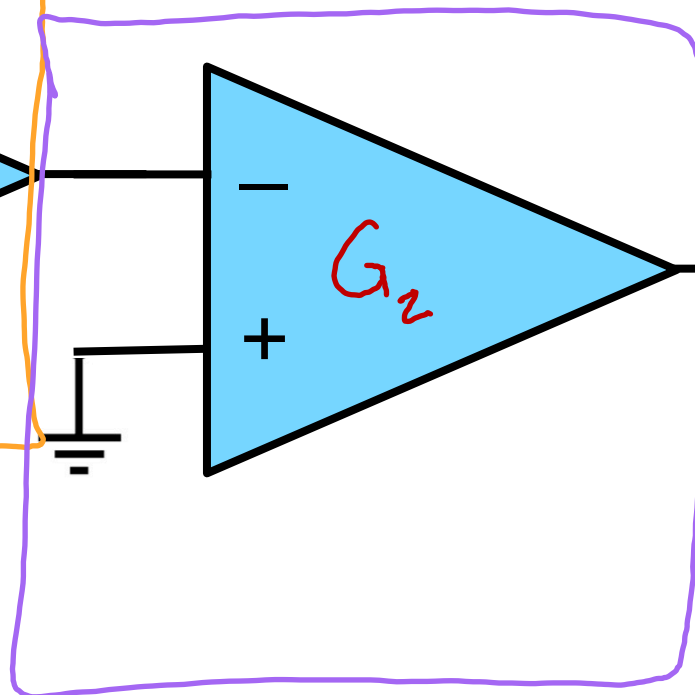
$$V_{out_2} = G_2 V_{in_2} = G_2 G_1 V_{in}$$


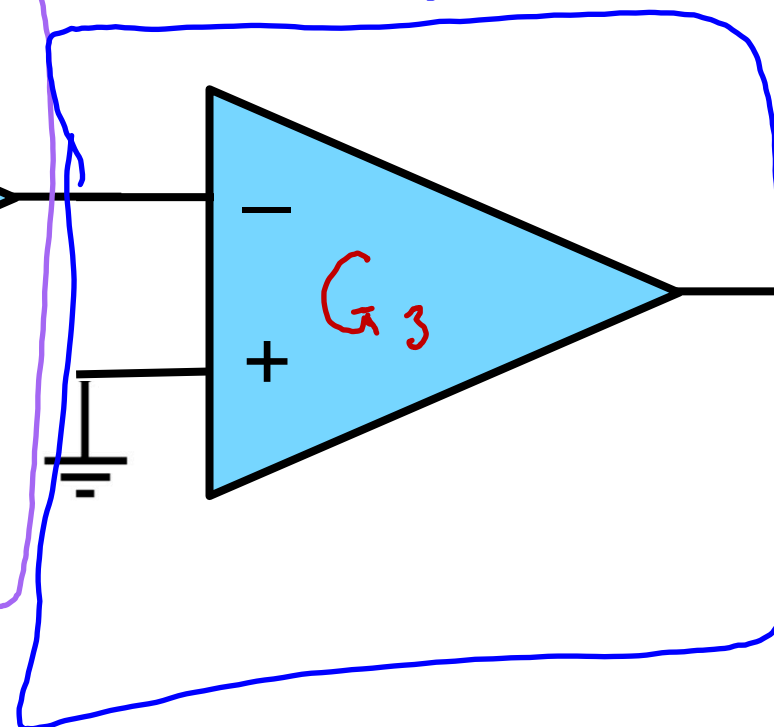
$$V_{out_3} = G_3 V_{in_3} = G_3 G_2 G_1 V_{in}$$




$$\frac{V_{out}}{V_{in}} = G_3 G_2 G_1$$





# Cascading Amplifiers

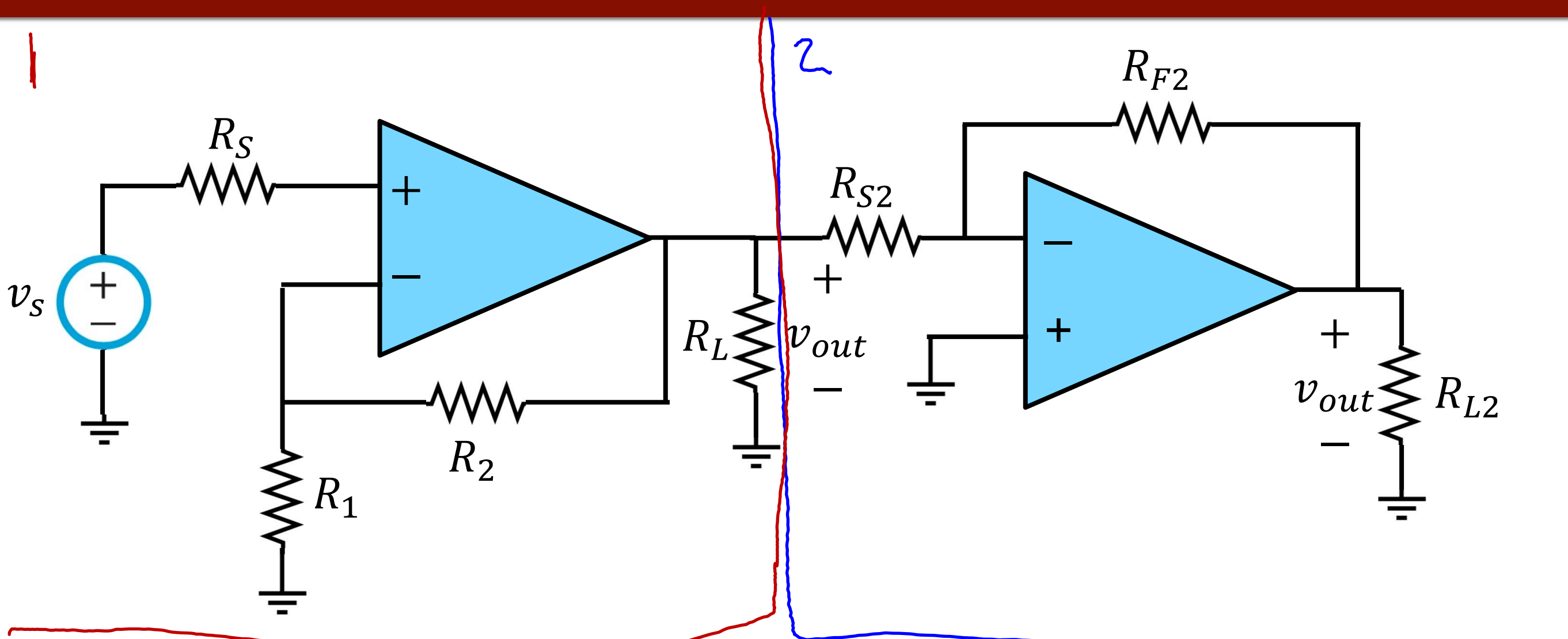

Non-Inverting

$$G_1 = \frac{R_2 + R_1}{R_1}$$

Inverting Op-Amp

$$G_2 = \frac{-R_{F2}}{R_{S2}}$$

$$\frac{v_{out}}{v_s} = G_1 G_2 = -\frac{R_{F2}(R_2 + R_1)}{R_{S2} R_1}$$