



Lecture Outline

Reminders to self:

- ☐ Turn on lecture recording to Cloud
- ☐ Turn on Zoom microphone

- Last Lecture

- Continued K-Maps (3- and 4-variable & don't cares in)
 - Started binary adders (Half-adder, part of full-adder)

- Today's Lecture

- Continue binary adders and subtractors
 - Finish full adder
 - Ripple carry adder and subtracter
 - Carry look-ahead enhancements



Handouts and Announcements

- Announcements
 - Homework Problems – no new assignments
 - Homework Reminders
 - Problems 2-4 and 4-1 due: 11:59pm Thursday 2/2
 - Problems 5-1 and 5-2 due: 11:25am Monday 2/6
 - Participation Quiz 4
 - Based on Lecture 9 (last lecture). 15min limit after you start.
 - Available 11:15am today, due 11:15am tomorrow, but also available 24hrs more with late penalty
 - Read for Friday: pages 193, 199-203



Handouts and Announcements

- Announcements

- Mini-Exam 2 Reminder

- Available 5pm Monday 2/6 through 5:00pm Tuesday 2/7
- Due in Carmen PROMPTLY at 5:00pm on 2/7
- Designed to be completed in ~36 min, but you may use more
- When planning your schedule:
 - I recommend building in 10-15 min extra
 - To allow for downloading exam, signing and dating honor pledge, saving solution as pdf, and uploading to Carmen
- I also recommend not procrastinating

- Exam review topics available on Carmen

- Sample Mini-Exams 1 and 2 from Au20 also available



Full Adder

- Add two binary bits, X_i and Y_i ; and carry bit C_i
- $X_i + Y_i + C_i = S_i, C_{i+1}$ (regular addition here)
- $S_i = \sum m(1,2,4,7)$
- $C_{i+1} = \sum m(3,5,6,7)$
- K-map for S_i

$\begin{matrix} Y_i C_i \\ X_i \end{matrix}$					
		00	01	11	10
0	0	1	0	1	
1	1	0	1	0	

X_i	Y_i	C_i	S_i	C_{i+1}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

- Four groups of 1 - the four minterms are already minimal
- For S_i each minterm has an odd number of 1s
- $S_i = X_i \oplus Y_i \oplus C_i$

Ran out of time here.

Review before continuing.



Full Adder

- Add two binary bits, X_i and Y_i ; and carry bit C_i
- $X_i + Y_i + C_i = S_i, C_{i+1}$ (regular addition here)
- $S_i = \sum m(1,2,4,7)$
- $C_{i+1} = \sum m(3,5,6,7)$
- K-map for C_{i+1}

		$Y_i C_i$			
		00	01	11	10
X_i	0			1	
	1		1	1	1

X_i	Y_i	C_i	S_i	C_{i+1}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

- Groups of 2, 1 variable is eliminated

- $C_{i+1} = X_i Y_i + X_i C_i + Y_i C_i$

Sheet of paper (it's in the wind)




Ripple Carry Adder


- $S_i = X_i \oplus Y_i \oplus C_i$
- $C_{i+1} = X_i Y_i + X_i C_i + Y_i C_i$
- The circuits for each of the i bits are:



*Not unique:
other full adders exist*

 

 - The Carry-out circuit has two levels of logic
 - Two gate-delays for the C_{out} signal to be stable after x , y and c_{in} are applied
- In block diagram form, each Full Adder block contains both the Sum and Carry-out circuits





Four-bit Adder

- In principle, one could make a four-bit adder directly from a truth table using a brute force approach
 - Add $B_3B_2B_1B_0$ to $A_3A_2A_1A_0$
 - Need to allow for a carry-in bit, C_0 *Why?*
 - Nine inputs
 - Five outputs: $S_3S_2S_1S_0$ and C_4 (*Carry out*)
 - Truth table will have $2^9 = 512$ rows
 - This approach very difficult, and logic circuit to implement very complex
- Alternate approach
 - Use multiple instances of the full-adder block
 - This type of approach - using multiple instances of smaller functional blocks - is standard in digital design
 - Allows reliable design of complex systems to perform complex tasks




Ripple Carry Adder

- To make a four-bit adder use four full adders



- Add $B_3B_2B_1B_0$ to $A_3A_2A_1A_0$, bit-by-bit
- With the carry-out from the i -th bit becoming the carry-in of the $i + 1$ bit
- Figure shows addition of $|011$ and $|011$
- Result is 0110 with a carry of 1

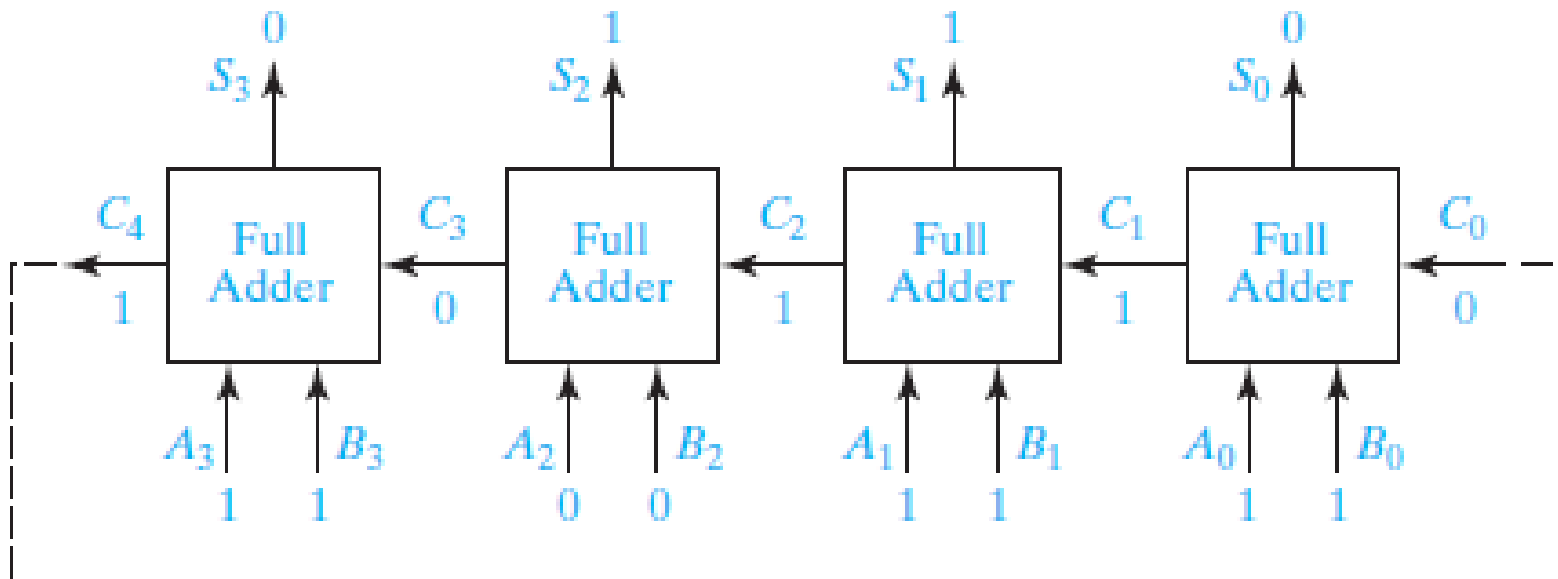Question: What can you say about the result if this is 1's or 2's complement addition?




- Dashed line wire is only needed for: end-around carry for 1's complement
- For 2's complement the carry out of bit 4 is discarded, so wire not needed



Ripple Carry Adder

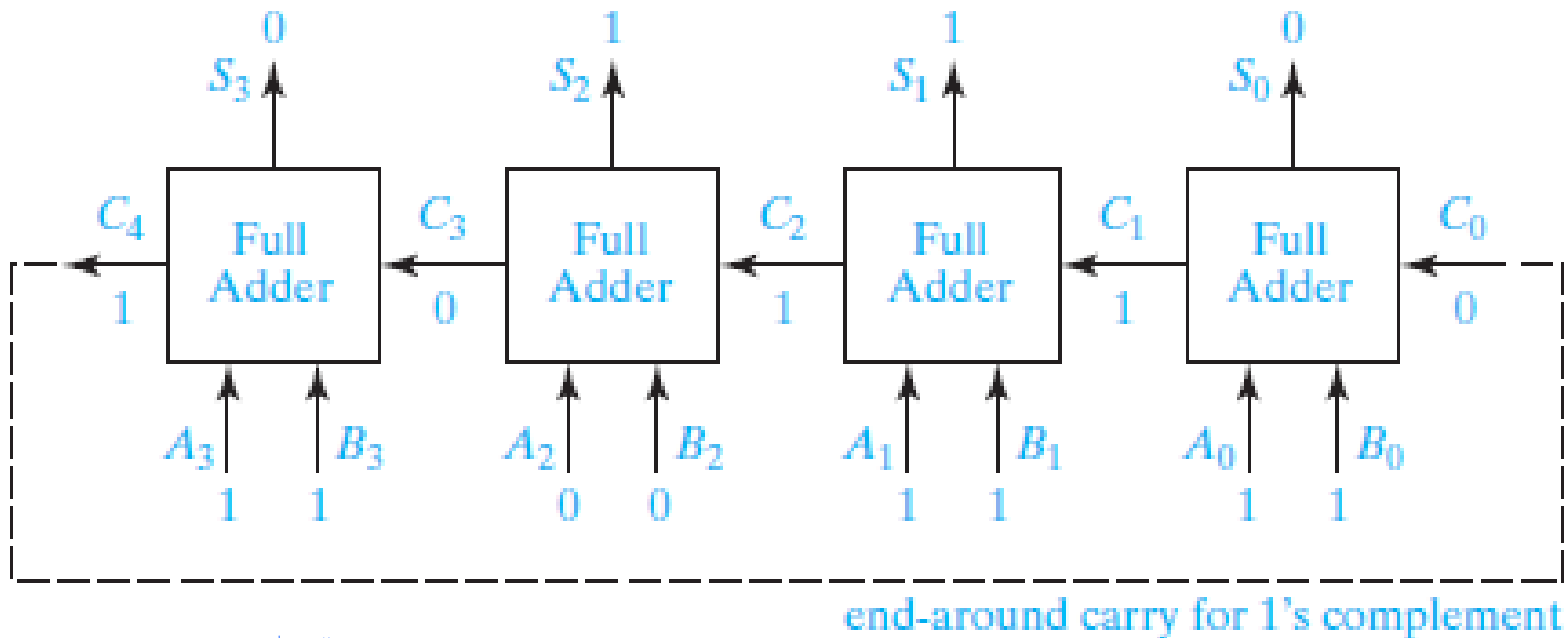- For 2s complement addition
 - Since each there is a delay of 2 gate-delays to generate each carry, and
 - the carry from one bit ripples into the next bit (*hence the name*)
 - there is a total delay of 8 gate-delays to generate the final carry




I lost my phone #
Can I have yours?
(I need a study partner)



Ripple Carry Adder

 
- For 2s complement addition
 - The final carry is discarded (for the result)
 - Note that $C_0 = 0$, giving simplifications $S_0 = A_0 \oplus B_0$ and $C_1 = A_0 B_0$





Ripple Carry Adder

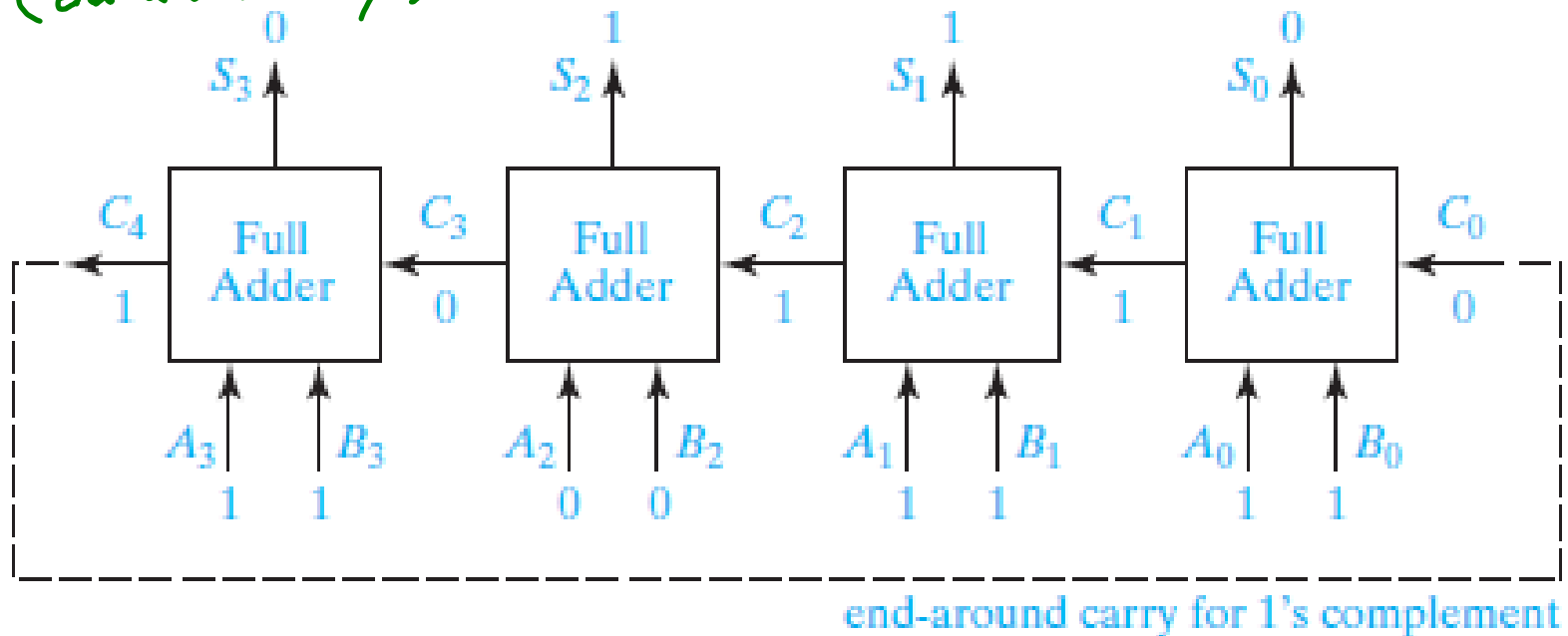- For 1s complement addition
 - The final carry is used for the end-around carry
 - Fed back as C_0 , as shown by the dashed line
 - Have to wait an additional 7 gate delays for certainty its effects rippled to S_3
- (Write in results after end-around carry)*






Ripple Carry Adder

- Overflow detection

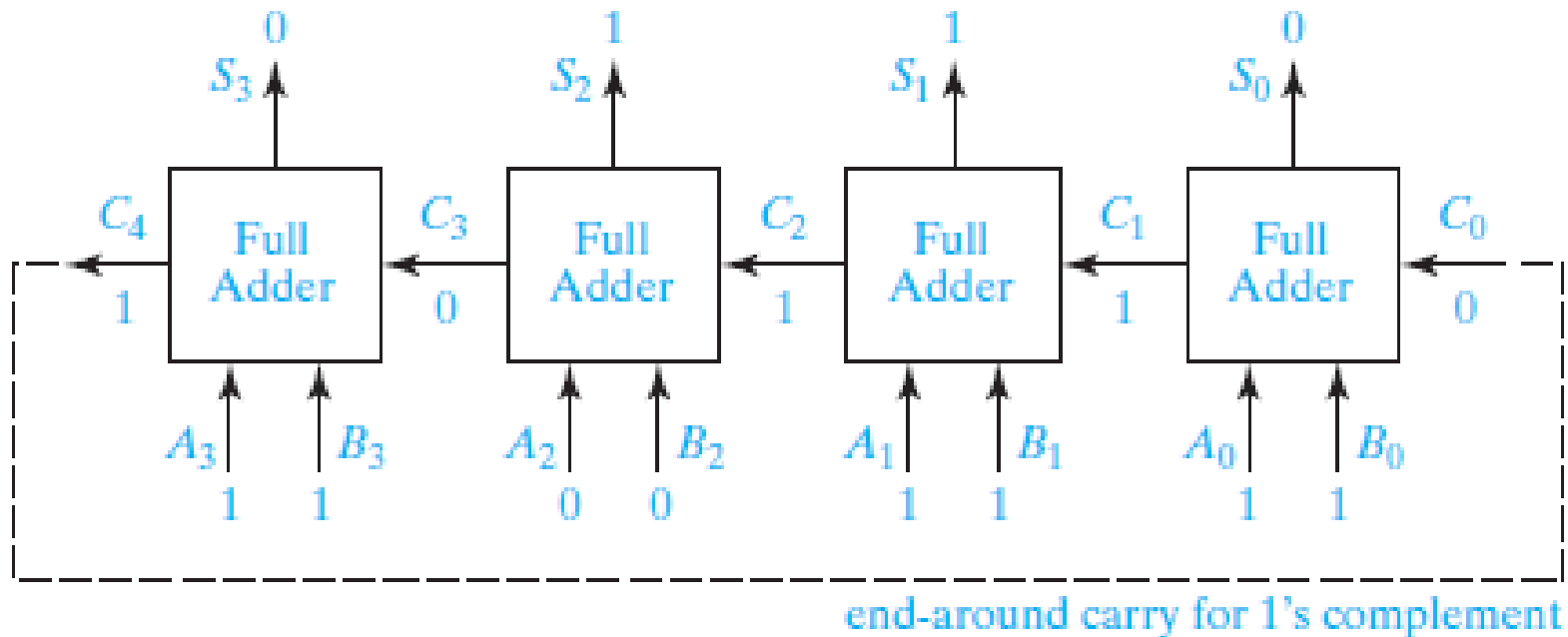
- Adding two positive numbers and getting a negative result
- Adding two negative numbers and getting a positive result
- Use the sign bits of A , B and S
- Overflow $V = A'_3B'_3S_3 + A_3B_3S'_3$





Subtractor (v1)

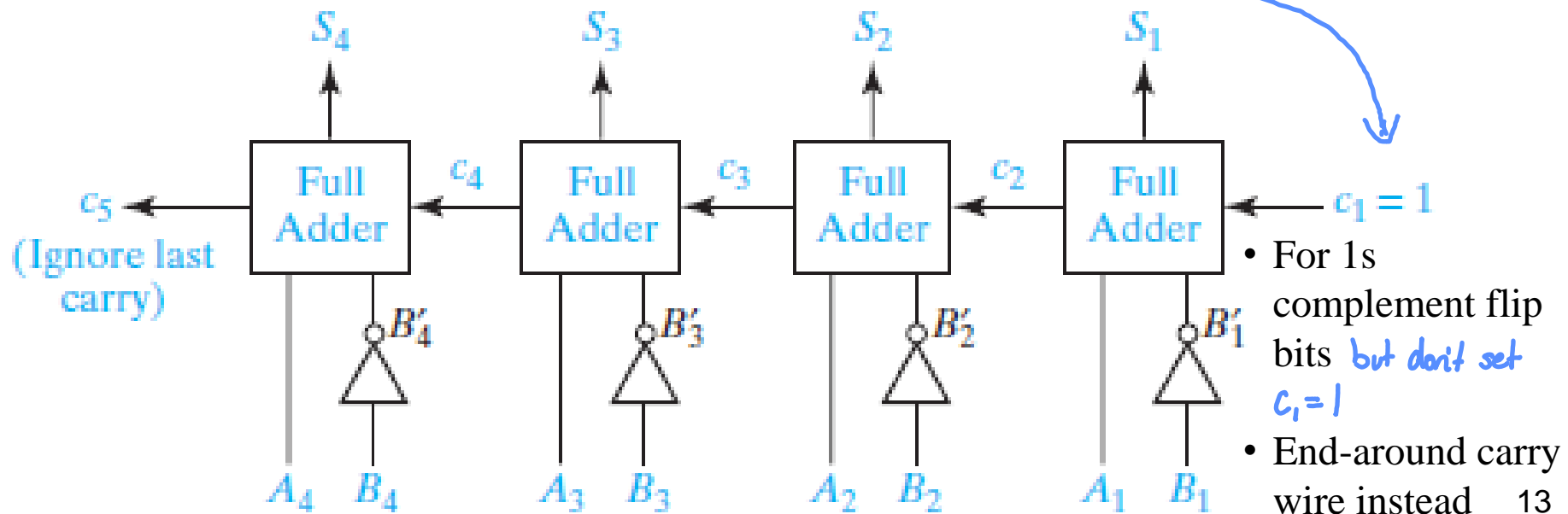- Can be done using the ripple carry adder already developed
- Add the complement of the number to be subtracted
- Can be done with either 1s complement or 2s complement
- 2s complement version shown here (flip bits and add 1)
 - Inverters flip bits B_i
 - Add 1 by setting Carry-in = 1






Subtractor (v2)

- Alternative: perform direct subtraction using full subtractor blocks
- Develop using steps similar to that for full adder, but with *difference* and *borrow* truth table


x_i	y_i	b_i	$b_{i+1}d_i$	
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	1	0
1	0	0	0	1
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

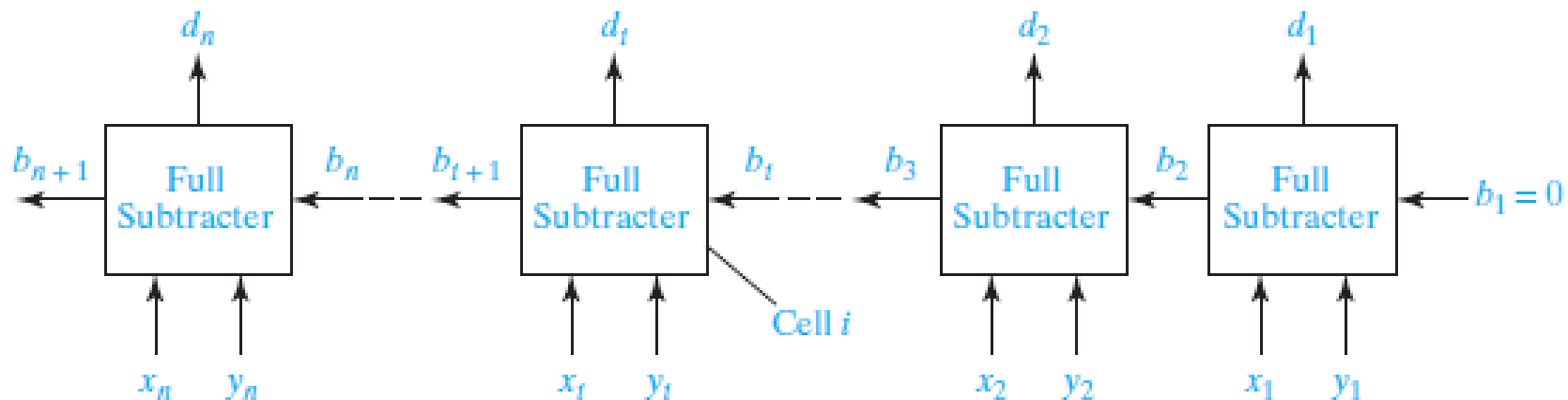



Adder/Subtractor

 
- Both of those versions of a subtractor are separate circuits
 - Need an adder circuit
 - Need a separate subtractor circuit
- Possible to implement a single adder/subtractor circuit
 - With control bit that determines if addition or subtraction is performed
 - Control bit: SUB/\overline{ADD} (1 \rightarrow subtract, 0 \rightarrow add)



B	SUB/\overline{ADD}	OUT
0	0	0
0	1	1
1	0	1
1	1	0



Adder/Subtractor

 

Alternate overflow detection:

- Chapter 1: An overflow occurs iff the carry out of the sign position is not equal to the carry into the sign position
- Caution: For 1's complement may falsely flag overflow before end-around carry ripples through



Ripple Carry Adder


From earlier in lecture

- Since each there is a delay of 2 gate-delays to generate each carry, and
- the carry from one bit ripples into the next bit (*hence name “ripple carry”*)
- there is a total delay of 8 gate-delays to generate the final carry

Intel 4004

first CPU to have
single microprocessor

Speed can be improved

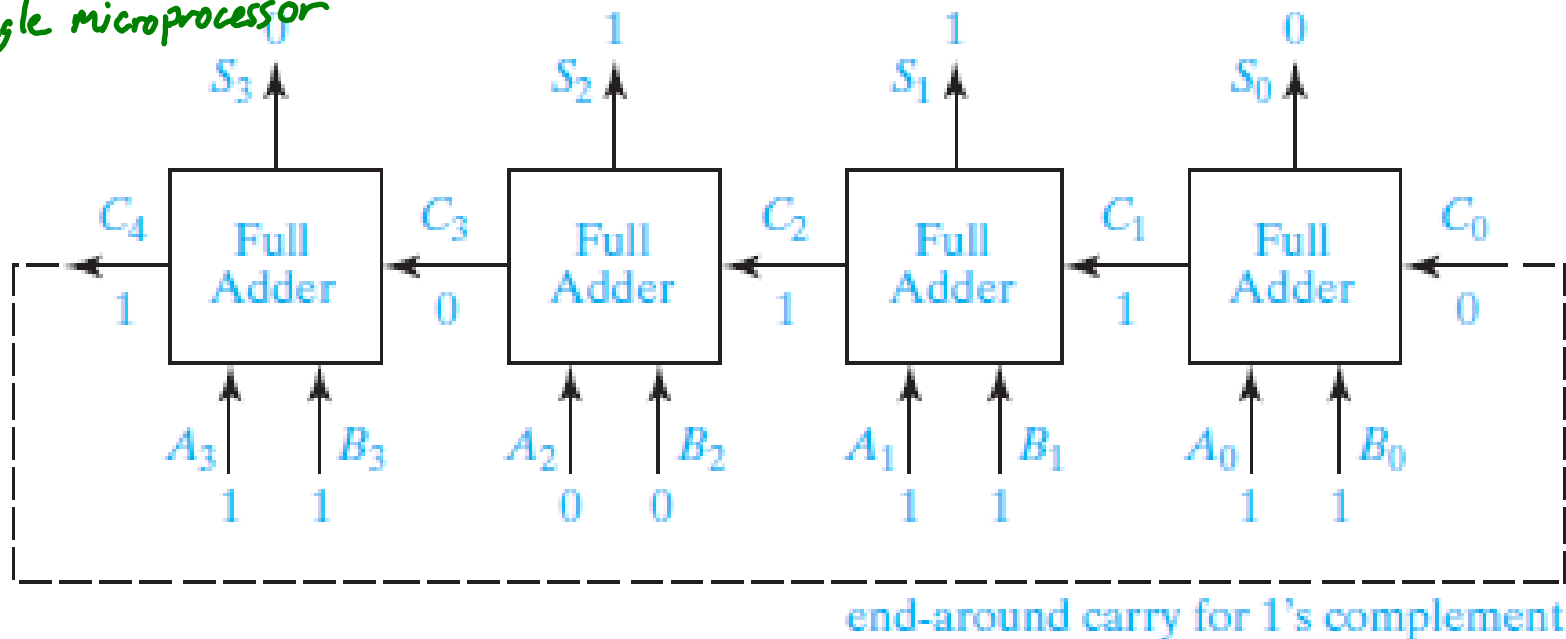



Carry-Lookahead Adder

- In a parallel adder, carry out of i^{th} stage can be written as
$$C_{i+1} = A_i B_i + C_i (A_i + B_i) = A_i B_i + C_i (A \oplus B) = G_i + P_i C_i$$

OR can be replaced by XOR since
 $A_i B_i$ term already covers the 11 case
(look at truth table from earlier)

- Where $G_i = A_i B_i$ is condition for Generation of carry at that stage, &
- $P_i = A_i \oplus B_i$ is condition for Propagation of carry-in to carry-out
- Can be used to algebraically express each carry in terms of
 - The values of the i^{th} bit of A and B , through G_i , and
 - The carry into the first stage, C_0

$$C_1 = G_0 + P_0 C_0$$

$$C_2 = G_1 + P_1 G_0 + P_1 P_0 C_0$$

$$C_3 = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0$$

$$C_4 = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 C_0$$

For a 4-bit
lookahead
carry adder



Carry-Lookahead Adder

$$C_1 = G_0 + P_0 C_0$$

$$C_2 = G_1 + P_1 G_0 + P_1 P_0 C_0$$

$$C_3 = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0$$


$$C_4 = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 C_0$$

Implement in a
2-stage
combinational
logic circuit:

Two-gate delays

Requires a
5-input
AND gate

Requires a
5-input
OR gate

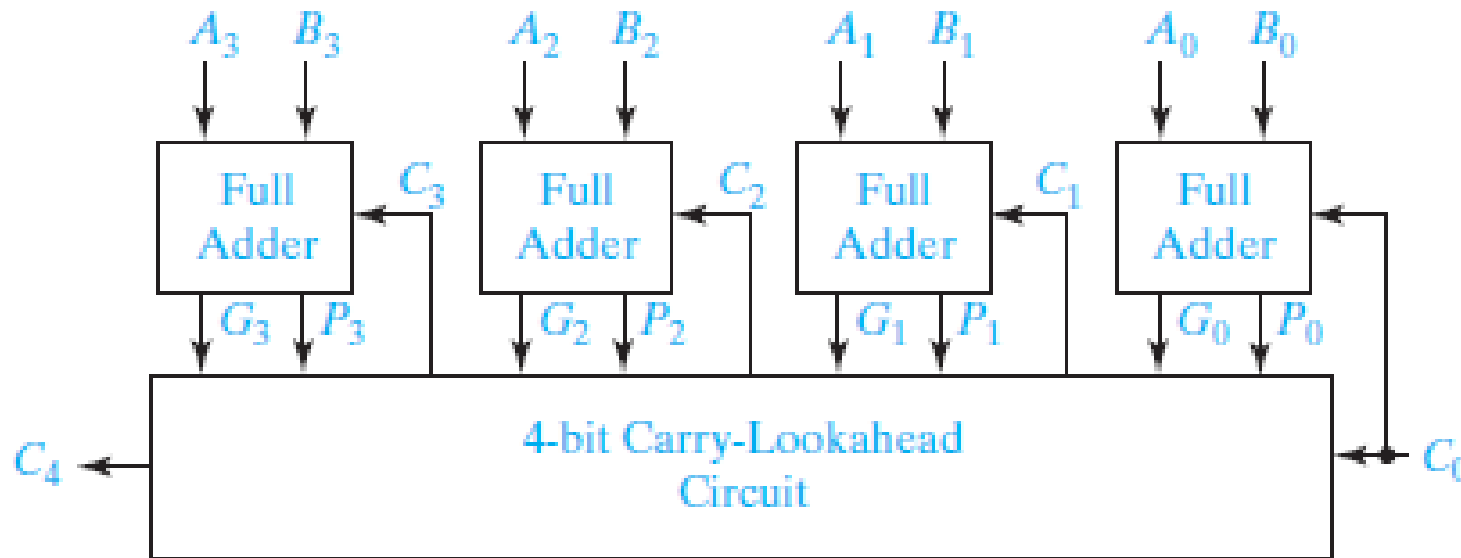


Modified full adder circuit on next slide: (G_i & P_i but no C_{i+1})


- After the G_i and P_i of the full adders are stable, a change in C_0 propagates to all C_i ($i = 1, 2, 3, 4$) in 2 gate-delays
- Ripple carry adder: change in C_0 took 8 gate-delays to reach C_4



Carry-Lookahead Adder

 

Original Full Adder

 




16-bit Carry-Lookahead Adder


- If more than four bits need to be added
 - In principle the carry-lookahead circuit can be expanded
 - But each additional bit means number of inputs to AND and OR gates increases
 - Number of inputs is known as “*fan-in*”
 - Practical limits (from transistor-level design of gates) set a maximum fan-in
 - In practice, can cascade the 4-bit carry-lookahead circuits
 - A 16-bit adder shown here

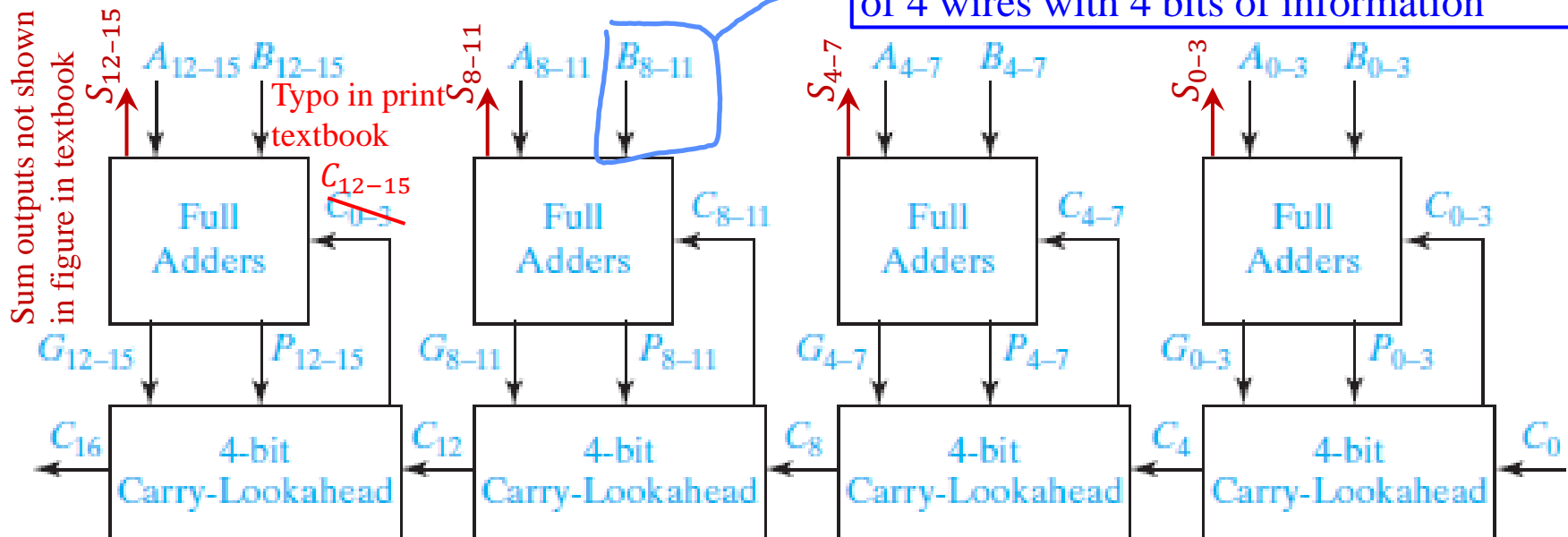Observe notation: Now represents a “bus” of 4 wires with 4 bits of information





16-bit Carry-Lookahead Adder

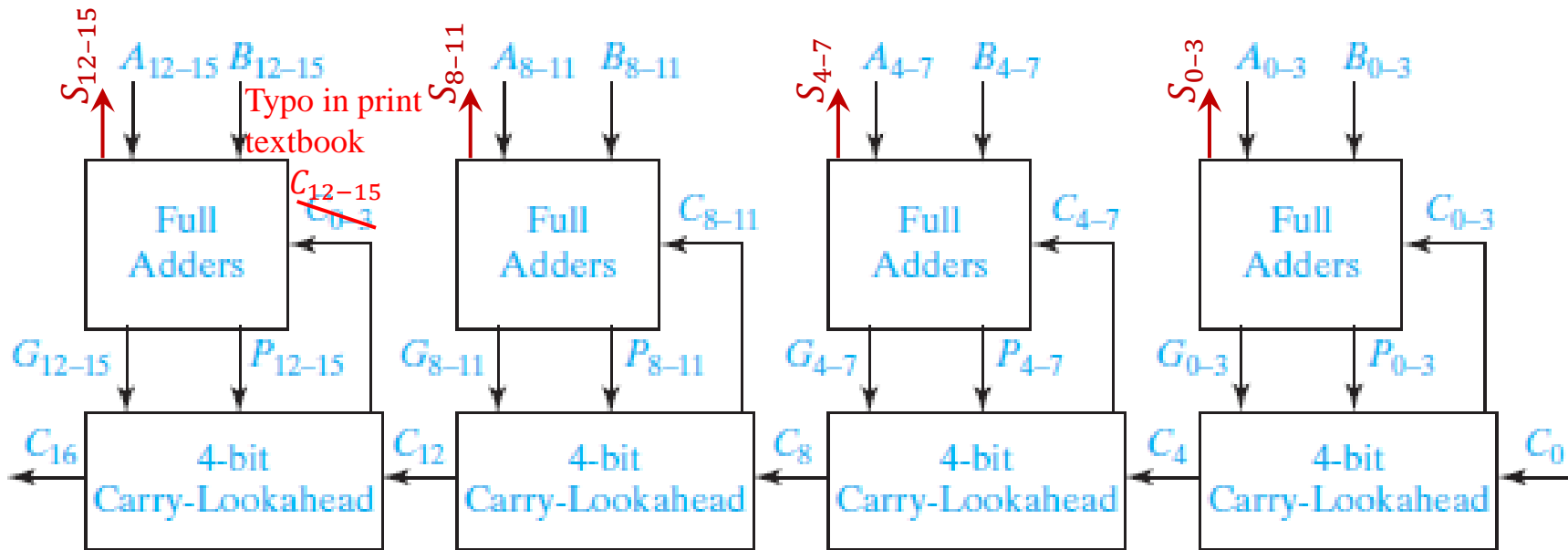


- But now there is ripple delay cascading through the Carry-Lookahead circuits: $C_0 \Rightarrow C_4 \Rightarrow C_8 \Rightarrow C_{12} \Rightarrow C_{16}$
- It is still an improvement over brute force 16 bit ripple adder
 - Brute force 16 bit ripple adder: gate delays for C_{16} to settle
 - 16 bit adder shown here: gate delays
- Additional improvement possible: additional level of Carry-Lookahead



16-bit Carry-Lookahead Adder

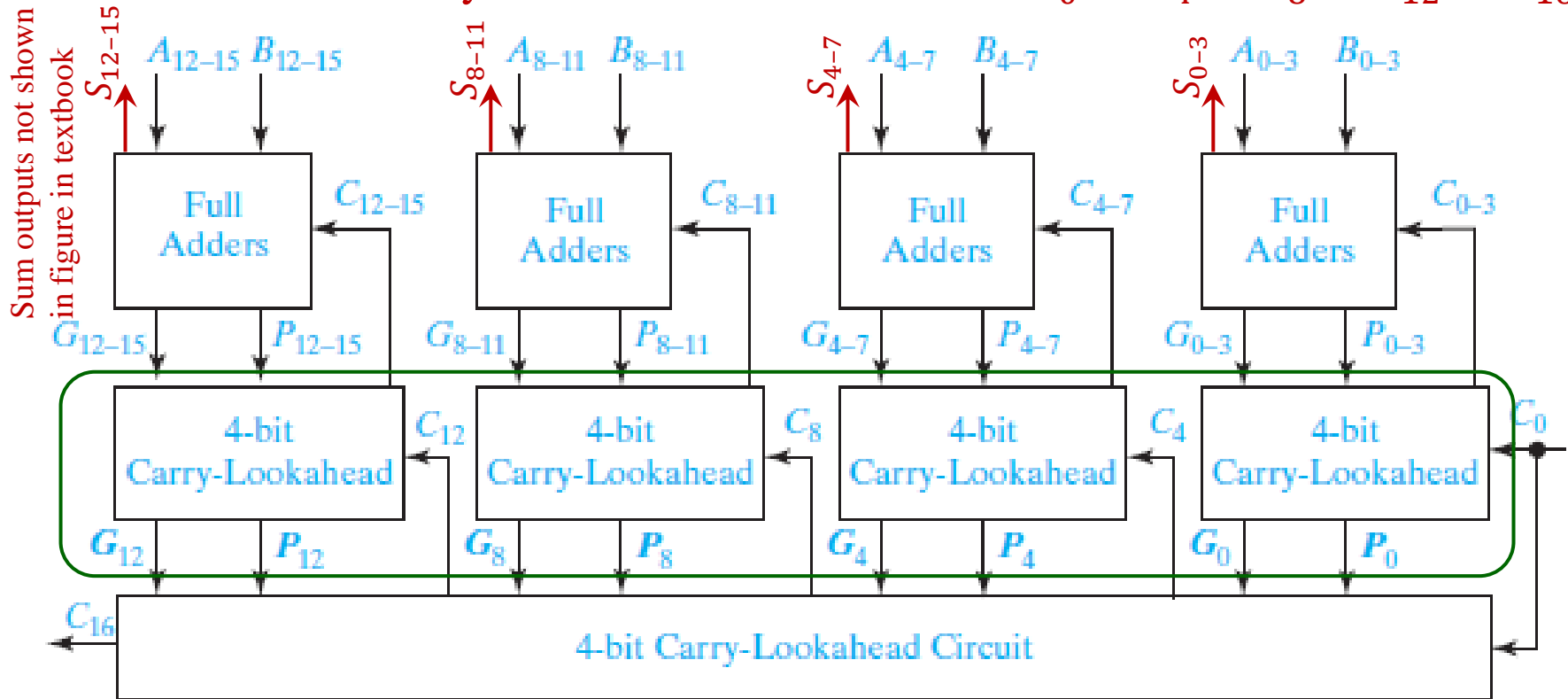Additional level of Carry-Lookahead added to handle $C_0 \Rightarrow C_4 \Rightarrow C_8 \Rightarrow C_{12} \Rightarrow C_{16}$



This is same Carry-Lookahead circuit as before

But first level of Carry-Lookahead modified to output G and P as shown, but not the carries to pass forward