



# Lecture Outline

---

## Reminders to self:

- ☐ Turn on lecture recording to Cloud
- ☐ Turn on Zoom microphone

## • Last Lecture

- Continued Multiplexers
- Brief look at CMOS gates at transistor level
- Started Three-state buffers / Tri-state outputs

## • Today's Lecture

- Continue Three-state buffers / Tri-state outputs
- Decoders
- Encoders
- ROM



# Handouts and Announcements

---

- Announcements

- Homework Problems 9-1 and 9-2

- Posted on Carmen yesterday afternoon (2/16)
- HW 9-1 due: 11:25am Wednesday 2/22
- HW 9-2 due: 11:59pm Thursday 2/23

- Homework Reminder:

- HW 8-1 and 8-2 Now Past-Due: 11:59pm Thursday 2/16

- Participation Quiz 8 available starting 12:25pm today

- Due 12:25pm Saturday 2/18
- Available until 12:25pm Sunday 2/19 with late penalty

- Read for Monday: pages 275-280, 331, 336-342



# Handouts and Announcements

---

- Announcements

- Mini-Exam 3 Reminder

- Available 5pm Monday 2/20 through 5:00pm Tuesday 2/21
- Due in Carmen PROMPTLY at 5:00pm on 2/21
- Designed to be completed in ~36 min, but you may use more
- When planning your schedule:
  - I recommend building in 10-15 min extra
  - To allow for downloading exam, signing and dating honor pledge, saving solution as pdf, and uploading to Carmen
- I also recommend not procrastinating

- Exam review topics available on Carmen


- Sample Mini-Exams 3 and 4 from Au20 also available

## Adder/Subtractor

Here is a 3-bit version, implemented using multiplexers

## Quiz 10 review

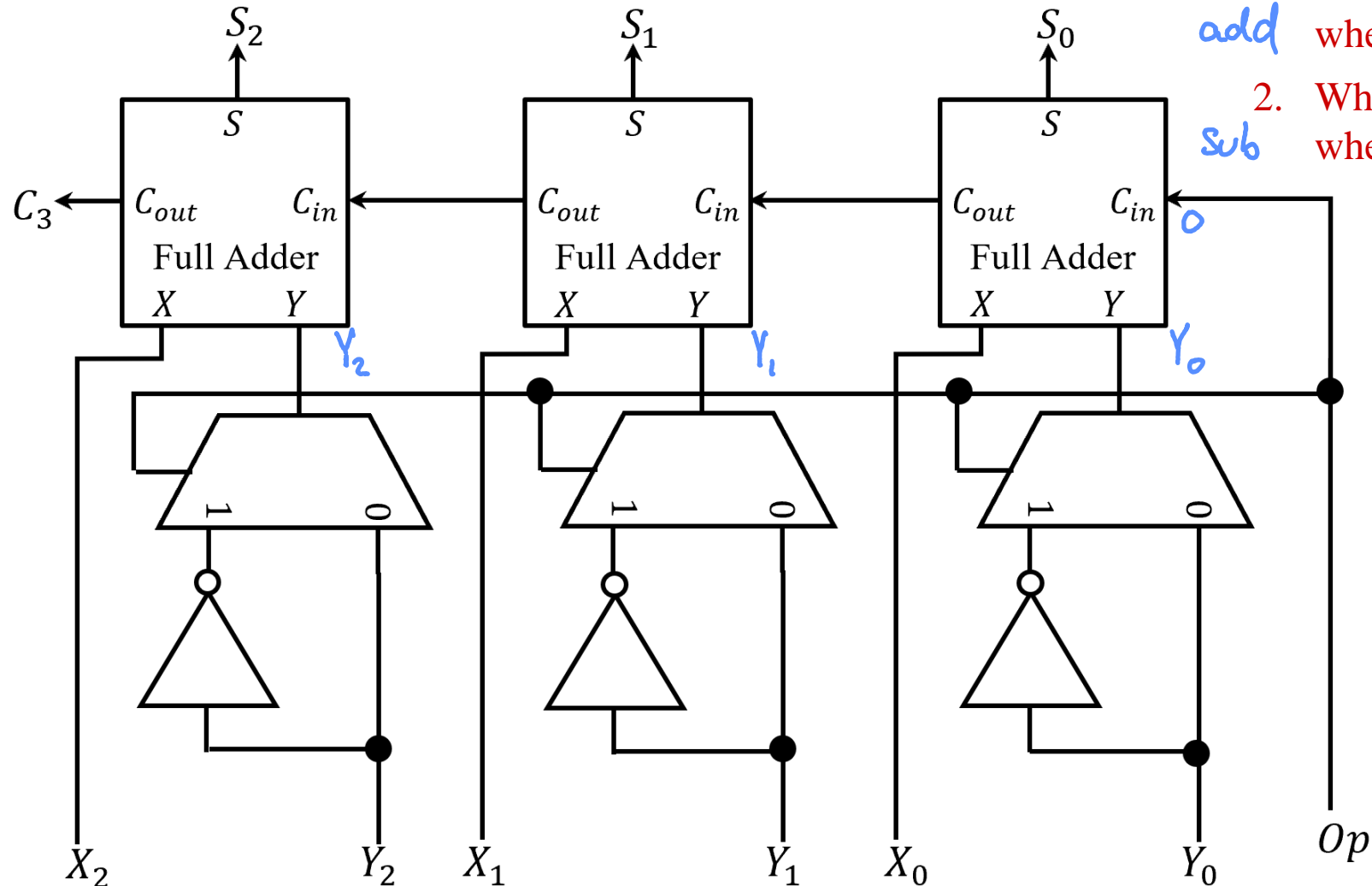1. What operation  
*add* when  $Op = 0$ ?
2. What operation  
*sub* when  $Op = 1$ ?





# HW 7-3 Review

Draw a logic circuit that uses only 2-input NAND gates to implement the following function. Your circuit **must use the minimum number of 2-input NAND gates.**

Since you are limited to only 2-input NAND gates you may need to use more than two levels of logic.

$$F(A, B, C, D) = ABCD' + ABC' + AB'C'D + A'BC' + AB'C$$

- **Start by minimizing the expression**

- We taught how to use K-Maps for that: when algorithms properly followed you know you have a minimum SOP expression
- Some students tried Boolean algebra instead – all of the ones I graded stopped algebra too soon - before they had a minimum expression → too many gates
- Some students didn't minimize at all → saw a case with 21 gates! – can be done with 6

- **Then try to factor expression to reach fan-in constraint**

- Brute force implementation likely needs extra gates – often 2-NAND used as inverters
- Optimal solution of this problem didn't need any inverters

- **Then convert circuit/expression of 2-AND and 2-OR gates to 2-NAND only**





- Graphical approach with inversion bubbles, or
- Boolean algebra with liberal use of DeMorgan's



# Three-State Buffers

## • Straight-through/Cross-through MUX

- 
- 
- 
- 

    

- Two outputs tied together
- But only one active at a time
- Other in high-Z state




## Three-State Buffers

- Three-state bus as alternative to MUX data selector
- Example: 4-bit adder with one operand sourced from four different locations

FIGURE 9-15

4-Bit Adder with  
Four Sources for  
One Operand

© Cengage Learning 2014

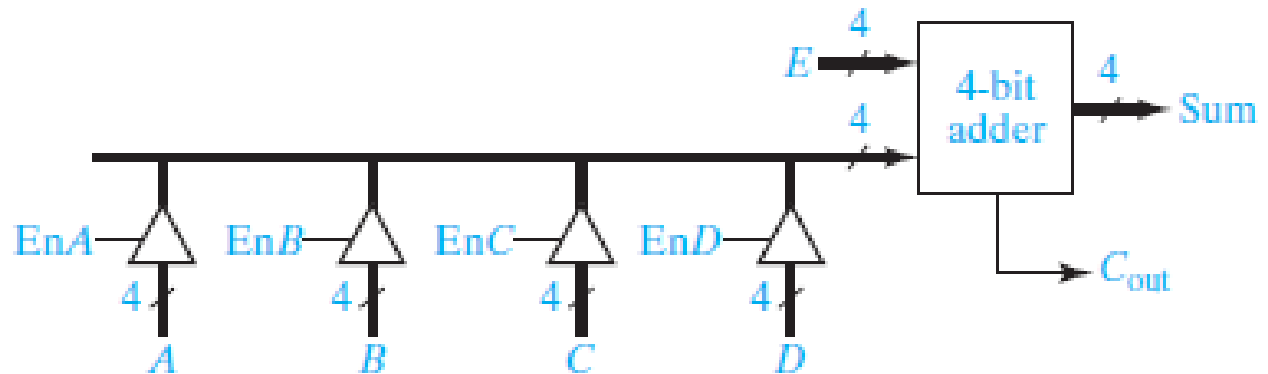

- A bus controller is needed to ensure that only one of  $EnA$ ,  $EnB$ ,  $EnC$ , and  $EnD$  are true at any time
- Outputs of the other buffers must be in
- Device known as                      can be used for bus control




# Decoder

- A decoder is another commonly used type of IC
- Example: 3-8 Decoder Block Diagram and Truth Table:

**FIGURE 9-17**

A 3-to-8 Line Decoder

© Cengage Learning 2014

 

- Input binary #
- Activates the line corresponding to that number

•

•





# Three-State Buffers

- Device known as **decoder** can be used for bus control


 


FIGURE 9-15

4-Bit Adder with  
Four Sources for  
One Operand


© Cengage Learning 2014

 


 
# Decoder


- In general,  $n$ -to- $2^n$  line decoder generates all  $2^n$  minterms of the  $n$  input variables
- Example: Use to implement
  - $f_1 = \sum m(1,2,5,7)$
  - $f_2 = \sum m(0,3)$




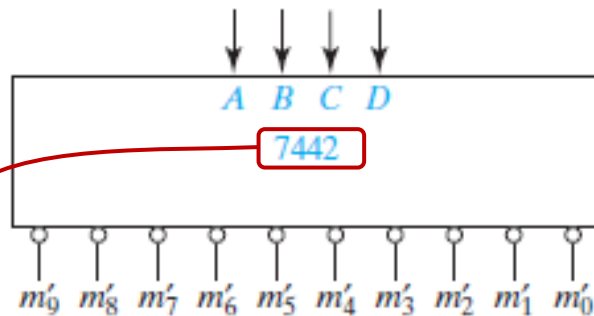
## Decoder

- Decoder may also have inverting outputs
- And may also only have a subset of the lines



(b) Block diagram

7400-series TTL part number  
4-to-10 line decoder

- Generates  
or
- Use inverted outputs  
with                      gates to  
generate functions

BCD Input				Decimal Output									
A	B	C	D	0	1	2	3	4	5	6	7	8	9
0	0	0	0	0	1	1	1	1	1	1	1	1	1
0	0	0	1	1	0	1	1	1	1	1	1	1	1
0	0	1	0	1	1	0	1	1	1	1	1	1	1
0	0	1	1	1	1	1	0	1	1	1	1	1	1
0	1	0	0	1	1	1	1	0	1	1	1	1	1
0	1	0	1	1	1	1	1	1	0	1	1	1	1
0	1	1	0	1	1	1	1	1	1	0	1	1	1
0	1	1	1	1	1	1	1	1	1	1	0	1	1
1	0	0	0	1	1	1	1	1	1	1	1	0	1
1	0	0	1	1	1	1	1	1	1	1	1	1	0
1	0	1	0	1	1	1	1	1	1	1	1	1	1
1	0	1	1	1	1	1	1	1	1	1	1	1	1
1	1	0	0	1	1	1	1	1	1	1	1	1	1
1	1	0	1	1	1	1	1	1	1	1	1	1	1
1	1	1	0	1	1	1	1	1	1	1	1	1	1
1	1	1	1	1	1	1	1	1	1	1	1	1	1

(c) Truth Table




## Decoder

- Use inverted outputs with OR gates to generate functions

**FIGURE 9-19**

Realization of a  
Multiple-Output  
Circuit Using a  
Decoder

© Cengage Learning 2014

 

$$f_1(a, b, c, d) = m_1 + m_2 + m_4 \text{ and } f_2(a, b, c, d) = m_4 + m_7 + m_9$$



# Priority Line Encoder

- Encoders have the inverse function of decoders
- If more than one input = 1, then the biggest input wins
  - Example:  $y_7$  &  $y_3 = 1$
  - Output =
  - The don't cares implement that
- Output  $d = 1$  if any input = 1. Not all encoders have this.

**FIGURE 9-20**  
An 8-to-3 Priority Encoder


© Cengage Learning 2014

$y_0$	$y_1$	$y_2$	$y_3$	$y_4$	$y_5$	$y_6$	$y_7$	$a$	$b$	$c$	$d$
0	0	0	0	0	0	0	0	0	0	0	0
1	0	0	0	0	0	0	0	0	0	0	1
X	1	0	0	0	0	0	0	0	0	1	1
X	X	1	0	0	0	0	0	0	1	0	1
X	X	X	1	0	0	0	0	0	1	1	1
X	X	X	X	1	0	0	0	1	0	0	1
X	X	X	X	X	1	0	0	1	0	1	1
X	X	X	X	X	X	1	0	1	1	0	1
X	X	X	X	X	X	X	1	1	1	1	1


 
# Basic Encoder Example

Magnetic reed switches  
wired to deliver logic 1  
when activated by  
magnet




Wheel position  
encoded into 3-bit  
binary word:  $abc$

$a$	$b$	$c$	Wheel Position
0	0	0	North
0	0	1	North-East
0	1	0	East
0	1	1	South-East
1	0	0	South
1	0	1	South-West
1	1	0	West
1	1	1	North-West


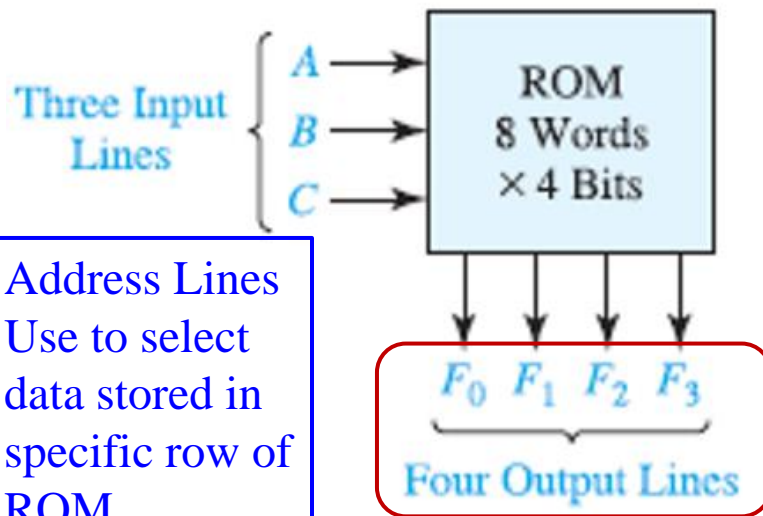
# Read-Only Memory

- Read-only memory ( ) consists of an array of semiconductor devices interconnected to store an array of binary data
- Once binary data is stored in the ROM:
  - Data can be whenever desired
  - But data that is stored during normal operation
  - Lookup Table ( )
- Example: An 8-Word, 4-bit ROM



(a) Block diagram

A	B	C	F <sub>0</sub>	F <sub>1</sub>	F <sub>2</sub>	F <sub>3</sub>
0	0	0	1	0	1	0
0	0	1	1	0	1	0
0	1	0	0	1	1	1
0	1	1	0	1	0	1
1	0	0	1	1	0	0
1	0	1	0	0	0	1
1	1	0	1	1	1	1
1	1	1	0	1	0	1

(b) Truth table for ROM


**Typical** (Example)  
Actual data will be  
for programmed  
application

Typical Data  
Stored in  
ROM  
( $2^3$  words of  
4 bits each)


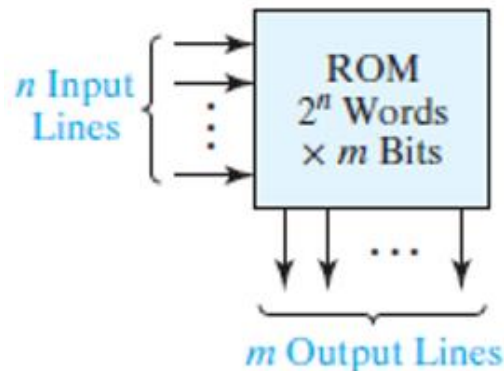
# Read-Only Memory

- A ROM with  $n$  input lines and  $m$  output lines contains
  - an array of  $2^n$  words
  - each word is  $m$  bits long.
- Input lines serve as address to select one of the  $2^n$  words
- When an input combination is applied to the ROM, the pattern of 0's and 1's stored in the corresponding word appears at the output lines
- A  $2^n \times m$  ROM can realize
  - $m$  functions
  - of  $n$  variables
  - because it can store a truth table with
    - $2^n$  rows and
    - $m$  columns



$n$ Input Variables	$m$ Output Variables
00 ... 00	100 ... 110
00 ... 01	010 ... 111
00 ... 10	101 ... 101
00 ... 11	110 ... 010
...	...
11 ... 00	001 ... 011
11 ... 01	110 ... 110
11 ... 10	011 ... 000
11 ... 11	111 ... 101

Typical Data Array Stored in ROM  
( $2^n$  words of  $m$  bits each)

- 64k  $\times$  8-bit ( $n = 16, m = 8$ )
- 512k  $\times$  16-bit ( $n = ?, m = ?$ )
- 32 word, 4-bit ROM ( $n = ?, m = ?$ )






# Read-Only Memory

## • Basic ROM Structure:

- A ROM essentially consists of a decoder and a memory array
- When a pattern of  $n$  0's and 1's is applied to the decoder inputs
  - Exactly one of the  $2^n$  decoder outputs is 1
  - This decoder output line selects one of the words in the memory array
  - The bit pattern stored in this word is transferred to the memory output lines

**FIGURE 9-23**  
Basic ROM  
Structure

© Cengage Learning 2014

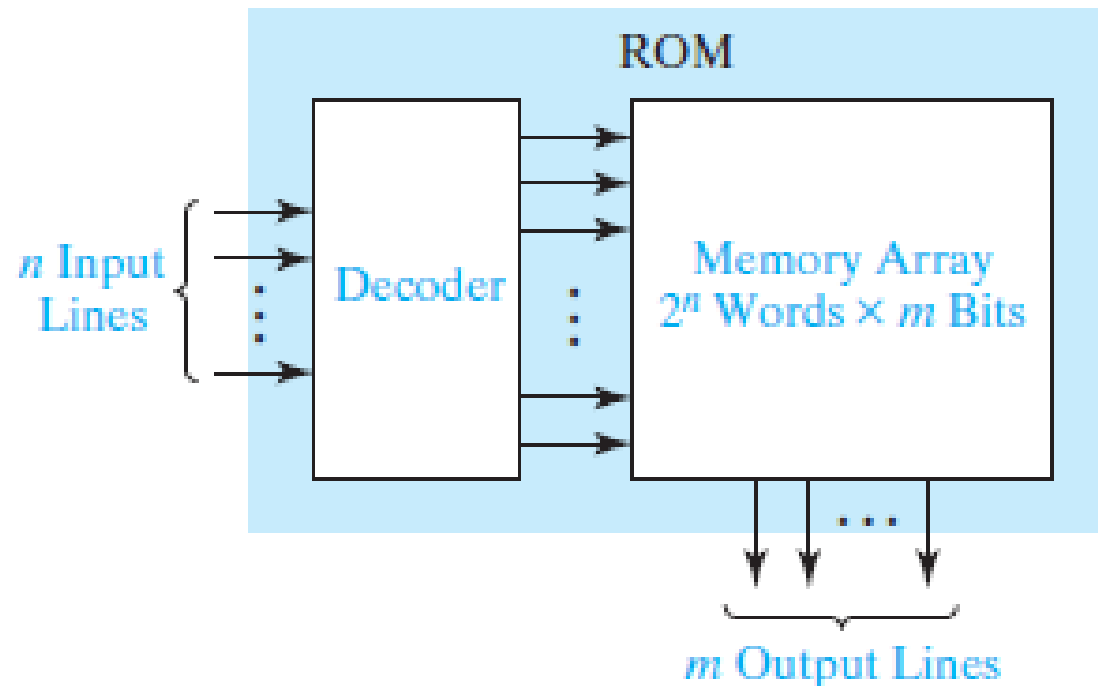



# Read-Only Memory

- One possible internal structure of an 8 Word  $\times$  4-bit ROM:

- Decoder generates minterms and selects based on input address


- Switching elements placed at intersections of **Word Lines** (minterm lines)

and **Output Lines** where a 1 is stored

- When any minterm that has a switching element attached is set to 1 a voltage  $A$  high is applied to that output line  $B$   $C$


- If no 1 is applied to an Output Line the **pull-down resistors** at top of array pull that Output Line to ground ( )

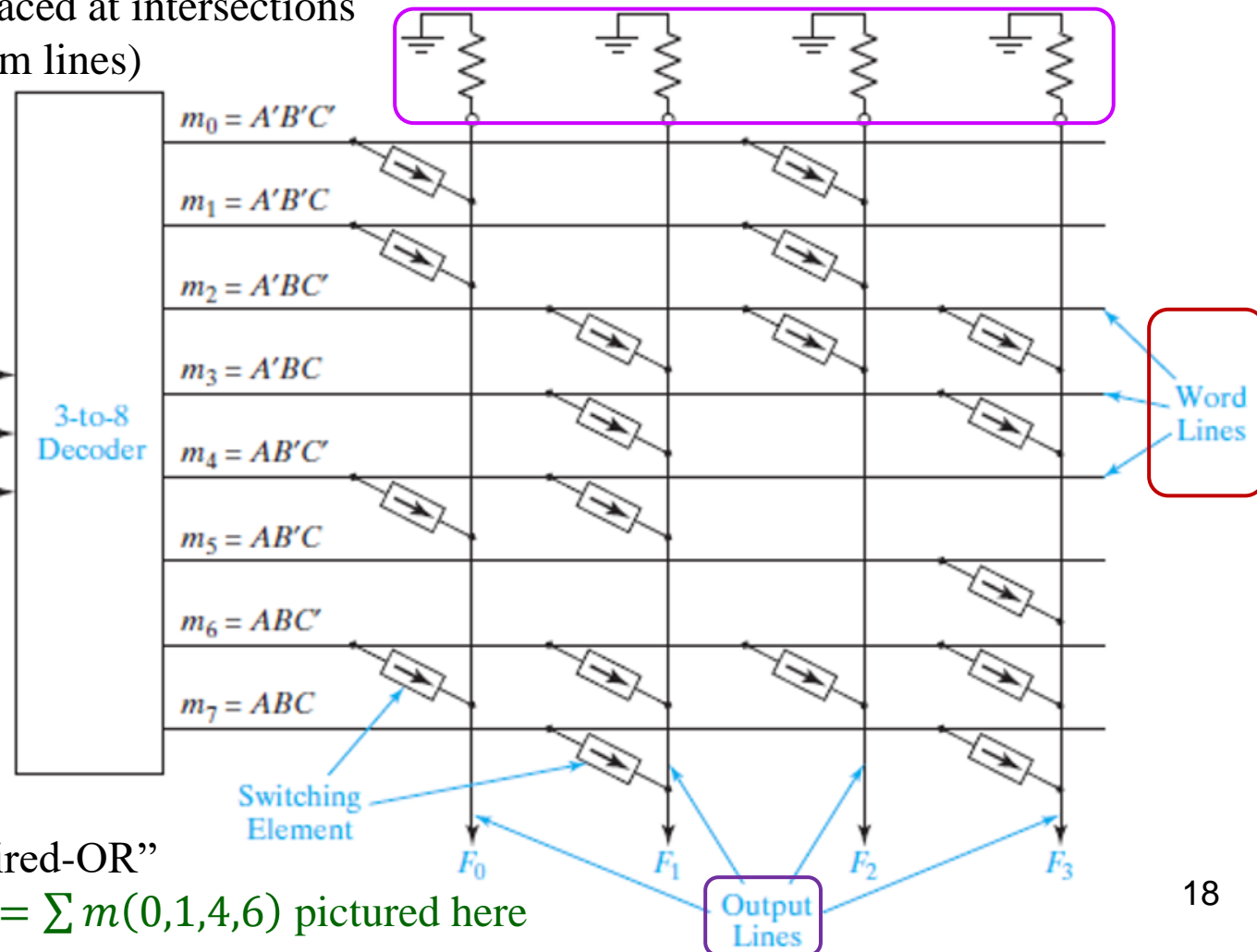- This implements a “wired-OR” gate. For example  $F_0 = \sum m(0,1,4,6)$  pictured here





## Read-Only Memory

 

- For this example, the four implemented functions are:

$$F_0 = \sum m(0, 1, 4, 6) = A'B' + AC'$$

$$F_1 = \sum m(2, 3, 4, 6, 7) = B + AC'$$

$$F_2 = \sum m(0, 1, 2, 6) = A'B' + BC'$$



$$F_3 = \sum m(2, 3, 5, 6, 7) = AC + B$$



# Read-Only Memory

  Example: ROM for seven-segment display driver



- Seven-segment display: an electronic display device for displaying decimal numerals
- Alternative to the more complex dot matrix displays
- Used in things such as digital clocks, electronic meters, basic calculators, etc.
  - Light up B and C → Displays a 1
  - Light up B, C, F and G → Displays a 4
  - Etc.
- Goal: ROM LUT for BCD to seven-segment driver








# Read-Only Memory

<i>W</i>	<i>X</i>	<i>Y</i>	<i>Z</i>	<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>E</i>	<i>F</i>	<i>G</i>
0	0	0	0							
0	0	0	1							
0	0	1	0							
0	0	1	1							
0	1	0	0							
0	1	0	1							
0	1	1	0							
0	1	1	1							
1	0	0	0							
1	0	0	1							

 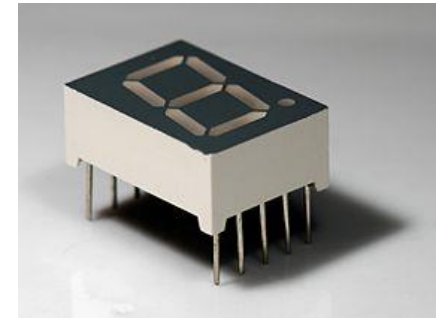



# Read-Only Memory

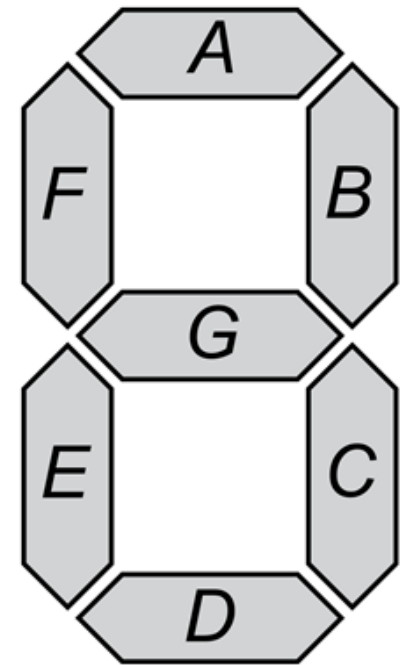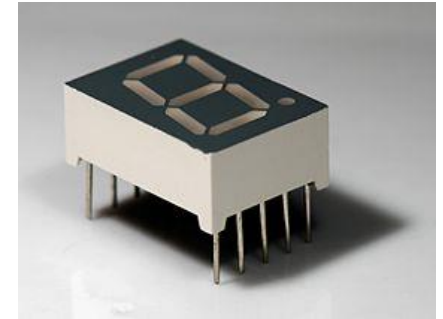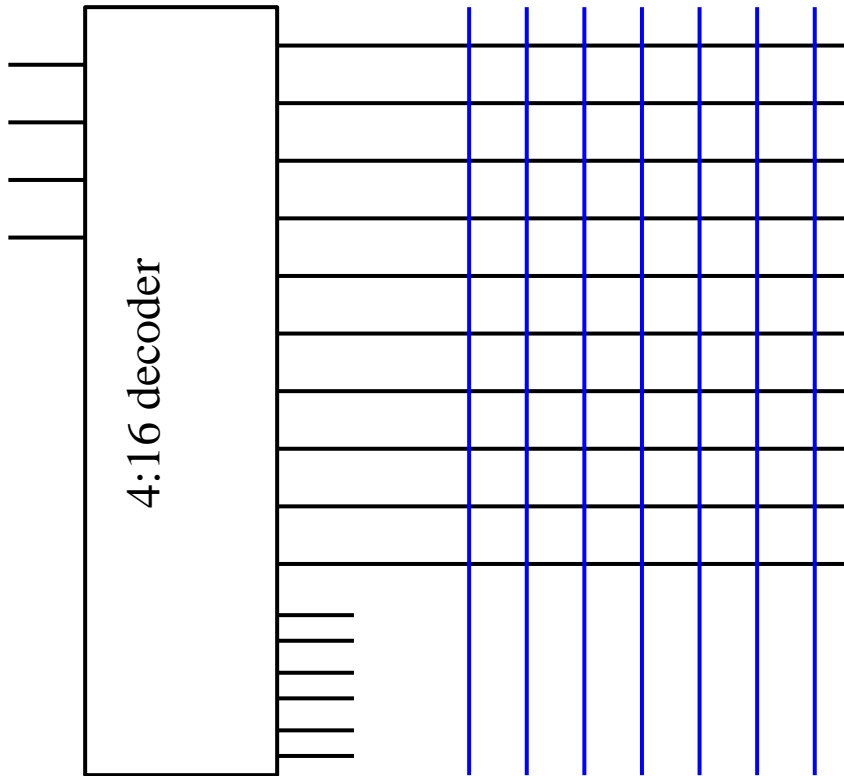



## Types of ROM (Non-volatile memory)

- **Standard ROM**

- Permanent
- Switches between word and output lines hardwired in
- Either the switch is there, or it is not
- Done at “Mask-level” during fabrication of IC

- **Programmable ROM (PROM)**

- Can electronically set the locations of the “on” switches
- **Once**

- **Electronically Erasable PROM (EEPROM)**

- Can electronically reprogram
- On order of 100 to 1000 times
- Uses a special type of FET for the switches
- Takes large voltages to erase/reprogram
- Limited number of times before FET fails