
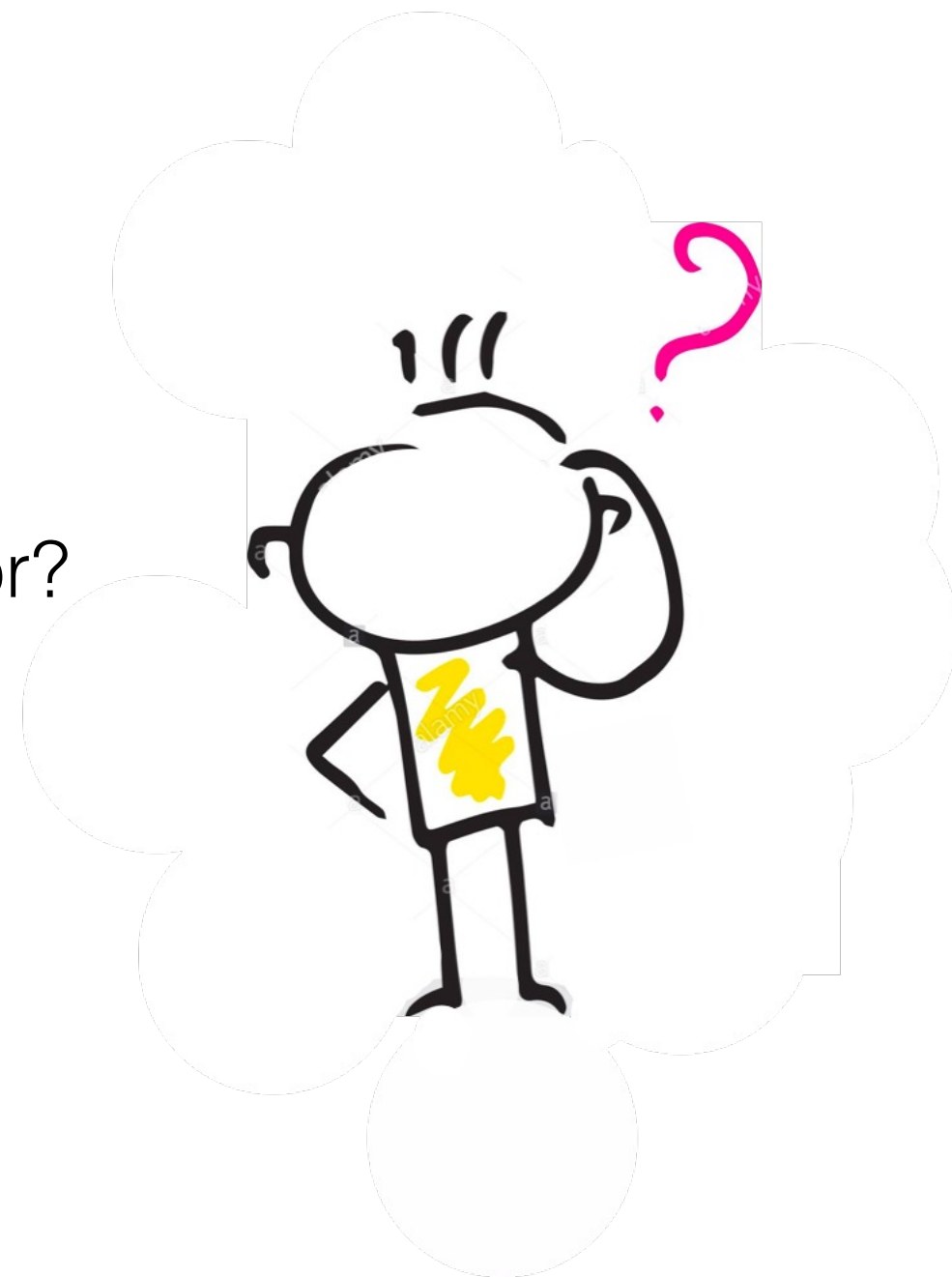


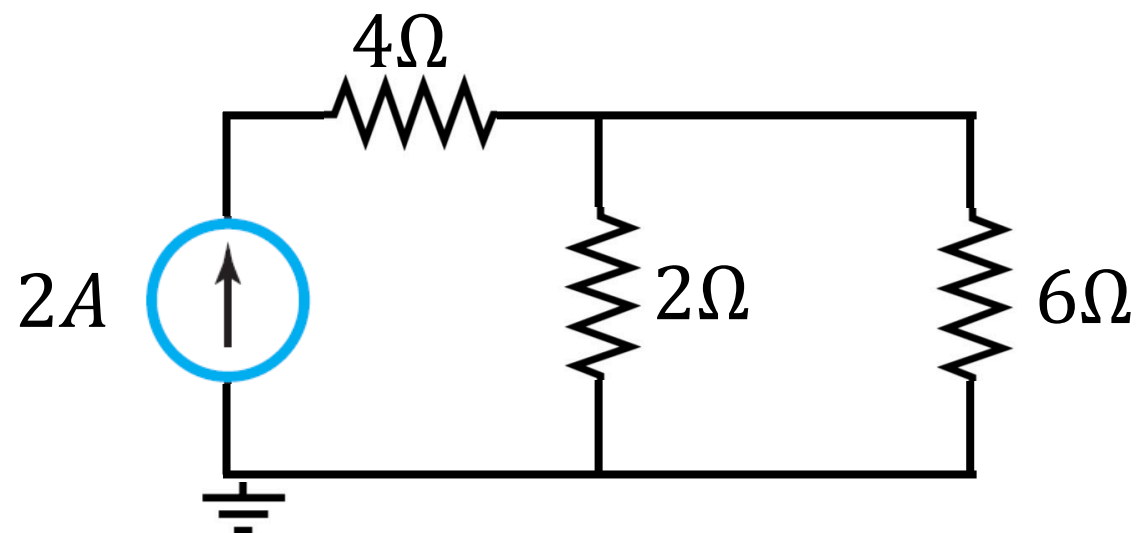

1. What is a voltage divider and what is a current divider?

2. What is the current across the 2Ω resistor?






THE OHIO STATE UNIVERSITY

COLLEGE OF ENGINEERING

Node Voltage Analysis




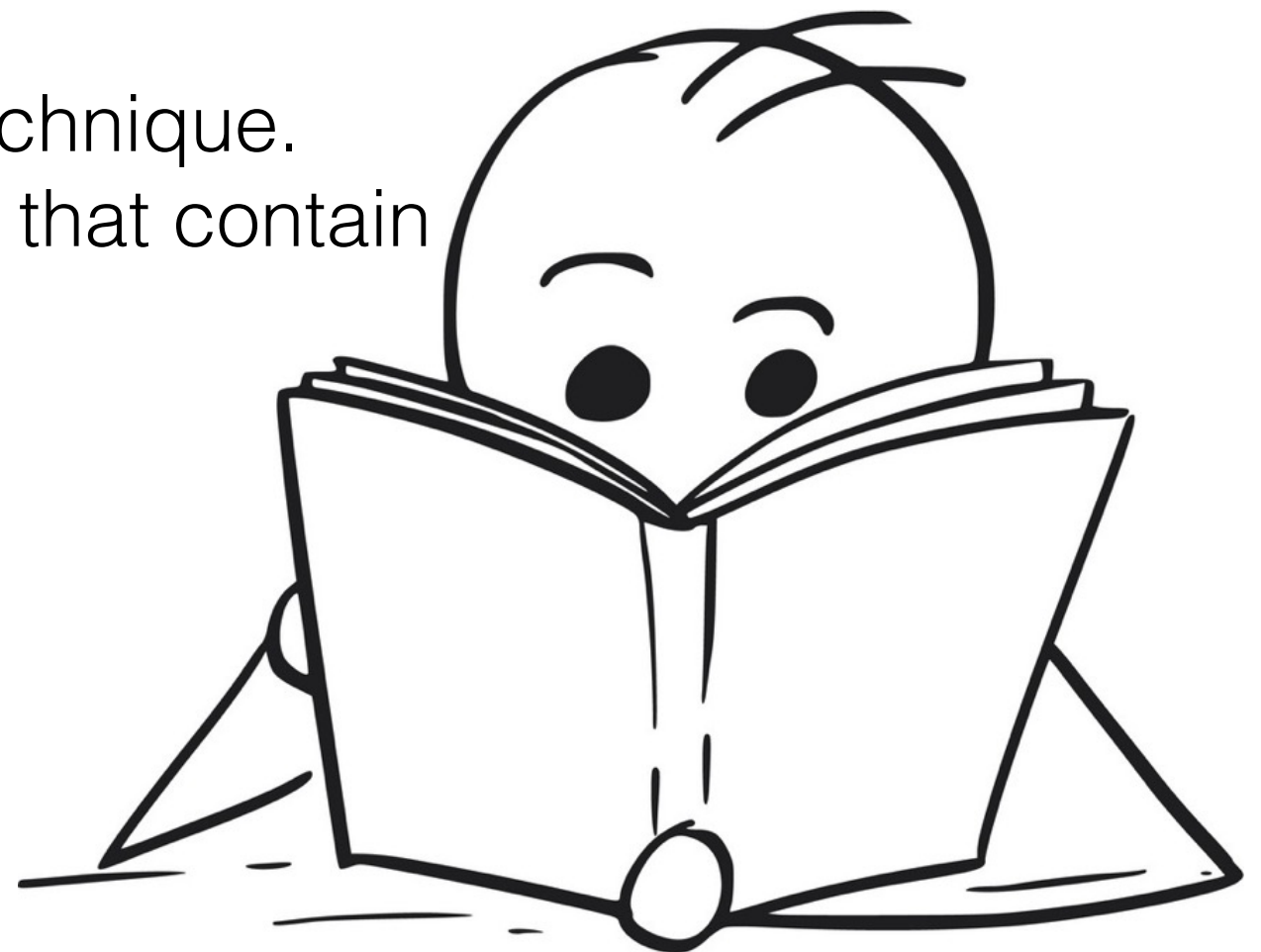
- Learning Objectives:
 - Apply the node-voltage analysis technique to linear electric circuits.
 - Identify a super-node.
 - Apply the node-voltage technique to analyze electric circuits that contain super-nodes.






Node Voltage Method

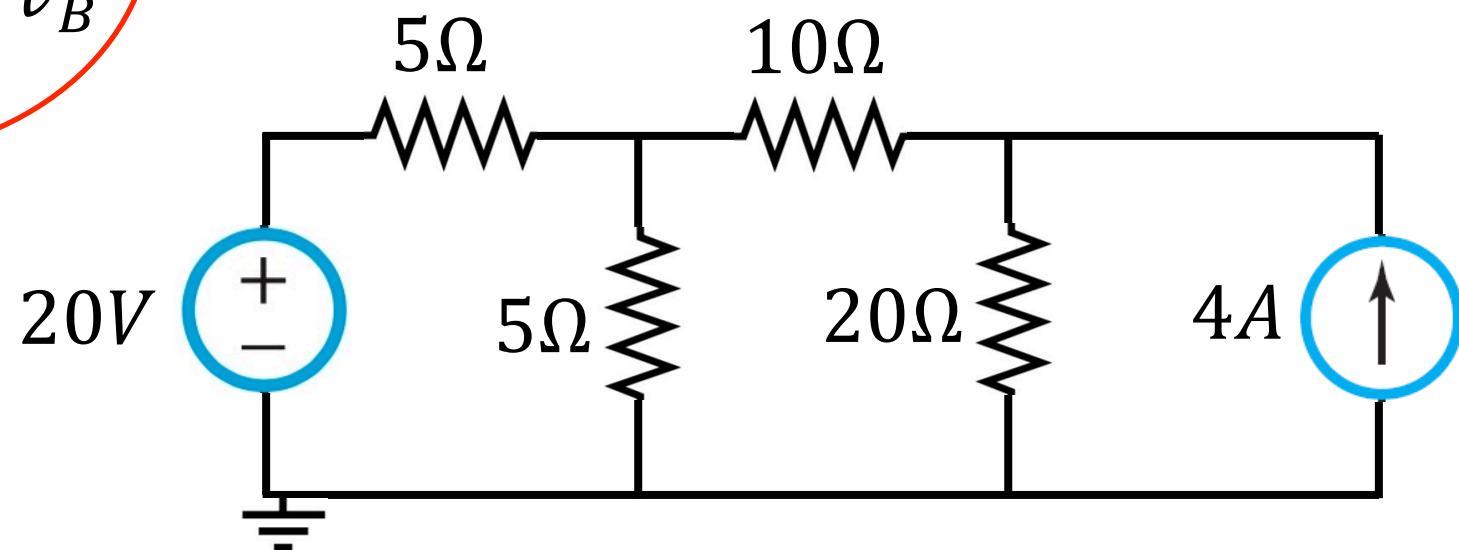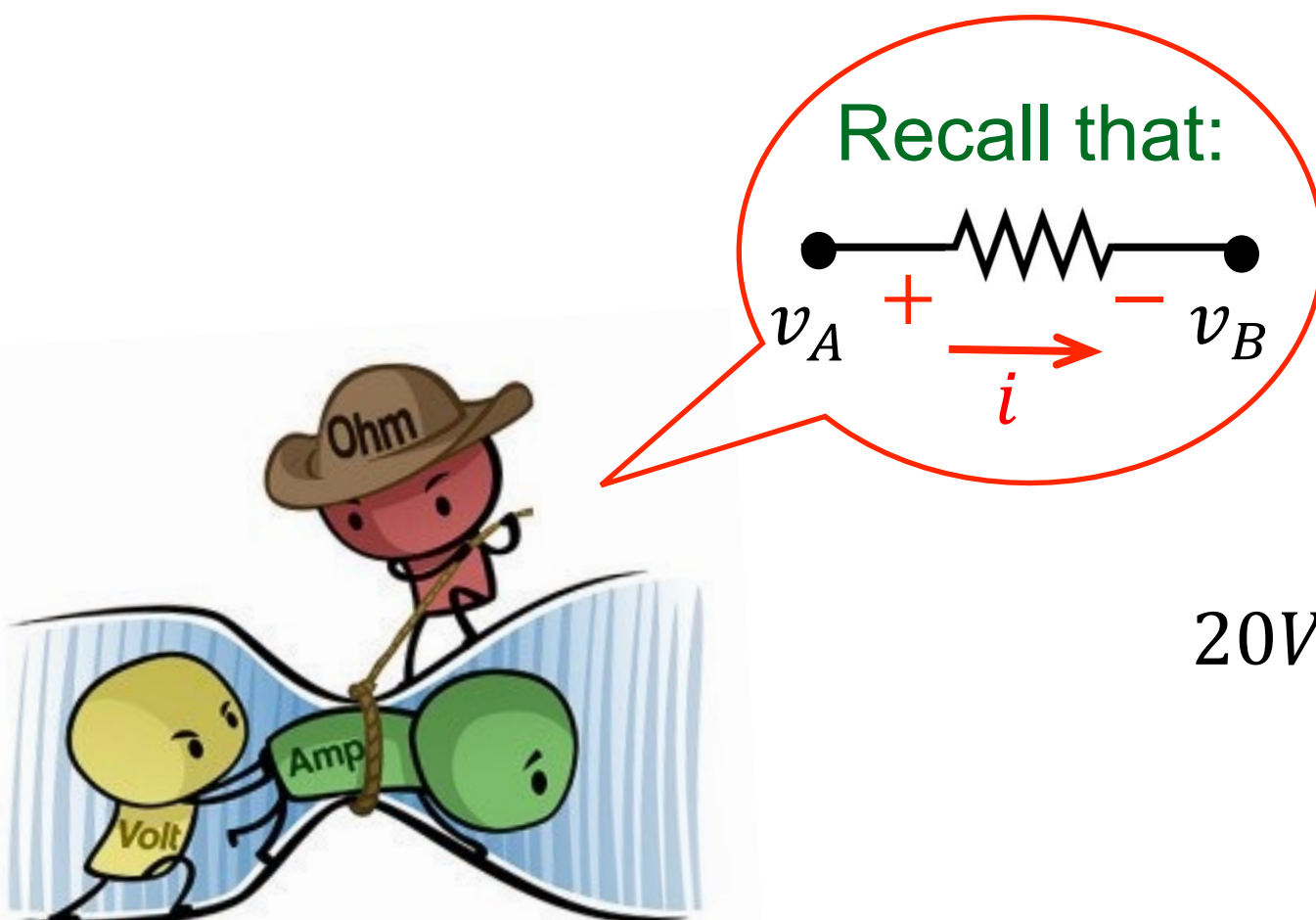1. Identify how many nodes there are and assign variables to each of them. Mainly used to solve for node voltages.
2. Select a reference node.
3. Identify if the voltage on any of the nodes is known.
4. Assume a direction for the current on each of the elements.






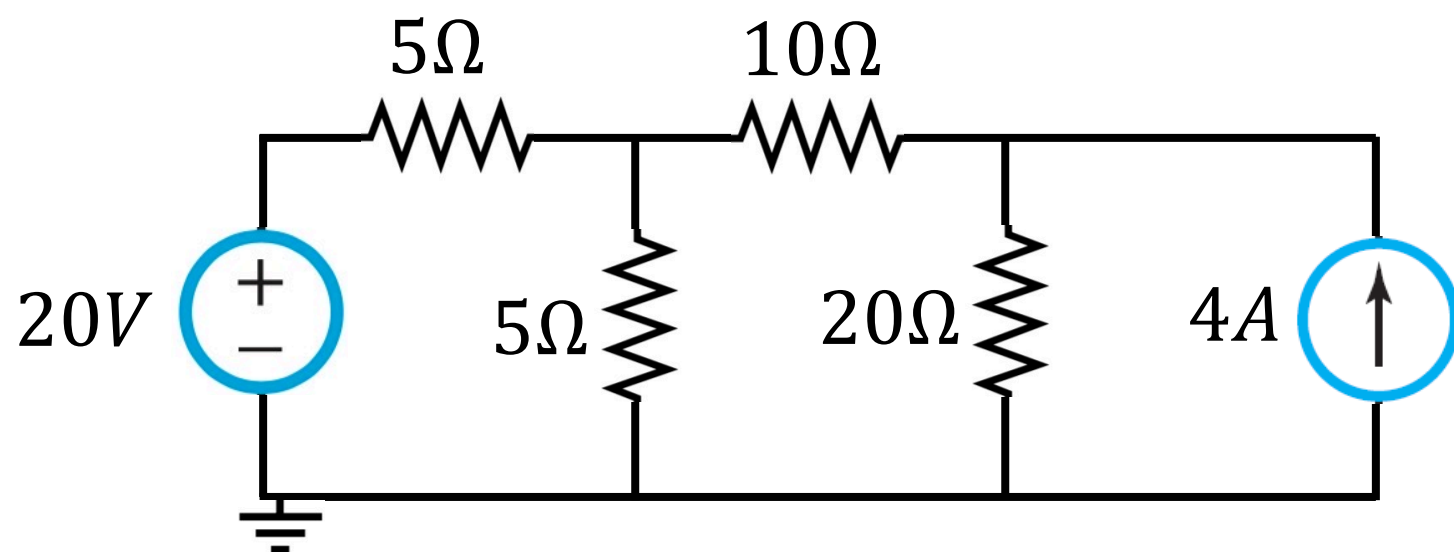1. Identify how many nodes there are and assign variables to each of them.
2. Select a reference node.
3. Identify if the voltage on any of the nodes is known.
4. Assume a direction for the current on each of the elements.
5. Apply KCL to all remaining nodes.
6. Solve.





- Non-grounded voltage source.

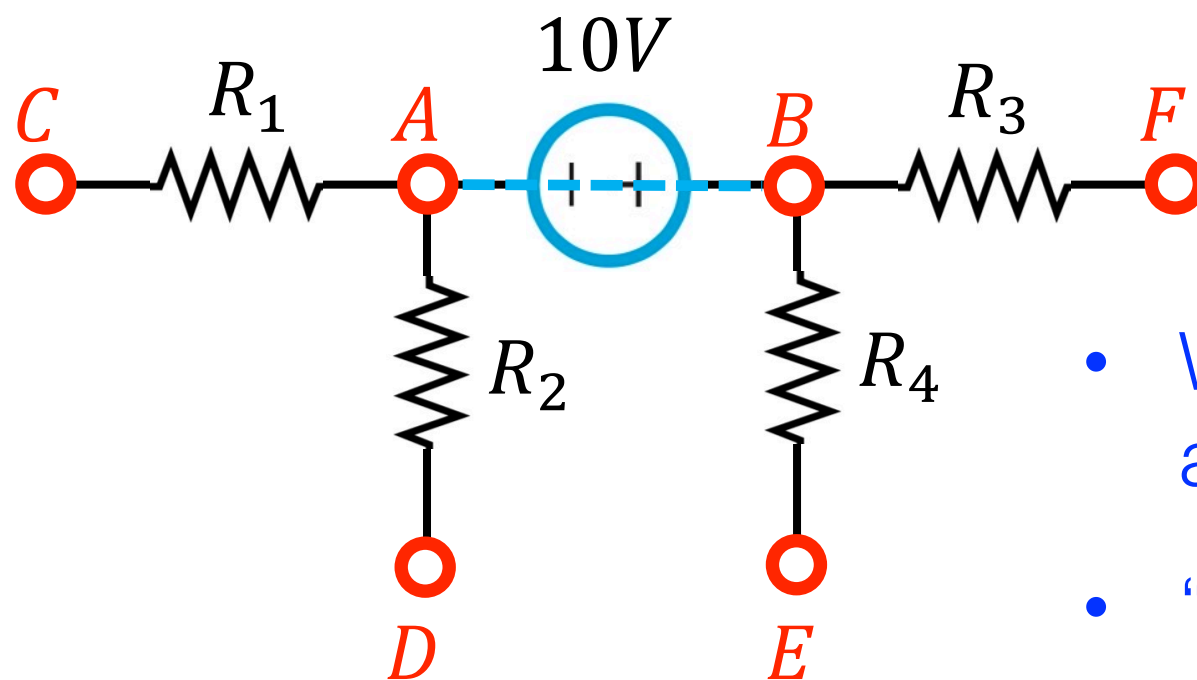

- We do not know the current flowing across the voltage source.
- “Remove the voltage source.”



Using node voltage analysis, find the voltage across R_4 .

