



THE OHIO STATE UNIVERSITY

COLLEGE OF ENGINEERING

s-Domain Circuit Analysis




- Learning Objectives:
 - Use the Laplace transform for circuit analysis.







s-Domain Circuit Analysis

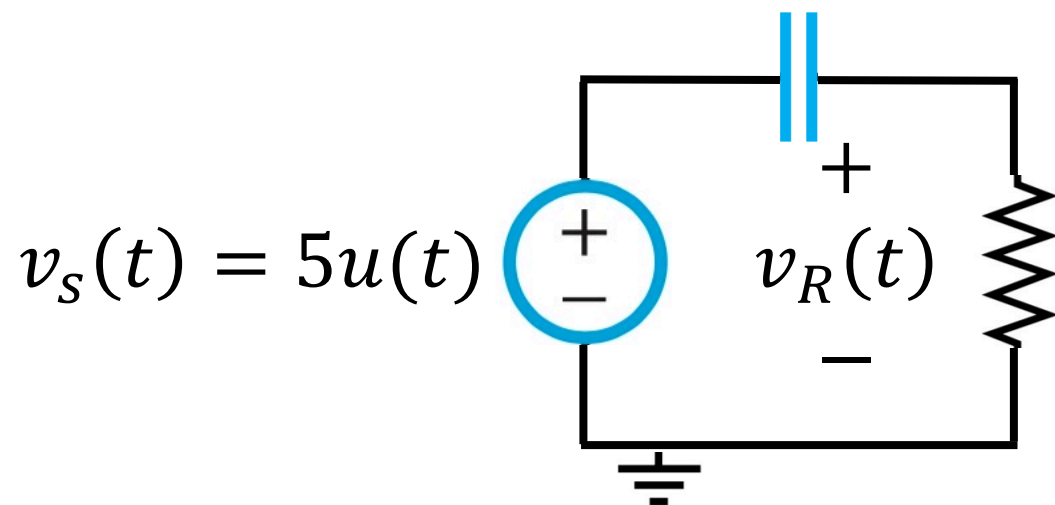

1. Calculate initial conditions.

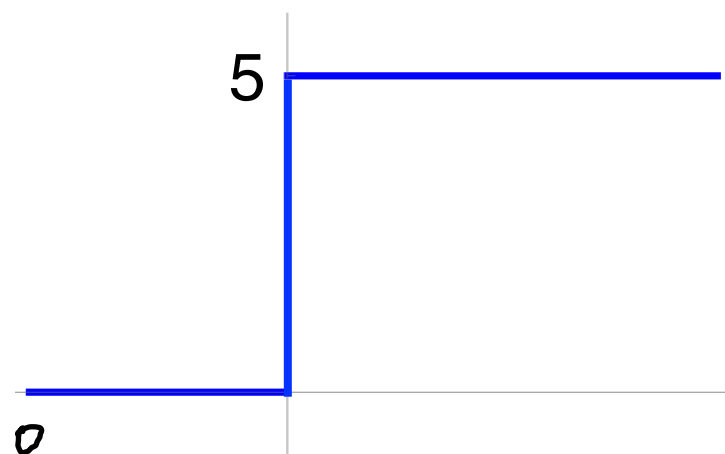

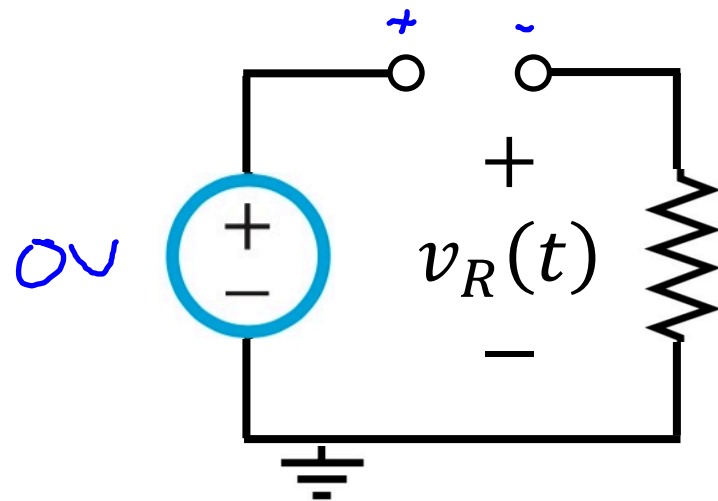

1. Calculate initial conditions.

$$V_C(0) = 0V$$


2. s-domain circuit.


$$t > 0$$

$$V_s(t) = 5u(t) \rightarrow V_s(s) = \frac{5}{s}$$

$$Z_R = R$$

Cap

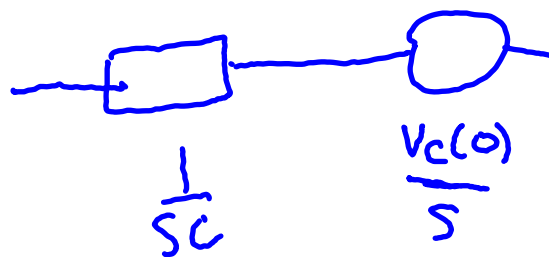

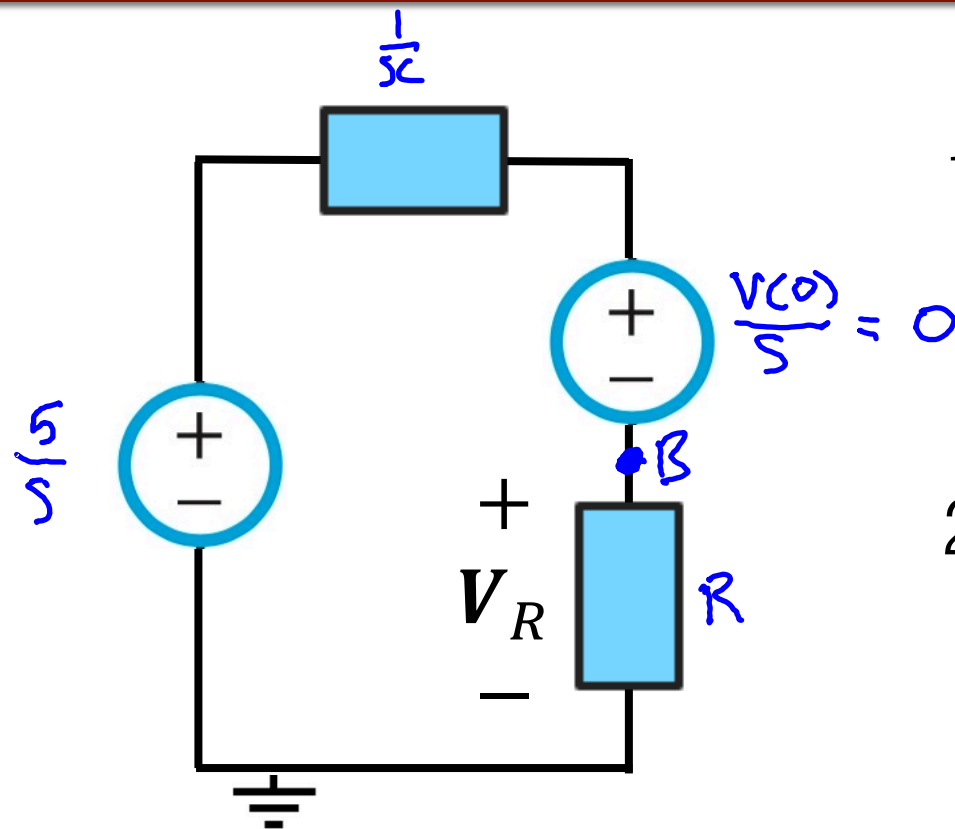

1. Calculate initial conditions.

2. s-domain circuit.


DC circuit

Voltage Division

$$V_R = \frac{R}{R + \frac{1}{sC}} \cdot \frac{5}{s}$$

Highest exponent
of s needs
a coefficient of 1
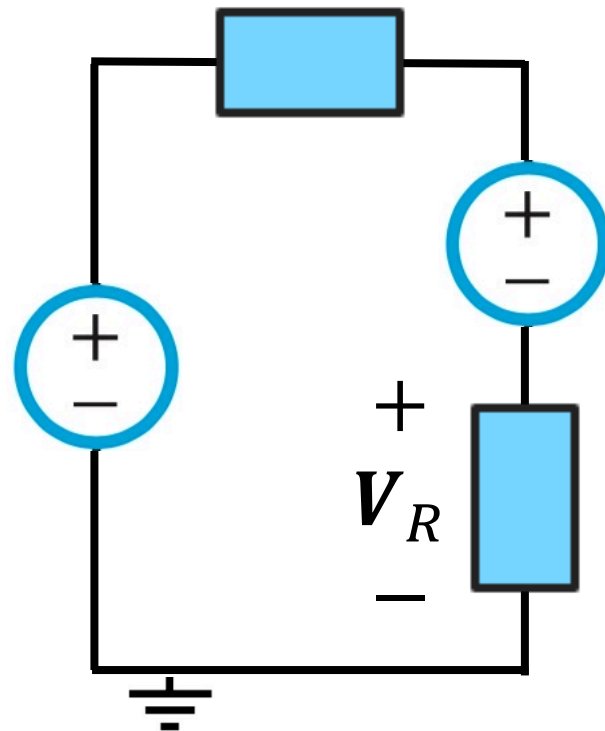
$$\begin{aligned} &= \frac{5R}{sR + \frac{1}{C}} \\ &= \frac{s}{s + \frac{1}{CR}} \end{aligned}$$



1. Calculate initial conditions.



2. s-domain circuit.

3. Go back to time domain.


1. $\delta(t)$	\longleftrightarrow	1
2. $u(t)$	\longleftrightarrow	$\frac{1}{s}$
3. t	\longleftrightarrow	$\frac{1}{s^2}$
4. t^n	\longleftrightarrow	$\frac{n!}{s^{n+1}}$
5. e^{-at}	\longleftrightarrow	$\frac{1}{s + a}$
6. te^{-at}	\longleftrightarrow	$\frac{1}{(s + a)^2}$
7. $t^n e^{-at}$	\longleftrightarrow	$\frac{n!}{(s + a)^{n+1}}$



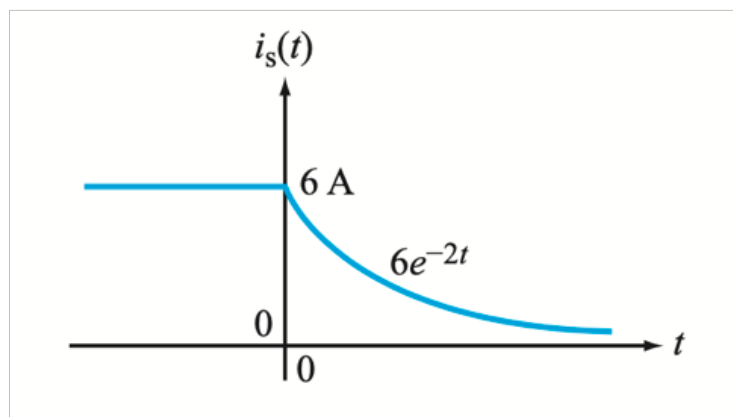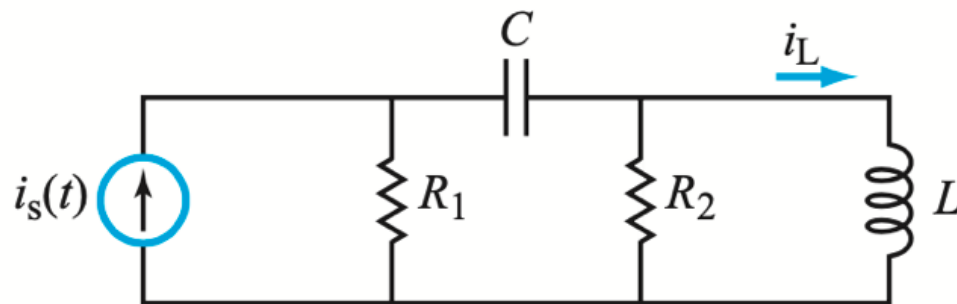Given the current-source waveform displayed below, determine $i_L(t)$ in the circuit, given that $R_1 = 10\Omega$, $R_2 = 5\Omega$, $L = 0.6196\text{H}$, and $LC = \left(\frac{1}{15}\right)\text{sec}$.



• initial condition $\neq 0$

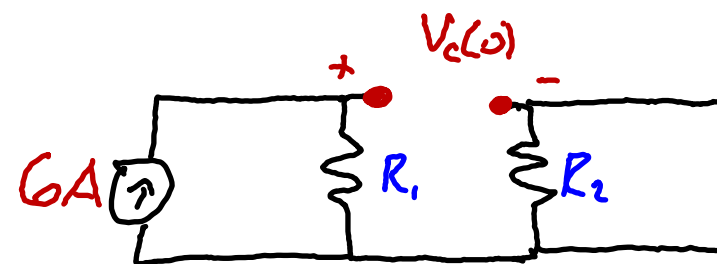


$$\begin{aligned} V_C(0) &= V_{R_1} \\ &= i_{R_1}(R_1) = 6(10) \\ &= 60\text{V} \end{aligned}$$

$$i_L(0) = 0\text{A}$$



• Move circuit to S-Domain

$$i_s(t) = 6e^{-2t} \Rightarrow I_s(s) = \frac{6}{s+2}$$

Capacitor

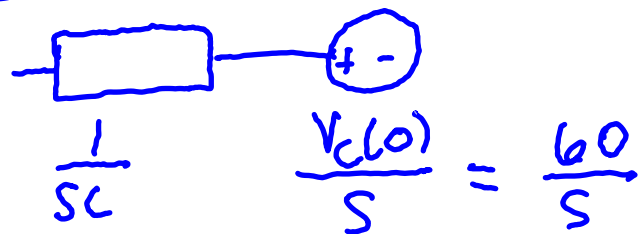

inductor

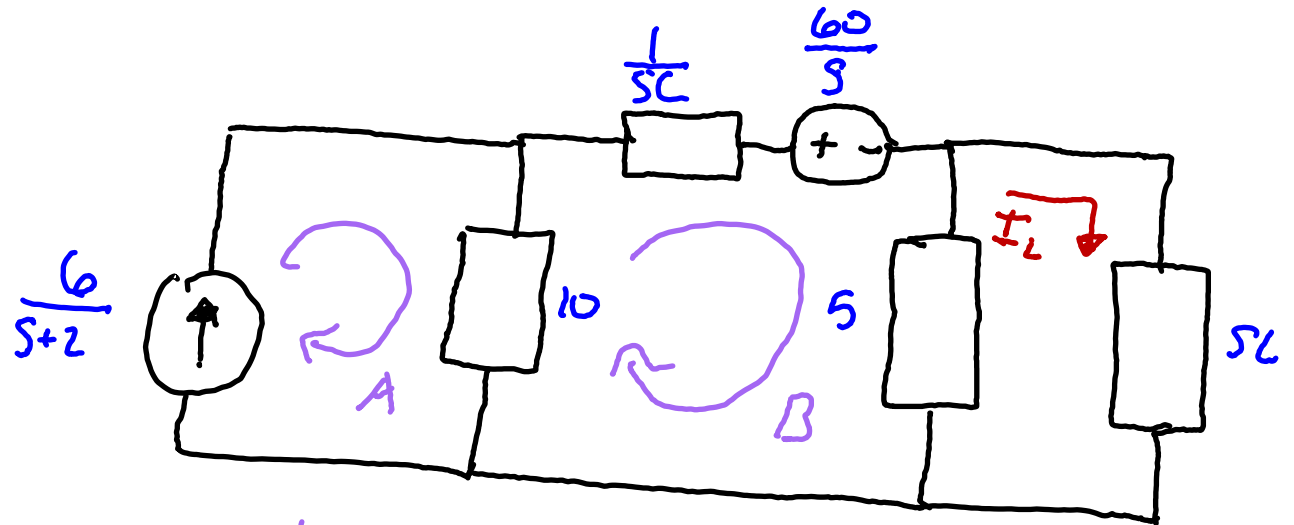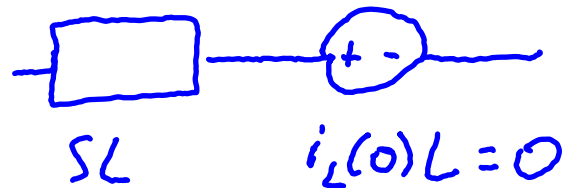

Mesh Current Analysis: $i_A = \frac{6}{s+2}$

KVL @ B:

$$V_{10} = V_{ZC} + \frac{60}{s} + V_5$$

$$10i_{10} = \frac{1}{sC}i_{ZC} + \frac{60}{s} + 5i_5$$

$$10\left(\frac{6}{s+2} - I_B\right) = \frac{1}{sC}I_B + \frac{60}{s} + 5(I_B - I_L)$$

$$\frac{60}{s+2} - \frac{60}{s} = I_B \left[\frac{1}{sC} + 5 + 10 \right] - 5I_L$$

$$\frac{60s - 60s - 120}{(s+2)s} = I_B \left[\frac{1}{sC} + 15 \right] - 5I_L \quad (1)$$

KVL @ L:

$$V_5 = V_{ZL}$$

$$5i_5 = sLi_L$$

$$5(I_B - I_L) = sLi_L$$

$$5I_B = I_L(sL + 5)$$

$$I_B = \frac{I_L(sL + 5)}{5} \quad (2)$$

② in ①

I'm not writing all that, just download the slides bro

$$= I_L [s^2 + 6s + 5]$$

$$= I_L (s+1)(s+5)$$

↓

$$I_L = \frac{-64.554}{(s+1)(s+2)(s+5)}$$