



Lecture 1 Outline

Reminders to self:

- ☐ Turn on lecture recording to Cloud
- ☐ Turn on Zoom microphone

- Last Lecture
 - Continued Boolean algebra – through XOR operation
- Today's Lecture
 - Continue Boolean algebra – resume at Distributive Law
 - Foundations for K-Maps
 - Minterms
 - Maxterms



Handouts and Announcements

- Announcements

- Homework Problems 2-3

- Posted on Carmen yesterday (1/24)
- Due in Carmen 11:59pm, Tuesday 1/31

- Homework Problems 2-1 and 2-2 reminder

- HW 2-1 due: 11:59pm Thursday 1/26
- HW 2-2 due: 11:25am Monday 1/30

- Participation Quizzes 1&2

- Quiz 1 available 11:10am today, Quiz 2 12:25pm today
- Due 24 hrs later, but available +24hrs with late penalty
- 15min time limit – clock starts when you start

- Read for Friday: Pages 123, 134-143



Boolean Algebra – Basic Laws

Distributive Law of Boolean Algebra:

- Ordinary Distributive Law:

- $X(Y + Z) = XY + XZ$

- Second Distributive Law (not valid for ordinary algebra)

- $X + YZ = (X + Y)(X + Z) = XX + XZ + XY + YZ = X + XZ + XY + YZ$

- This is the “dual” of the first distributive law

$$= X(1 + Z + Y) + YZ$$

- “Duality” concept satisfied in Boolean algebra

$$= X + YZ$$

- Given a Boolean algebra expression

- Interchange all constants 1 and 0
 - Interchange AND and OR operations
 - Variables and complements unchanged

- A more direct algebraic proof of the second distributive law is shown on page 45 of the textbook



Boolean Algebra – DeMorgan's Laws

Duality Examples:

- Interchange all constants 1 and 0
- Interchange AND and OR operations
- Variables and complements unchanged
- Examples:
 - $F = X + X' = 1 \Rightarrow \text{DUAL}(F) \rightarrow XX' = 0$ (Complementarity Laws)
 - $G = X + X = X \Rightarrow \text{DUAL}(G) \rightarrow XX = X$ (Idempotent Laws)
 - $H = X + 0 = X \Rightarrow \text{DUAL}(H) \rightarrow X \cdot 1 = X$ (Operations with 0 and 1)
 - $K = X + 1 = 1 \Rightarrow \text{DUAL}(K) \rightarrow X \cdot 0 = 0$ (Operations with 0 and 1)
 - $L = X + Y = Y + X \Rightarrow \text{DUAL}(L) \rightarrow XY = YX$ (Commutative Law)
 - OR & AND forms of Associative Law also related by duality
 - Distributive Laws by duality shown on previous slide



Boolean Algebra – DeMorgan's Law


DeMorgan's Law:

~~$$F = \overline{AB} \neq \bar{A}\bar{B}$$~~

~~$$F = \overline{A + B} \neq \bar{A} + \bar{B}$$~~

- The NOT operation isn't distributable by normal means
- Special rule \Rightarrow DeMorgan's Law to find the complement
 1. Take the DUAL
 2. Complement each literal
- First form of DeMorgan's Law: $\overline{X + Y} = \bar{X}\bar{Y}$
- Second form of DeMorgan's Law: $\overline{XY} = \bar{X} + \bar{Y}$
- Note: Two forms are duals of each other
- Truth table proof of DeMorgan's Laws:

X	Y	X'	Y'
0	0	1	1
0	1	1	0
1	0	0	1
1	1	0	0

 



Boolean Algebra – DeMorgan's Law

DeMorgan's Examples:

$$F = (A + \bar{B})(C + D)$$

Find \bar{F}

$$\bar{F} = \overline{(A + \bar{B})(C + D)} = \overline{(A + \bar{B})} + \overline{(C + D)} = \bar{A}B + \bar{C}\bar{D}$$

$$\bar{G} = A\bar{C}D + \bar{B}C$$

Find G

$$G = \bar{\bar{G}} = \overline{A\bar{C}D + \bar{B}C} = \overline{(A\bar{C}D)}\overline{(\bar{B}C)} = (\bar{A} + C + \bar{D})(B + \bar{C})$$



Boolean Algebra – Completeness

Functional Completeness:

- A set of logic operations is said to be functionally complete if any Boolean function can be expressed in terms of this set of operations
- The set {NOT, AND, OR} is functionally complete
- Similarly, the set {NOT, NAND, NOR} is functionally complete
- But OR can be realized using NOT & AND, etc. (use DeMorgan's - **Sketch**)
- Can implement any Boolean expression with just

- {NOT, AND}, or
- {NOT, OR}, or
- {NOT, NAND}, or
- {NOT, NOR}

- But a NAND gate (or NOR gate) with inputs tied together is a NOT
- Any Boolean expression can be implemented with just NAND gates (or just NOR gates)
(**Sketch OR using 2-input NAND**)





Boolean Algebra – Simplification

- Boolean algebra laws and theorems can be used to algebraically simplify expressions into forms that are more readily implemented with logic gates
- Theorems and algebraic techniques useful for simplification and proving validity are covered in greater depth in some sections of Chapters 2 and 3
- But we are going to learn a graphical technique for reducing Boolean Expressions
 - Karnaugh Maps
 - Often abbreviated K-Maps



Combinational Switching Circuit Design

Main steps

1. Find switching function that describes desired behavior
2. Find simplified Boolean algebraic expression
3. Realize simplified expression using available logic elements



Finding the switching function

- Logic design problems often stated in terms of one or more English sentences
- First step in designing logic circuit is to translate sentences into Boolean equations
 - Break down each sentence into phrases, and
 - Associate a Boolean variable with each phrase
- If a phrase can have a value of true or false, then we can represent that phrase by a Boolean variable
- Phrases can be
 - either true or false, or
 - have no truth value



Finding the switching function

Example

- Statement: *The alarm will ring iff the alarm switch is turned on and the door is not closed, or it is after 6 p.m. and the window is not closed.*
- Break into the following phrases with Boolean variables A , B , C , D and Z :

$\underbrace{\text{The alarm will ring}}_Z$ iff $\underbrace{\text{the alarm switch is on}}_A$ and
 $\underbrace{\text{the door is not closed}}_{B'}$ or $\underbrace{\text{it is after 6 P.M.}}_C$ and
 $\underbrace{\text{the window is not closed.}}_{D'}$

$A = 1$ if alarm switch is on

$B = 1$ if door is closed ($B' = 1$ if door NOT closed)


$C = 1$ if after 6pm

$D = 1$ if window is closed ($D' = 1$ if window NOT closed)




To the Logic Circuit

Example

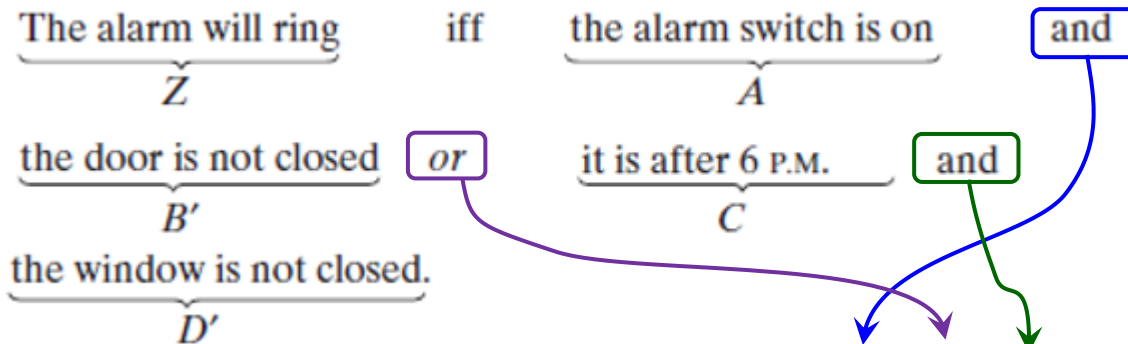

$$Z = AB' + CD'$$

 

$A = 1$ if alarm switch is on


$B = 1$ if door is closed

$C = 1$ if after 6pm

$D = 1$ if window is closed

- Already as simple as possible
- But could re-arrange if different gates available
- e.g. NAND

 
$$Z = A\bar{B} + C\bar{D} = \overline{\overline{A\bar{B}} + \overline{C\bar{D}}} = \overline{(\overline{A\bar{B}})(\overline{C\bar{D}})}$$






To the Logic Circuit

TI CD4011B – Quad 2 Input CMOS NAND

 

Pin 1

Pin 14

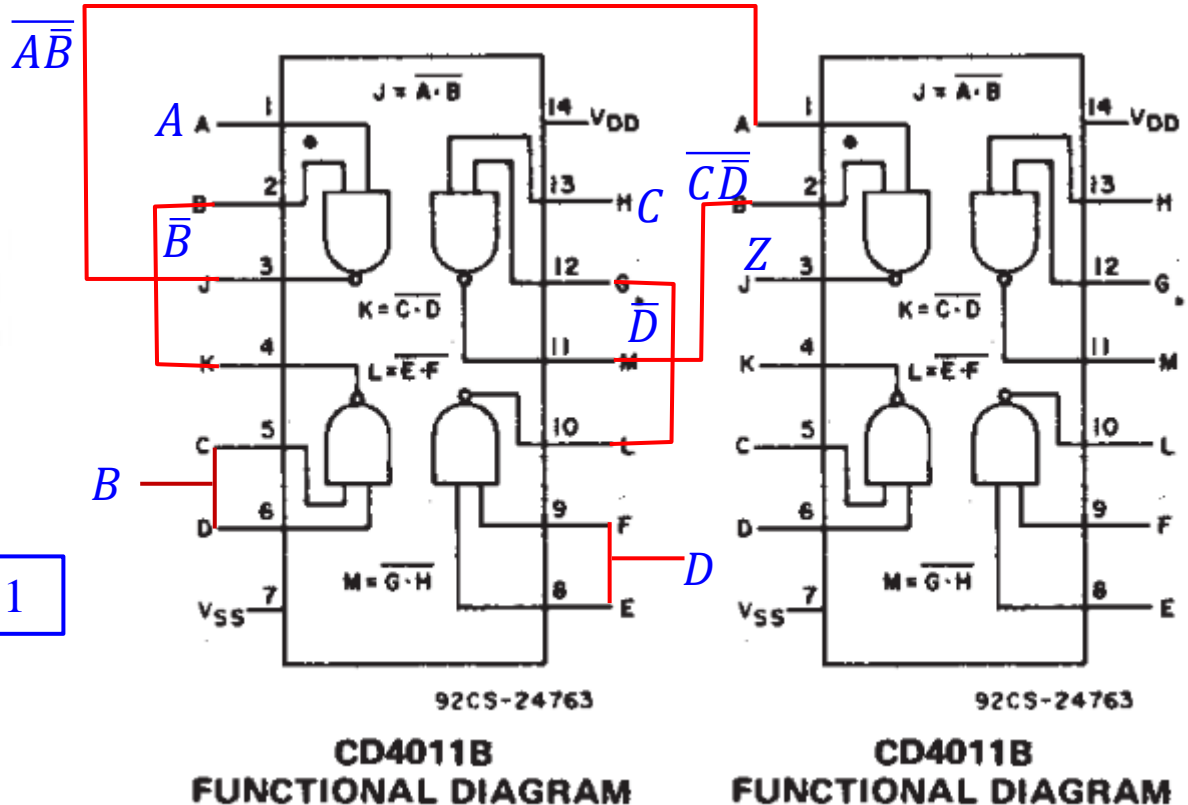




Logic Design via Truth Table

 Example: Consider a three-input, one output system where

- A, B, C are inputs that represent digits of binary number N , and
- f is the output such that
 - $f = 1$ if $N \geq 011_2$ and
 - $f = 0$ if $N < 011_2$



(a)


OR these to find
the expression that
yields $f = 1$

A	B	C	f	f'
0	0	0	0	1
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	1	0
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0

(b)



Logic Design via Truth Table

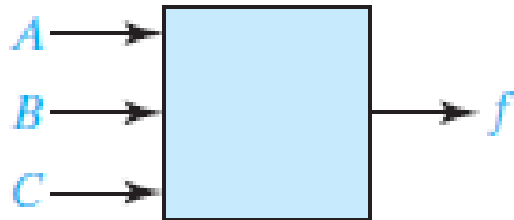


(a)

OR these to find
the expression that
yields $f = 1$

A	B	C	f	f'
0	0	0	0	1
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	1	0
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0

(b)

Sketch circuit

 

$$f = A'BC + AB'C' + AB'C + ABC' + ABC$$


$$f = A'BC + AB'(C' + C) + AB(C' + C)$$

$$\text{Can be simplified to } f = A'BC + \underset{1}{\underbrace{AB'(C' + C)}} + \underset{1}{\underbrace{AB(C' + C)}} = A'BC + A = A + BC$$

Elimination theorem



Logic Design via Truth Table

 

(a)

A	B	C	f	f'
0	0	0	0	1
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	1	0
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0

(b)

Alternatively, could write f' by OR-ing

$$f' = A'B'C' + A'B'C + A'BC'$$

Then use DeMorgan's to find f

Alternatively, could write f based on the 0's of the function

$$f = (A + B + C)(A + B + C')(A + B' + C)$$

Also simplifies to $f = A + BC$