

### Homework 01: Latches and Flip-Flops

Solve the **four** following problems. Show all your work/process. Please neatly write or type your answers, and please scan or upload your answers in a single PDF file to the assignment submission on Carmen. Answers may be graded for correctness, thoroughness, completion, or some combination.

**1.1** An  $XY$  latch has two inputs  $X$  and  $Y$ , and one state variable  $Q$ . It operates as follows:

- If  $X = Y$ , the latch state does not change ( $Q^+ = Q$ ).
- If  $X = 0$  and  $Y = 1$ , the latch state becomes 1 ( $Q^+ = 1$ ).
- If  $X = 1$  and  $Y = 0$ , the latch state becomes 0 ( $Q^+ = 0$ ).

- a. Construct the state table for this  $XY$  latch. Circle the stable states.
- b. Derive the characteristic equation (next-state equation) for this  $XY$  latch.
- c. Derive a circuit for this  $XY$  latch which has only four two-input NAND gates and two inverters. Draw the circuit.
- d. Are there any transitions between input combinations which might cause unreliable operation for this  $XY$  latch? If so, which transitions? Explain and verify your answer.
- e. In your circuit of part (c), is there a gate output which is usable as the complement of  $Q$ ? If so, which output? (You can label it on your circuit and refer to the label.) Explain and verify your answer.

**1.2** Figure 1 shows an  $AB$  latch circuit with two inputs  $A$  and  $B$ , one state variable  $Q$ , and another output  $P$ .


 


Figure 1:  $AB$  latch with state  $Q$  and output  $P$ .

- a. Derive the characteristic equation (next-state equation) for this  $AB$  latch. The equation should be in terms of only the present state  $Q$  and the inputs  $A$  and  $B$ .

- b. Construct the state table for this  $AB$  latch. Circle the stable states.
- c. Are there any transitions between input combinations which might cause unreliable operation for this  $AB$  latch? If so, which transitions? Explain and verify your answer.
- d. Is the output  $P$  usable as the complement of  $Q$ ? Explain and verify your answer.

**1.3** Figure 2 shows a gated latch circuit with gate signal  $G$ , two other inputs  $M$  and  $N$ , one state variable  $Q$ , another output  $P$ , and two labeled intermediate gate outputs  $A$  and  $B$ .

 

**Figure 2:** Gated latch with gate input  $G$ , other inputs  $M$  and  $N$ , intermediate outputs  $A$  and  $B$ , state  $Q$ , and output  $P$ .

- a. Construct a truth table for this circuit with every combination of values for  $G$ ,  $M$ ,  $N$ , and  $Q$ . Include columns for the intermediate outputs  $A$  and  $B$ , the output  $P$ , and the next state  $Q^+$ . From this truth table, construct a K-map and derive the next-state equation for this circuit. The equation should be in terms of only the present state  $Q$  and the inputs  $G$ ,  $M$ , and  $N$ .
- b. Is the output  $P$  usable as the complement of  $Q$ ? Verify your answer.
- c. For the Figure 2 circuit, assume that Gate 1 has a propagation delay of  $30\text{ ns}$  and Gates 2, 3, and 4 have propagation delays of  $10\text{ ns}$ . Construct a timing diagram for the circuit for the following situation:
  - Initial conditions at time  $0\text{ ns}$ :  $M = N = Q = 0, G = 1$
  - Input change at time  $10\text{ ns}$ :  $G$  changes from 1 to 0
 Show signals for  $G$ ,  $M$ ,  $N$ ,  $A$ ,  $B$ ,  $P$ , and  $Q$  on the timing diagram.
- d. Derive a circuit for this gated latch which has only four NAND gates (either two-input or three-input) and three inverters. Draw the circuit.

- 1.4 Complete the following timing diagram for the rising-edge-triggered D flip-flop shown in Figure 3. Assume  $Q$  begins at 1. Make sure any propagation delays are clear on your diagram.

 


Figure 3: Rising-edge-triggered controller-responder D flip-flop circuit.

