



# Lecture Outline

---

## Reminders to self:

- ☐ Turn on lecture recording to Cloud
- ☐ Turn on Zoom microphone

- Last Lecture

- Finish Limited Fan-in Design
- Started Multiple Output Logic Design

- Today's Lecture

- Continue Multiple Output Logic Design
  - Essential prime implicants and multiple-output circuits
  - Example with both limited fan-in and multiple-output (and NAND)
- Introduction to gate delays and timing diagrams
- Hazards in combinatorial logic



# Handouts and Announcements

---

- Announcements

- Homework Problems:

- 7-4 Posted on Carmen yesterday afternoon (2/9)
- 7-4 Due: 11:59pm Tuesday 2/14
- 8-1 Posted on Carmen this morning
- 8-1 Due: 11:59pm Thursday 2/16

- Homework Reminder: HW 7-3

- Posted on Carmen Tuesday (2/7)
- Due: 11:25am Monday 2/13

- Participation Quiz 6 opened at 11:15am today

- Read for Monday: pages 252, 260-268



- Announcements
  - ECE 2060 Laboratories
    - Start next week
    - You must attend your scheduled lab session
    - There are videos you are required to view prior to attending your first lab session
    - Refer to the Carmen pages for your lab section for details
    - Lab questions should be referred to Prof. Chapman and/or the GTA for your lab section



## Multiple Outputs

ECE2060

- Similar steps can sometimes help with multiple output design
- For multiple-output cases, some of the prime implicants essential to one function may not be essential to the multiple-output realization
- Prime implicants that are essential to the multiple-output realization must be included
- When checking 1s to see if they are covered by more than one prime implicant:
  - Look at the map of one of the functions
  - Check only the 1s that do not appear on the maps of other functions
  - Repeat for other functions
  - Can fail if there are more than two outputs, if there are no unique 1s
  - If you review the two 3-output examples from last lecture using this approach it fails to help – they were done by inspection and ingenuity
  - Next slide has a two-output example where this approach helps



## Essential Prime Implicants

## Multiple Outputs

$$f = a'b' + a'c'd$$


$$g = ad + bc'd$$

Individually: 6 gates  
14 inputs

Essential prime implicant for multiple-output realization

<i>ab</i> <i>cd</i>	00	01	11	10
00	<i>f</i>			
01	<i>f</i>	<i>f g</i>	<i>g</i>	<i>g</i>
11	<i>f</i>		<i>g</i>	<i>g</i>
10	<i>f</i>			
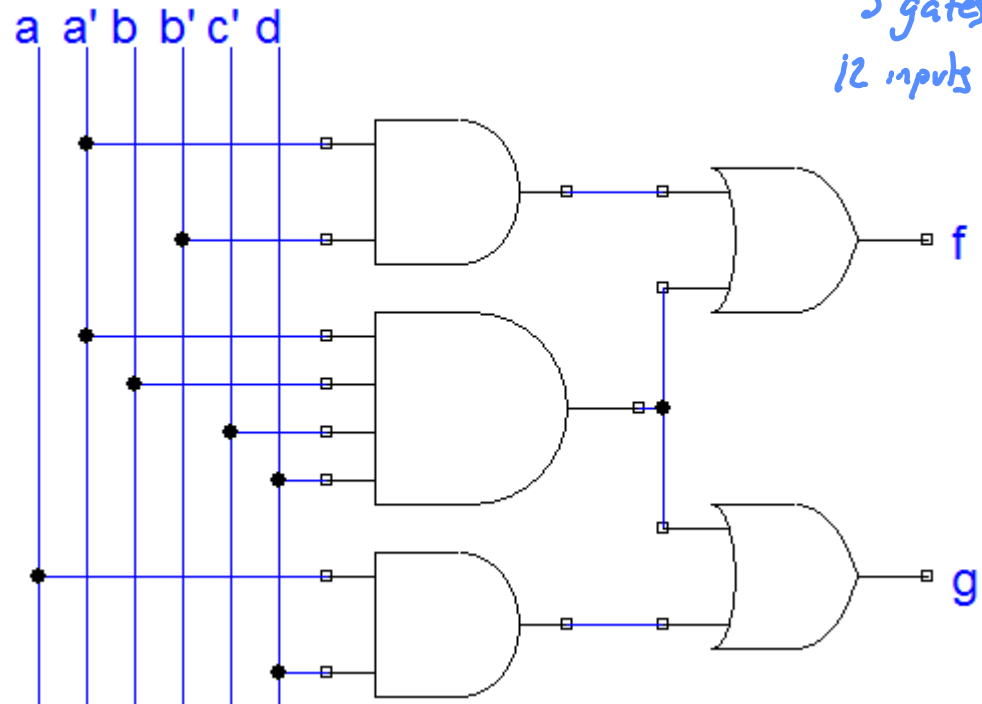
$$f = a'b' + a'b'c'd$$
$$g = ad + a'b'c'd$$





## Essential Prime Implicants

## Multiple Outputs

$$f = a'c' + acd'$$

$$g = bd + abc'$$

$$h = ac'd + abd' + acd'$$

Individually: 10 gates, 26 inputs

With re-use of  $acd'$ , 9 gates 23 inputs

$f$ : Essential for multiple-output realization

$ab \backslash cd$	00	01	11	10
00	$f$	$f$	$gh$	
01	$f$	$f_g$	$gh$	$h$
11		$g$	$g$	
10			$fh$	$fh$

$g$ : Essential for multiple-output realization

$h$ : Essential for multiple-output realization

$$f = a'c' + acd'$$

$$g = bd + abc'$$

$$h = ac'd + abc' + acd'$$

8 gates  
20 inputs



# Multiple Outputs and Limited Fan-in

ECE2060

---

- Techniques for multiple output design of 2-level circuits are not effective for more than two levels Factoring to make all gates meet fan-in limit often breaks up common terms
- Usually best to minimize each function individually
- Then factor to meet fan-in, trying to preserve or introduce common terms where possible



# Multiple Outputs and Limited Fan-in

ECE2060

## Example

Realize the functions given in Figure 8-2, using only **two-input NAND** gates and inverters. If we minimize each function separately, the result is


$$f_1 = b'c' + ab' + a'b$$

$$f_2 = b'c' + bc + a'b$$


$$f_3 = a'b'c + ab + bc'$$

**FIGURE 8-2**


© Cengage Learning  
2014

 

$$f_1 = \Sigma m(0, 2, 3, 4, 5)$$

 

$$f_2 = \Sigma m(0, 2, 3, 4, 7)$$

 

$$f_3 = \Sigma m(1, 2, 6, 7)$$

Each function requires a 3-input OR  $\rightarrow$  factor to reduce inputs





## Multiple Outputs and Limited Fan-in

ECE2060

$$f_1 = b'c' + ab' + a'b = b'(a + c') + a'b$$



*Common 2-input AND*

$$f_3 = a'b'c + ab + bc' = a'b'c + b(a + c')$$

*Common 2-input OR*

$$f_2 = b'c' + bc + a'b = b(a' + c) + b'c' \text{ or } = (b' + c)(b + c') + a'b$$
$$a'b'c = a'(b'c) = a'(b + c)'$$

  *Last step by DeMorgan's* *Common 2-input OR*



Convert to NAND



## Gate Delays and Timing Diagrams


---

- When the input to a logic gate is changed, the output will not change instantaneously
- Transistors or other switching elements within gate take finite time to react to a change in input
- The change in the gate output is delayed with respect to the input change
- Timing diagrams are frequently used in the analysis of sequential circuits
- These diagrams show various signals in the circuit as a function of time



 
# Gate Delays and Timing Diagrams

- Speed of a digital system is an important measure of performance
- Speed of basic logic inverter used to implement system is a core factor in that speed
- Characterized by time required for inverter to respond to change at its input



First consider response to ideal input pulse

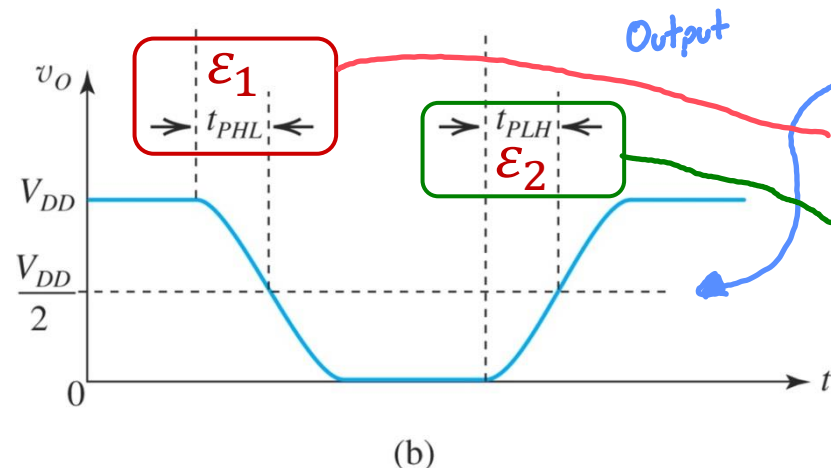- Output has rounded edges due to finite rise and fall time for charging internal capacitances
- Corresponding delay between each edge of input pulse and change in state of output of inverter



- Switching point defined by time output pulse passes halfway point of its change

•  $t_{PHL} = \epsilon_1 \equiv$  propagation delay: high  $\rightarrow$  low

•  $t_{PLH} = \epsilon_2$


• In general  $\epsilon_1 \neq \epsilon_2$

• For IC gates the propagation delays may be as short as  $1 \text{ ns} = 10^{-9} \text{ s}$


 
# Gate Delays and Timing Diagrams

- Actual input is not an ideal pulse
- Formal definition of propagation delays defined based on 50% points of both input and output



- Rise- and fall- times at the input defined based on transitions between 10% and 90% levels

- Transition times at output also defined based on 10% and 90% levels



# Gate Delays and Timing Diagrams

- This figure shows idealized timing diagram for circuit with two gates, assuming propagation delay of  $20\text{ ns}$

- Idealized in that rise and fall times assumed negligibly short

( compared to propagation delay )


- Vertical transitions ( infinite slope )

- This timing diagram indicates what happens when


- Inputs  $B$  and  $C$  are held at constant values 1 and 0 respectively, and

- Input  $A$  is changed to 1 at  $t = 40\text{ ns}$ , and

 - Changed back to 0 at  $t = 100\text{ ns}$



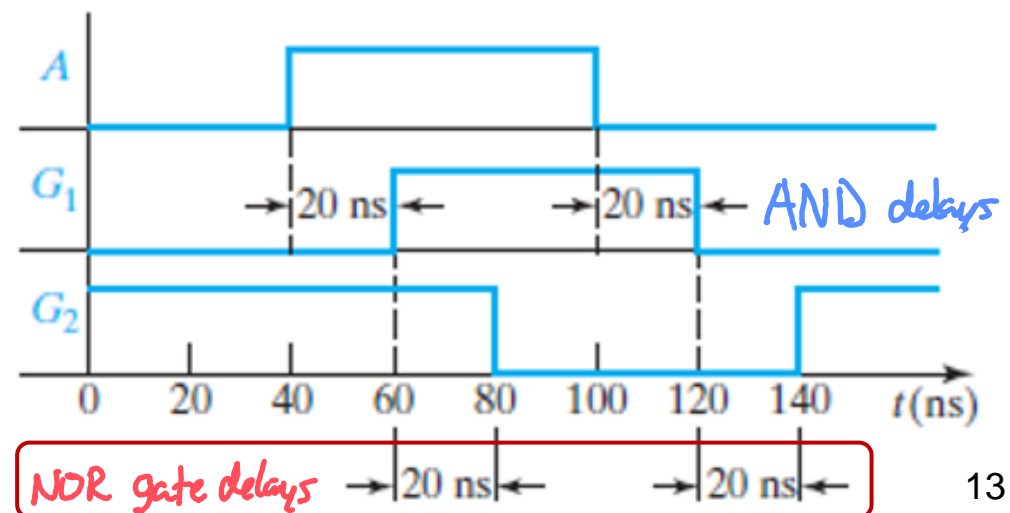$G_2$  responds 40 ns after  $A$  changes






# Gate Delays and Timing Diagrams

- **Effect of different arrival time of inputs to a gate**
  - 1  $\mu\text{s}$  delay element in one of the input lines
  - Two input pulses: 2  $\mu\text{s}$  and 3  $\mu\text{s}$ , separated by 3  $\mu\text{s}$
  - All transitions at input Y delayed 1  $\mu\text{s}$  relative to input X
- **Note that output pulse is not merely delayed by  $\epsilon$** 
  - AND gate  $\Rightarrow$  both inputs must be high for the output to be high
  - Duration of the output pulses is also shortened by 1  $\mu\text{s}$


FIGURE 8-6 Timing Diagram for Circuit with Delay

 

If timing effects are severe an expected output pulse could disappear!




# Another Gate-Delay Example

 

Assume

Inverter: 5 ns delay


Gates: 10 ns delay

 


 
# Hazards in Combinational Logic


- Switching transients occur when different paths from input to output have different propagation delays
  - A circuit output may momentarily go to 0 when it should remain a constant 1, we say that the circuit has a
  - If the output may momentarily go to 1 when it should remain a 0, we say that the circuit has a
  - If, when the output is supposed to change from 0 to 1 (or 1 to 0), the output may change three or more times, we say that the circuit has a
    - In all 3 cases, final steady-state outputs are correct
    - Transient errors before steady-state is reached



(a) Static 1-hazard



(b) Static 0-hazard

 

(c) Dynamic hazards







# Hazards in Combinational Logic
  
## Static 1 hazard

- Let  $A = C = 1$
- Then  $F = B' + B = 1$
- $F$  should remain 1 if  $B$  changes from 1 to 0
- But consider 10 ns propagation delays
  - 20 ns for  $D$  to change
  - Only 10 ns for  $E$  to change
  - Static 1 hazard at  $F$







# Hazards in Combinational Logic
  
## Static 1 hazard

- Let  $A = C = 1$
- Then  $F = B' + B = 1$
- Note that changing  $B$  from 0 to 1 doesn't cause a similar glitch
  - In this case the timing difference causes an overlap of when
  - Since they are inputs to an OR gate
- No glitch for one direction of change doesn't imply no glitch for the other direction of change






# Hazards in Combinational Logic
 
## Static 1 hazard

- $F = AB' + BC$
- Hazard happened when
- Any “1” not in the same “Prime Implicant” ( )
- leaves open a potential static 1 hazard
- To fix: add a loop that
- $F = AB' + BC$



		A	
		0	1
BC	00	0	1
	01	0	1
	11	1	1
	10	0	0

1-hazard

- Hazard removed by adding redundant logic
- Still SOP
- But no longer minimum SOP



# Hazards in Combinational Logic

## Static 0 hazard

- POS: circle the zeros
- $\bar{F} = A'B' + BC'$
- $F = \overline{A'B' + BC'} = (\overline{A'B'})(\overline{BC'}) = (A + B)(B' + C)$
- Potential static zero hazard for change of  $B$
- Add loop for  $A'C'$  to remove the static zero risk
- $F = (A + B)(B' + C)(A + C)$

		$A$	
		0	1
$BC$	00	0	1
	01	0	1
	11	1	1
	10	0	0



## Dynamic hazards

- Harder to identify
- Occur when multiple paths exist from input  $\Rightarrow$  output with different delays
- If ALL static hazards are resolved, then Dynamic Hazards no longer exist (but see the next slide)





## Hazards in Combinational Logic

---

- In our work on hazards we only considered 1 input changing at a time
- This is not always true
- Almost all circuits will have hazards if more than one input changes at a time
- They cannot all be eliminated by simply adding redundancy
- Glitches are of most importance in asynchronous sequential circuits
- The internal construction of latches and flip-flops we will learn later this semester are important examples of asynchronous sequential circuits
- But we will then see how to employ flip-flops in synchronous circuits
  - Included a clock signal to keep things synchronized
  - Take outputs to be valid only at specific times in clock cycle
  - Design circuit to ignore glitches from hazards at other times



# ECE2060 Timing Chart Example

  

Propagation delays for this example:

- Inverters: 5 ns
- 2-input gates: 10 ns
- 3-input gates: 15 ns

Vertical lines in timing diagram indicate 5 ns increments in time