




A current source in a linear circuit has $i = 15 \cos(25\pi t + 25)$

A. What is the amplitude of the current? $A = 15$

B. What is the angular frequency? $\omega = 25\pi$

C. Find the frequency of the current. $f = \frac{\omega}{2\pi} = 12.5 \text{ Hz}$

D. What is the phase? $\phi = 25^\circ$

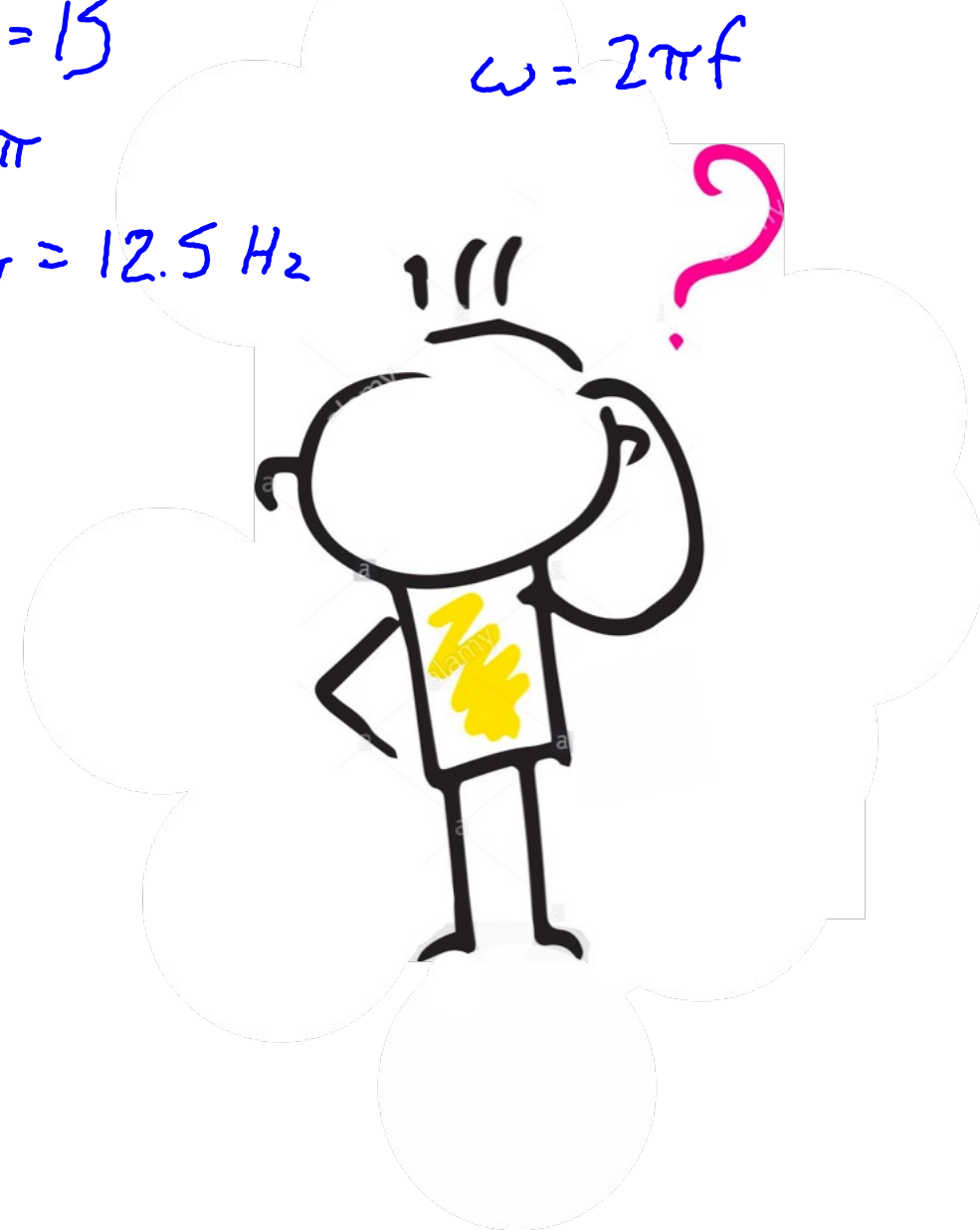



THE OHIO STATE UNIVERSITY

COLLEGE OF ENGINEERING

Phasor Domain




- Learning Objectives:
 - Transform time-varying sinusoidal functions to the phasor domain and vice versa.





On time domain:

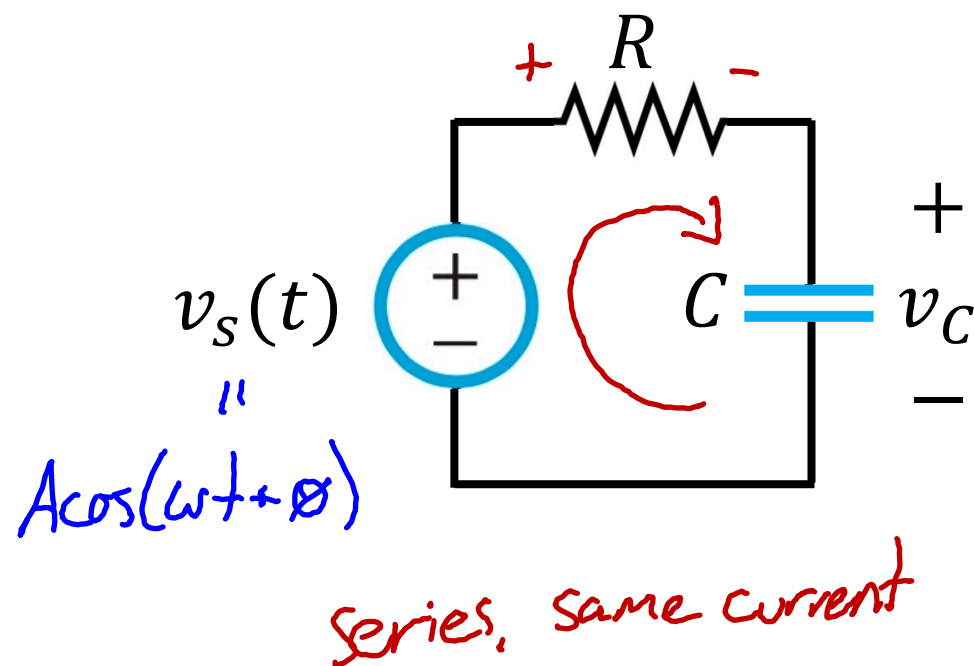- AC circuit with capacitors or inductors challenging
 - i-v relationships are time dependent



$$i_C(t) = C \cdot \frac{dv_C(t)}{dt} = i_R$$

KVL


$$A\cos(\omega t + \phi) = V_R + V_C(t)$$

$$A\cos(\omega t + \phi) = R \cdot i_R + V_C(t)$$

$$A\cos(\omega t + \phi) = RC \frac{dV_C(t)}{dt} + V_C(t)$$



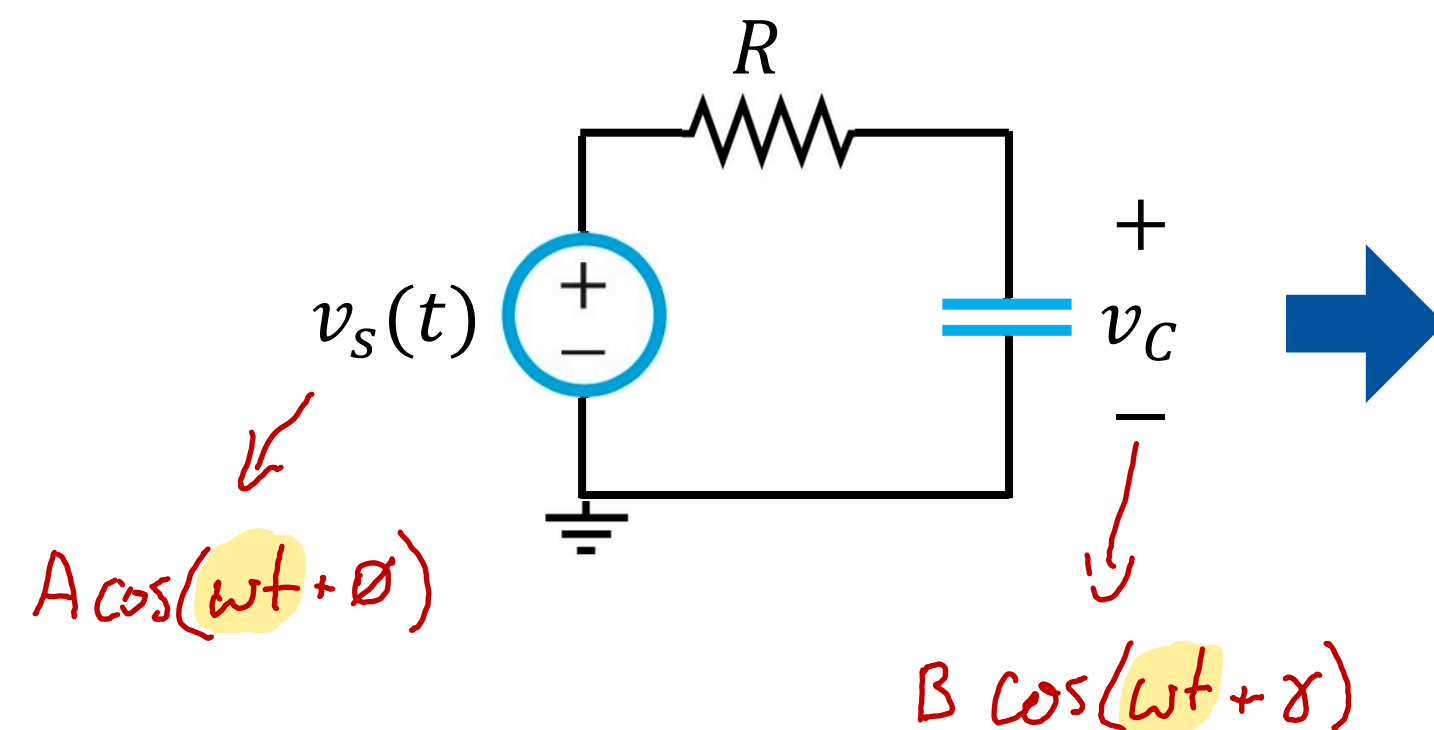- AC circuit: Circuit with a sinusoidal source.
- AC circuit with capacitors or inductors is described by a differential equation.
 - May be challenging to solve because i-v relationships are time dependent.



Phasor domain

- Sinusoidal signals can be represented as complex numbers.
- Differential equations get converted into linear equations with no sinusoidal functions.



- The phasor-analysis technique transforms equations from the time domain to the phasor domain.

Time domain:

time is increase

$$v(t) = A \cos(\omega t + \varphi)$$

$$= \text{Real} \{ A e^{(\omega t + \varphi)j} \}$$

same ω

$$= \text{Real} \{ \underbrace{A e^{\varphi j}}_{\text{Real}} + \underbrace{e^{\omega t j}}_{\text{Same for everything}} \}$$

Phasor domain:

phasor is bold

$$\mathbf{V}(j\omega) = A e^{\varphi j}$$


Frequency is common to all voltages and currents, so it is avoided in the phasor form.

Euler's identity:

$$Z = m e^{\theta j}$$

\downarrow
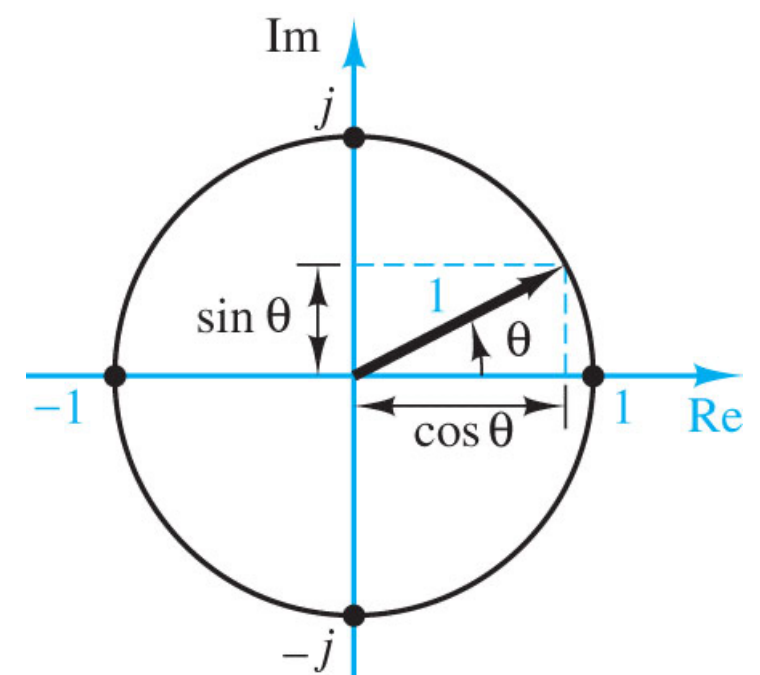
$$Z = \underbrace{m \cos(\theta)}_{\text{real}} + \underbrace{m \sin(\theta)j}_{\text{imaginary}}$$





Time domain:

$$v_1(t) = A \cos(\omega t + \varphi) = 10 \cos(5t + 45)$$

$$v_2(t) = A \cos(\omega t) = \cos(100t)$$

$$v_3(t) = A \cos(\omega t - 90^\circ) = 5 \cos(t - 90)$$

$$v_4(t) = A \sin(\omega t) = 20 \sin(2t) \\ \hookrightarrow 20 \cos(2t - 90)$$

$$\frac{dv(t)}{dt}$$

$$\int v(t) dt$$

Phasor domain:

$$\mathbf{V}_1(5j) = 10e^{45j}$$

$$\mathbf{V}_2(100j) = 1e^{0j} = 1$$

$$\mathbf{V}_3(1j) = 5e^{-90j} = -5j$$

$$\mathbf{V}_4(2j) = 20e^{-90j} = -20j$$




- i - v relationships of resistors, inductors, and capacitors can be expressed in phasor notation.
- Phasors and impedance simplify AC circuit analysis.
 - Allow use of same solution methods as DC circuits.




i-v relationships of resistors, inductors, and capacitors can be expressed in phasor notation.

Time domain:

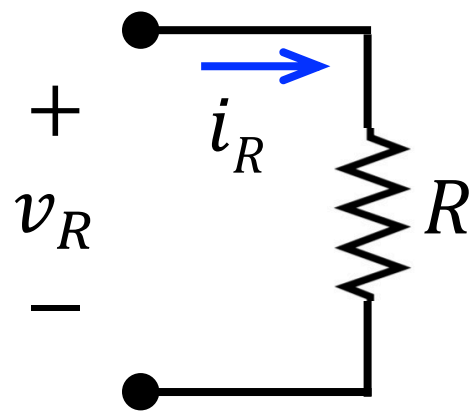

Impedance: Ratio of phasor voltage to phasor current.

Phasor domain:

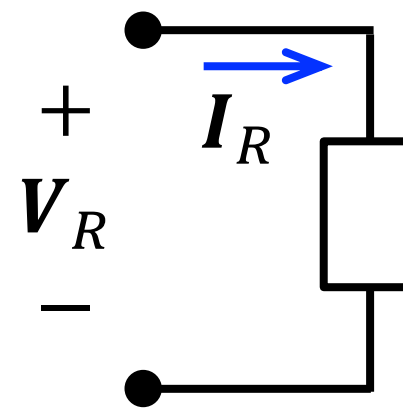





Impedance: Ratio of phasor voltage to phasor current.

$$Z = \frac{V}{I}$$

Time domain:

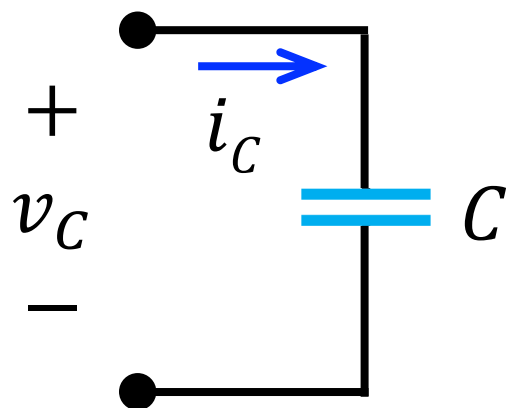

Phasor domain:

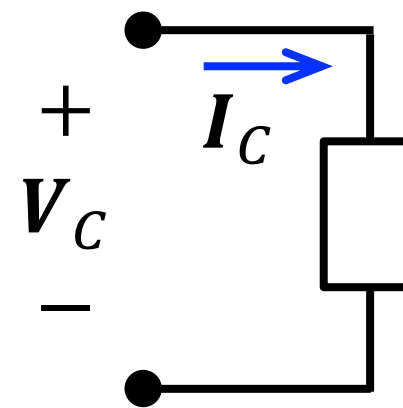





Impedance: Ratio of phasor voltage to phasor current.

$$Z = \frac{V}{I}$$

Time domain:

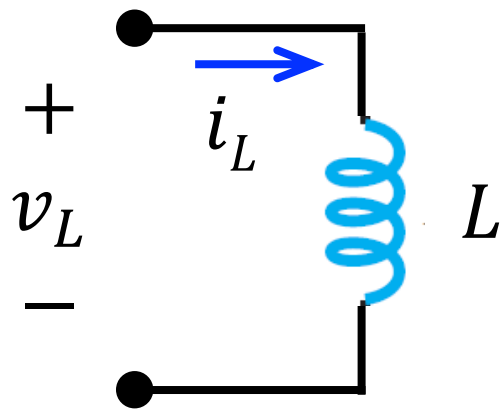

Phasor domain:

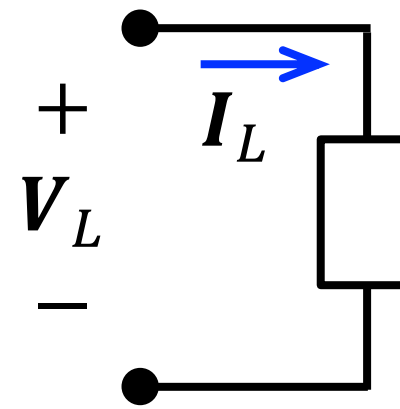



Rectangular form

Polar form

$$V = IZ$$

Resistor: $Z_R = R$

Capacitor: $Z_C = \frac{1}{j\omega C}$

Inductor: $Z_L = j\omega L$

